

Unit - II

2.4 Mesh Analysis Problems

Dr.Santhosh.T.K.

Syllabus

UNIT – II

14 Periods

DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.



AC Steady-state Analysis: AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits

Steps of Mesh Analysis

1. Identify mesh (loops).
2. Assign a current to each mesh. \rightarrow clockwise
3. Apply KVL around each loop to get an equation in terms of the loop currents.
 $V = IR \rightarrow$ Resistors \rightarrow drop
4. Solve the resulting system of linear equations for the mesh/loop currents.

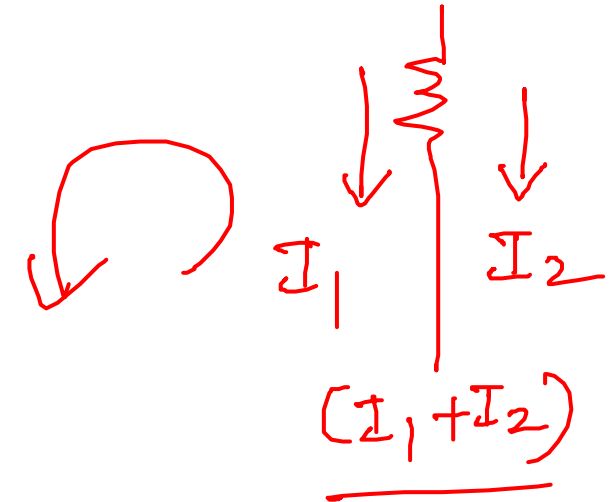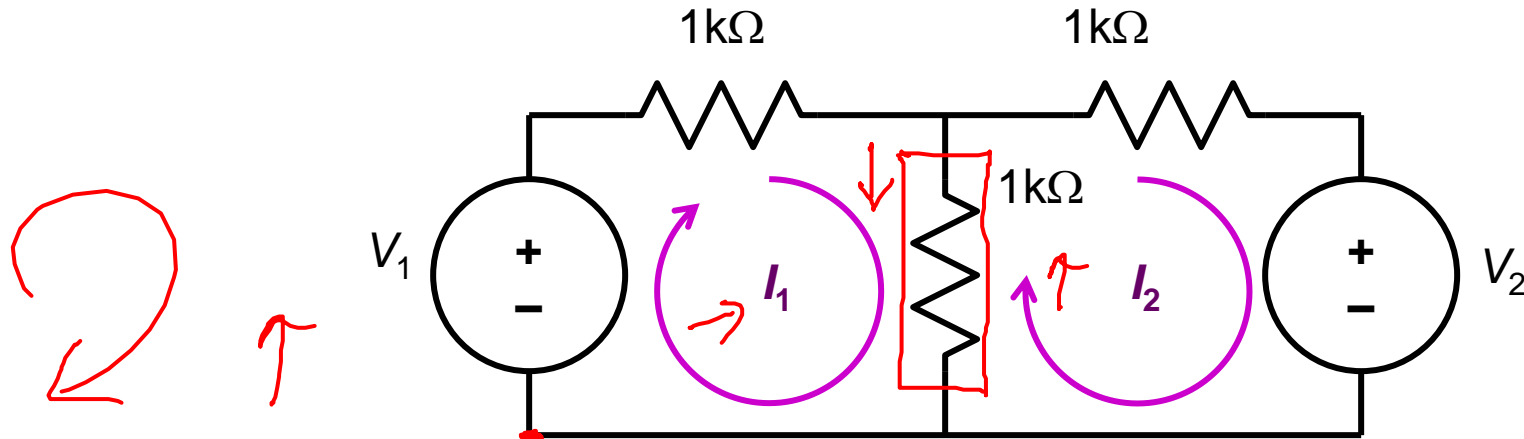
3. KVL Around Mesh 1

$$\rightarrow +V_1 - I_1 (1k) - (I_1 - I_2) 1k = 0$$



$$\begin{aligned} +V_1 - I_1 1k\Omega - (I_1 - I_2) 1k\Omega &= 0 \\ I_1 1k\Omega + (I_1 - I_2) 1k\Omega &= V_1 \\ \rightarrow I_1 2k\Omega - I_2 1k\Omega &= V_1 \end{aligned}$$

3. KVL Around Mesh 2

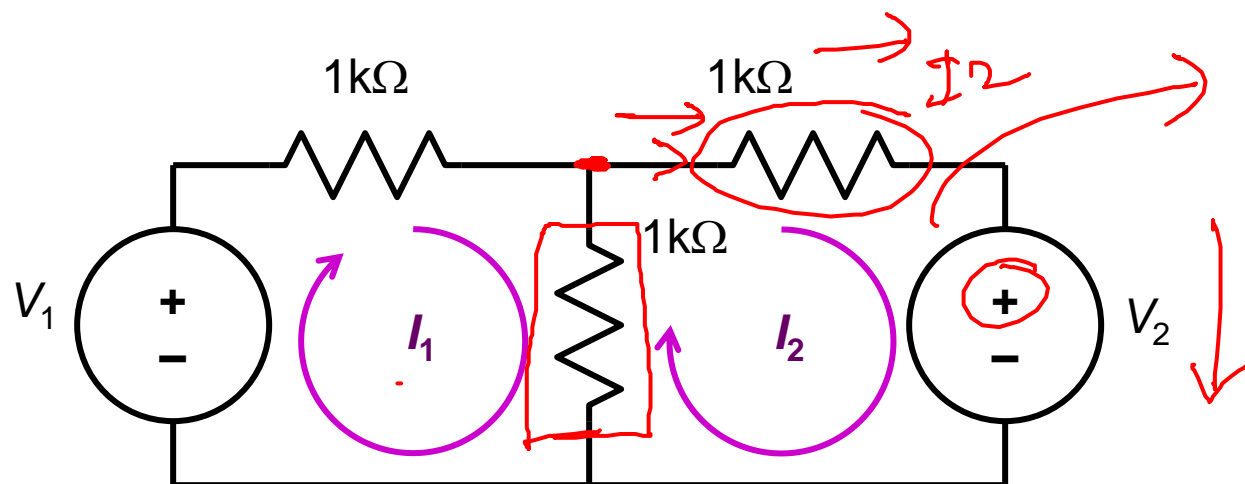

$$V_1 = 7V$$

$$V_2 = 4V$$

$$I_1 \text{ \& } I_2$$

$$V = I^2$$

$$-I_2(1k) - V_2 - 1k(I_2 - I_1) = 0$$

$$-(I_2 - I_1) 1k\Omega - I_2 1k\Omega - V_2 = 0$$

$$(I_2 - I_1) 1k\Omega + I_2 1k\Omega = -V_2$$

$$-I_1 1k\Omega + I_2 2k\Omega = -V_2$$

$$I_1(2k) - I_2(1k) = V_1$$

2

1

4. Solving the Equations

Let: $V_1 = 7V$ and $V_2 = 4V$

Results:

$$I_1 = 3.33 \text{ mA}$$

$$I_2 = -0.33 \text{ mA} \quad \leftarrow$$

Finally

$$V_{out} = (I_1 - I_2) 1k\Omega = 3.66V$$

Matrix Notation

- The two equations can be combined into a single matrix/vector equation

$$\begin{aligned}
 & \begin{matrix} \rightarrow I_2 - I_1 \\ \rightarrow I_1 - I_2 \end{matrix} \\
 & I_1 \cdot 2\text{k}\Omega - I_2 \cdot 1\text{k}\Omega = V_1 \\
 & -I_1 \cdot 1\text{k}\Omega + I_2 \cdot 2\text{k}\Omega = -V_2
 \end{aligned}$$

Resistance matrix


$$\begin{bmatrix} 1\text{k}\Omega + 1\text{k}\Omega & -1\text{k}\Omega \\ -1\text{k}\Omega & 1\text{k}\Omega + 1\text{k}\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ -V_2 \end{bmatrix}$$

\swarrow +ve
 \searrow -ve
 R
 $I = V$

Inspection Method

$a_{11} \rightarrow$ Sum of resistances in mesh 1 ✓

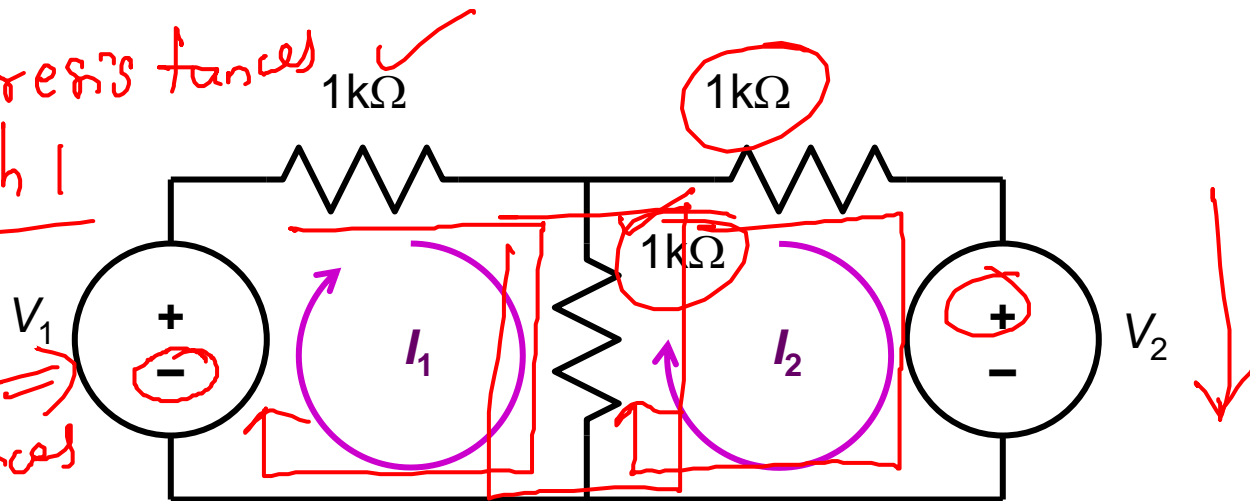$a_{22} \rightarrow$ Sum of resistances in mesh 2.



$$a_{12} \rightarrow -1k = a_{21}$$

$$\begin{bmatrix} 1k\Omega + 1k\Omega & -1k\Omega \\ -1k\Omega & 1k\Omega + 1k\Omega \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} +V_1 \\ -V_2 \end{bmatrix}$$

Practice Problem

Determine the power dissipation in the 4Ω resistor of the given network.



- ① 3 mesh
- ② I_1, I_2, I_3
- ③ KVL \rightarrow Inspection.

$$\begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -4 \\ 0 & -4 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} +60 \\ 0 \\ -20 \end{bmatrix}$$

\downarrow (R) (I) (V)

$$a_{11} = 5 + 3 = 8$$

$$a_{22} = 3 + 4 + 2 = 9$$

$$a_{23} = a_{32} =$$

$$a_{33} = 6 + 4 = 10$$

$$a_{12} = a_{21} = -3$$


$$a_{13} = a_{31} = 0$$

Problem

~~Cramer's~~

999m

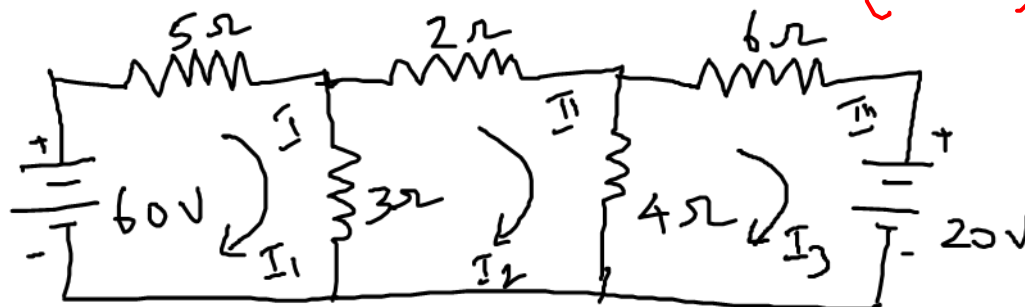Determine the power dissipation in the 4Ω resistor of the given network.



(Thrice) Mode

Eqn (1)

3

→ Cramer's rule

→ Calculator

→ Simultaneous eqn

$$ax + by + cz = d$$

$$\begin{array}{cccc} \downarrow & & & \\ \underline{a_{11}} & a_{12} & a_{13} & d_1 \\ a_{21} & a_{22} & a_{23} & d_2 \\ a_{31} & a_{32} & a_{33} & d_3 \\ & & \downarrow & \\ & & = & \rightarrow \end{array}$$

Mode
↓
Matrix

↓
Dimension
(3x3)

↓
Enter Values

MAT A

↓
dim-3

↓
a₁₁ → All
Values

Det(MAT A) ✓

Cramer's rule

$$\Delta = |R|$$

$$\begin{vmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{vmatrix}$$

$$\underline{\Delta I_1} =$$

$$\Delta I_2 =$$

$$\Delta I_3 =$$

$$\begin{vmatrix} V_1 \\ V_2 \\ V_3 \end{vmatrix}$$


$$\begin{vmatrix} a_{12} & a_{13} \\ a_{22} & a_{23} \\ a_{32} & a_{33} \end{vmatrix}$$

$$\rightarrow I_1 = \frac{\Delta I_1}{\Delta}$$

$$\begin{aligned} I_1 &= 8.36 \text{ A} \\ I_2 &= 2.31 \text{ A} \\ I_3 &= -1.07 \text{ A} \end{aligned}$$

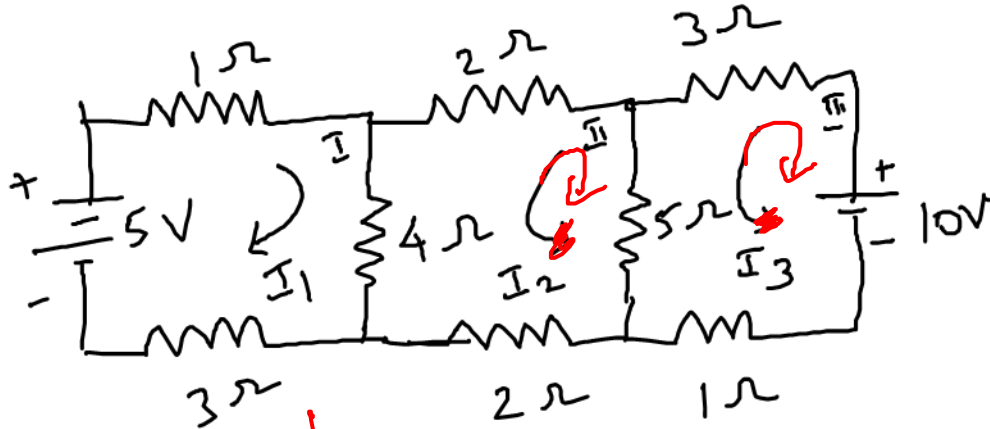Problem

- Find the mesh current and determine the power supplied by each of the voltage source in the given circuit.




$$\begin{aligned} I_1 &= 1.1 \text{ A} \\ I_2 &= 0.97 \text{ A} \\ I_3 &= 1.65 \text{ A} \end{aligned}$$

$$\begin{bmatrix} 8 & -4 & 0 \\ -4 & 13 & -5 \\ 0 & -5 & 9 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} +5 \\ 0 \\ -10 \end{bmatrix}$$

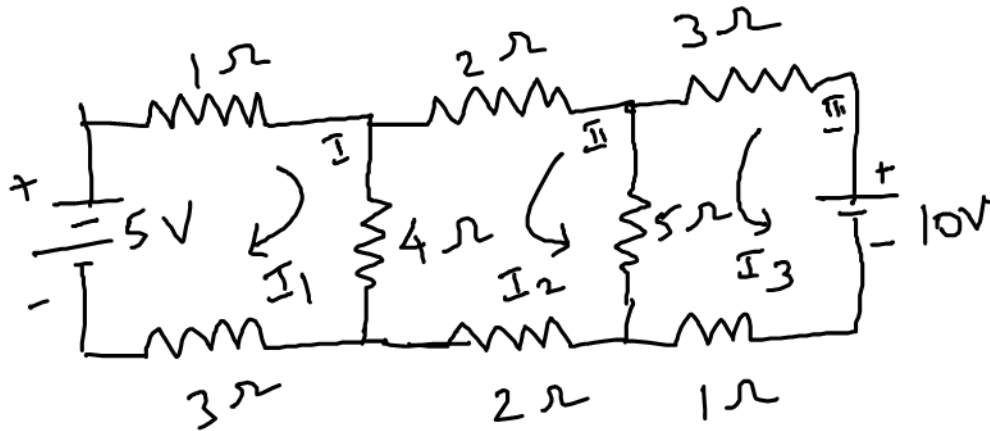
Problem

- Find the mesh current and determine the power supplied by each of the voltage source in the given circuit.




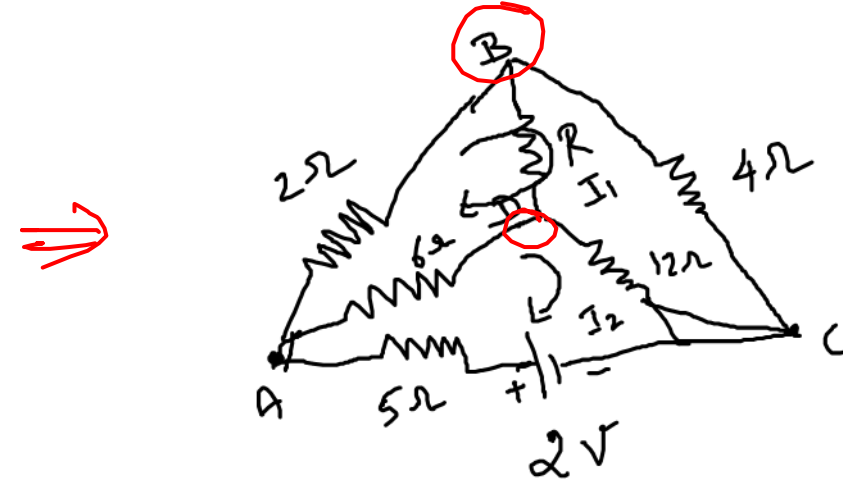Exercise


- Find the mesh currents in the given network when the current through the branch BD is zero.



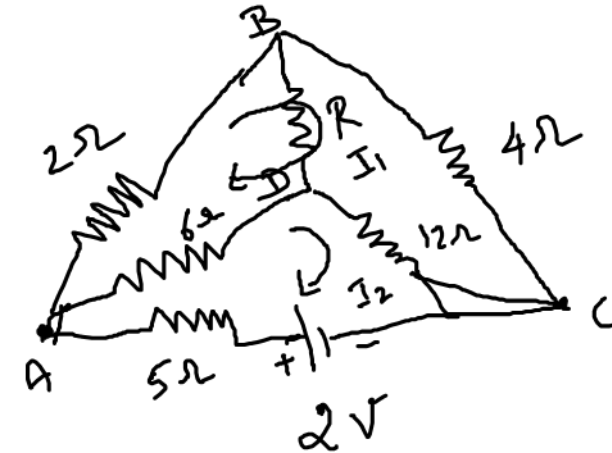- Find the mesh currents in the given network when the current through the branch BD is zero.



Cramer's Rule

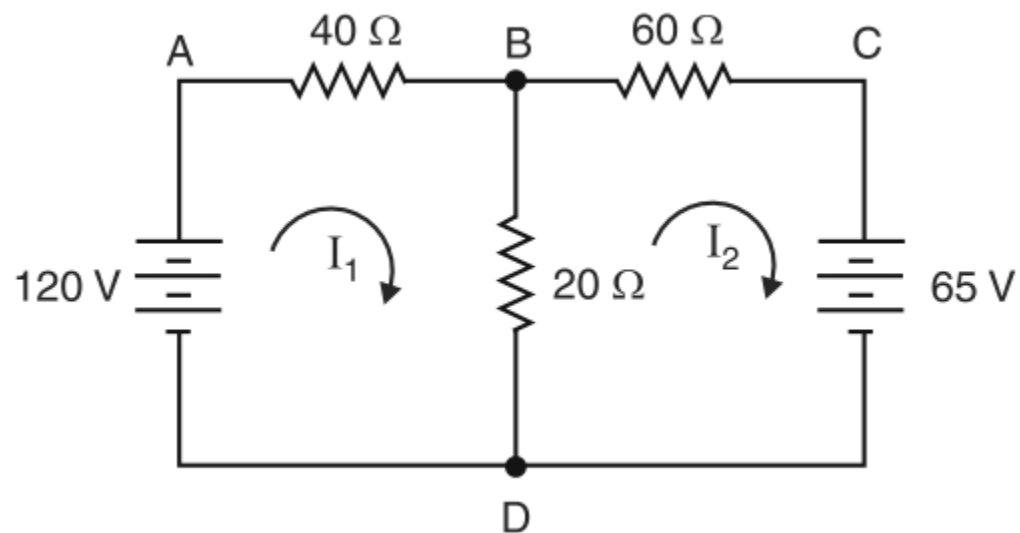

$$\begin{aligned}60I_1 - 20I_2 &= 120 \\ -20I_1 + 80I_2 &= -65\end{aligned}$$

$$I_1 = \frac{\begin{vmatrix} 120 & -20 \\ -65 & 80 \end{vmatrix}}{\begin{vmatrix} 60 & -20 \\ -20 & 80 \end{vmatrix}} = \frac{(120 \times 80) - (-65 \times -20)}{(60 \times 80) - (-20 \times -20)} = \frac{8300}{4400} = 1.886 \text{ A}$$

$$I_2 = \frac{\begin{vmatrix} 60 & 120 \\ -20 & -65 \end{vmatrix}}{\text{Denominator}} = \frac{(60 \times -65) - (-20 \times 120)}{4400} = \frac{-1500}{4400} = -0.341 \text{ A}$$

Advantages of Loop Analysis

- Solves directly for some currents
- Voltage sources are easy
- Current sources are either very easy or somewhat difficult
- Works best for circuits with few loops

Disadvantages of Loop Analysis

- Some currents must be computed from loop currents
- Does not work with non-planar circuits
- Choosing the supermesh may be difficult.

Summary

