

Principles of Electrical Engineering

Dr.Santhosh.T.K.

November 21, 2022

Assignment - 1

1. Find the equivalent resistance between the terminals 'A' & 'B'.

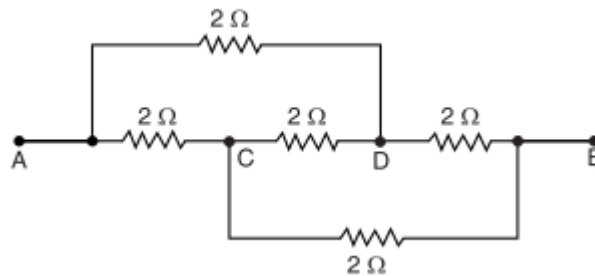


Figure 1:

2. For the circuit shown in Figure 2, find the currents flowing in all branches using Mesh Analysis.

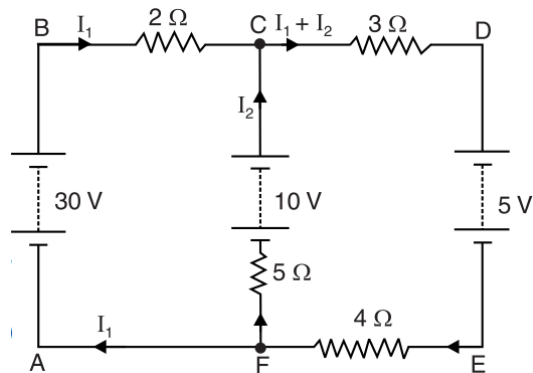


Figure 2:

3. Show that the node voltage v_0 is the average of the two input voltages using the method of superposition in the circuit shown in Figure 3.

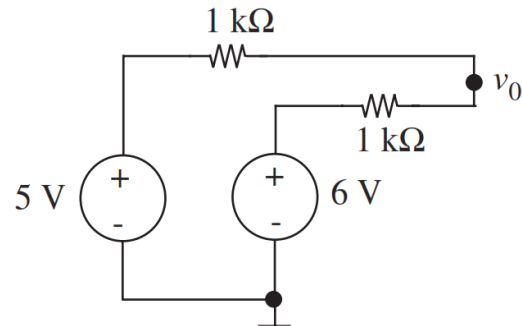


Figure 3:

4. Find the resistance of 1000 metres of a copper wire 25sq.mm in cross-section. The resistance of copper is $1/58$ ohm per metre length and 1 sq. mm cross-section. What will be the resistance of another wire of the same material, three times as long and one-half area of cross-section ?
5. With the help of star/delta transformation, obtain the value of current supplied by the battery in the circuit shown in Figure 4.

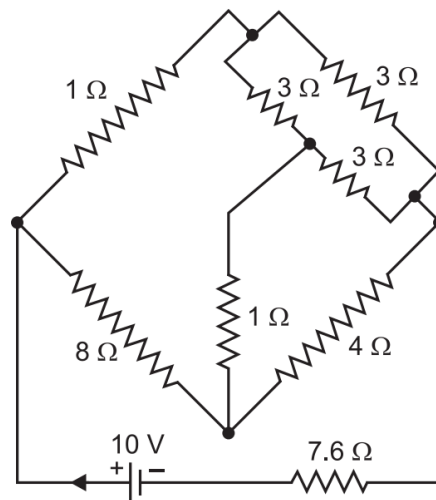


Figure 4:

6. Determine the current in 4Ω resistance of the circuit shown in Figure 5 .

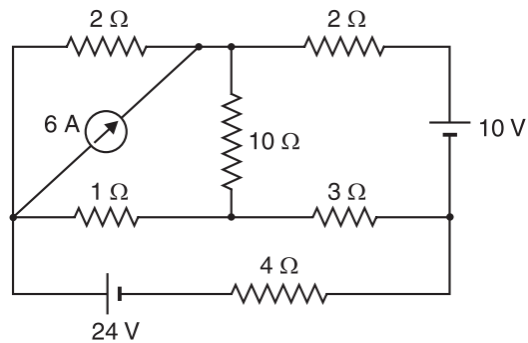


Figure 5:

7. Determine the currents I_1 , I_2 and I_3 for the circuit shown in Figure 6 using superposition theorem.

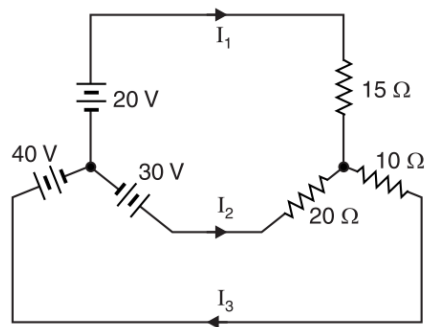


Figure 6:

8. Find the Thevenin equivalent circuit lying to the right of terminals x - y in Figure 7.

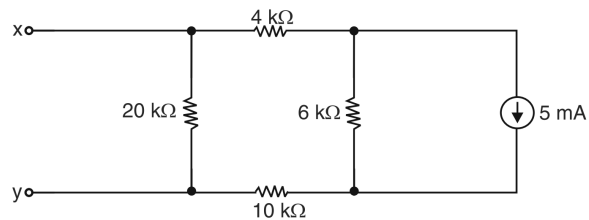


Figure 7:

9. Using Thevenin's theorem, find the voltage across $3\ \Omega$ resistor in Figure 8.

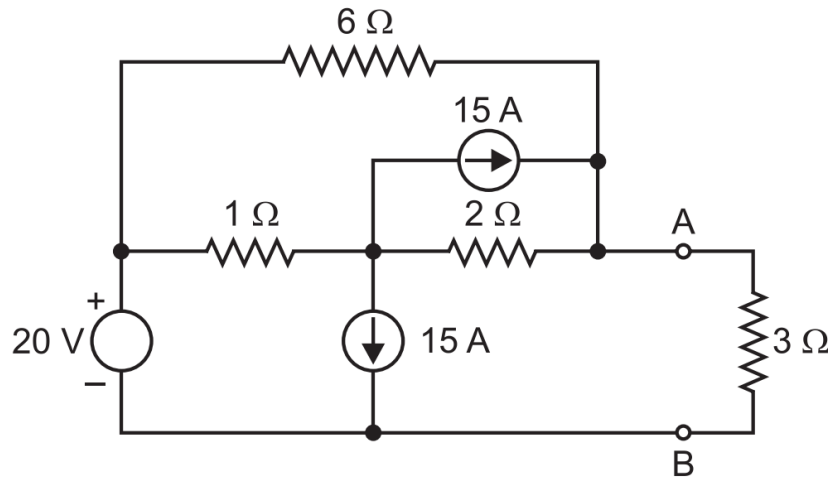


Figure 8:

10. For the circuit shown in Figure 9, find the value of R that will receive maximum power. Determine this power.

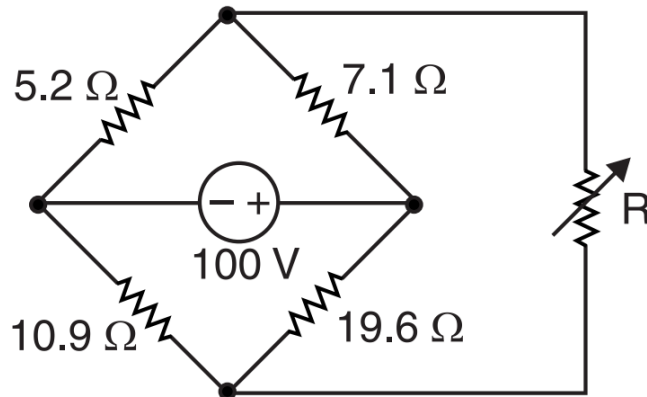


Figure 9: