

Unit - II

2.17 Three Phase Balanced Circuits

Dr.Santhosh.T.K.

Syllabus

UNIT – II

14 Periods

DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

AC Steady-state Analysis: AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits


Polyphase Circuits

Polyphase circuits contain multiple sources at the same frequency but different phases. Power is distributed over the power grid in the form of three-phase sinusoids.

Advantages of Three-Phase power distribution include:

- (Constant Power) Instantaneous power can be constant in a three phase system.
- (More Economical) For equivalent power, the 3-Phase systems are more economical than single-phase (can be driven with lower currents and voltages, and fewer wires required because of a common neutral connection between the phases).
- (Flexible) Single phase service can be extracted from the 3-phase systems or phases manipulated to create additional phases.


Three-Phase Power

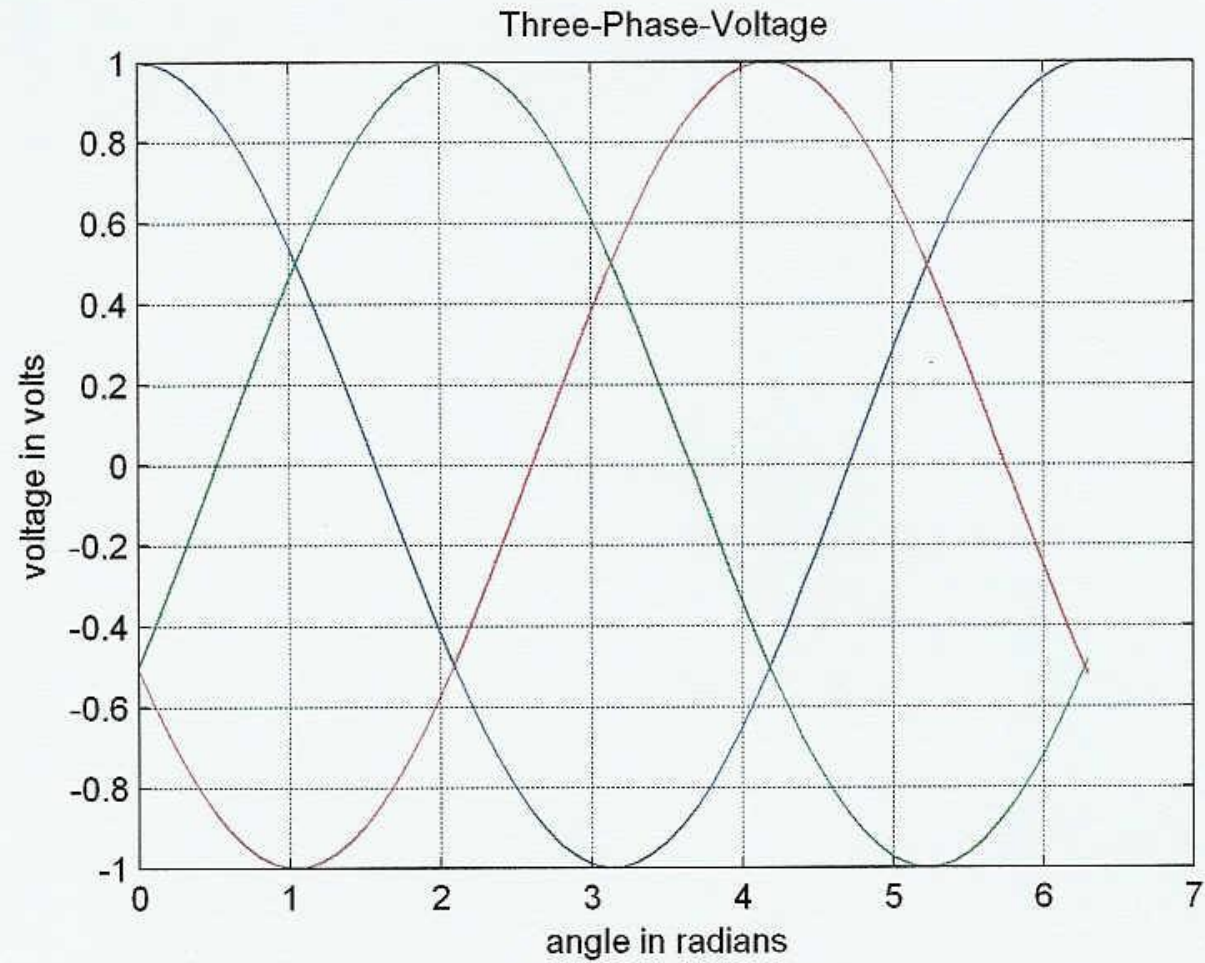


Definitions

- 4 wires
 - 3 “active” phases, A, B, C
 - 1 “ground”, or “neutral”
- Color Code
 - Phase A Red
 - Phase B Black
 - Phase C Blue
 - Neutral White or Gray

Phasor (Vector) Form for abc

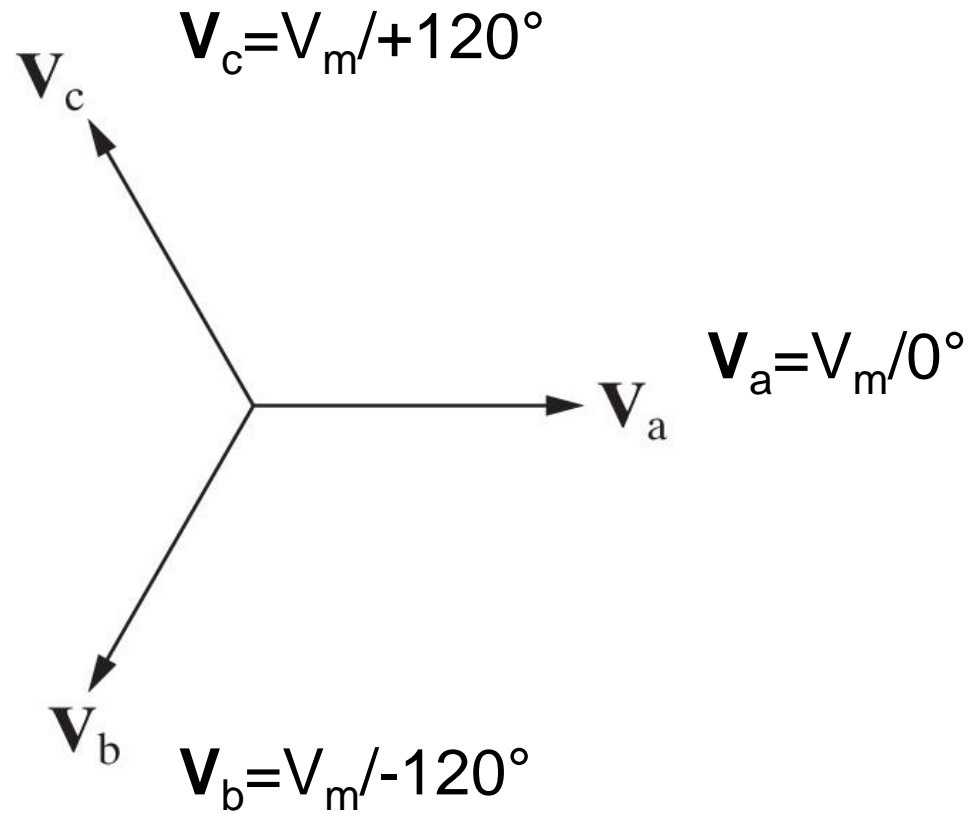


Phasor (Vector) Form for abc

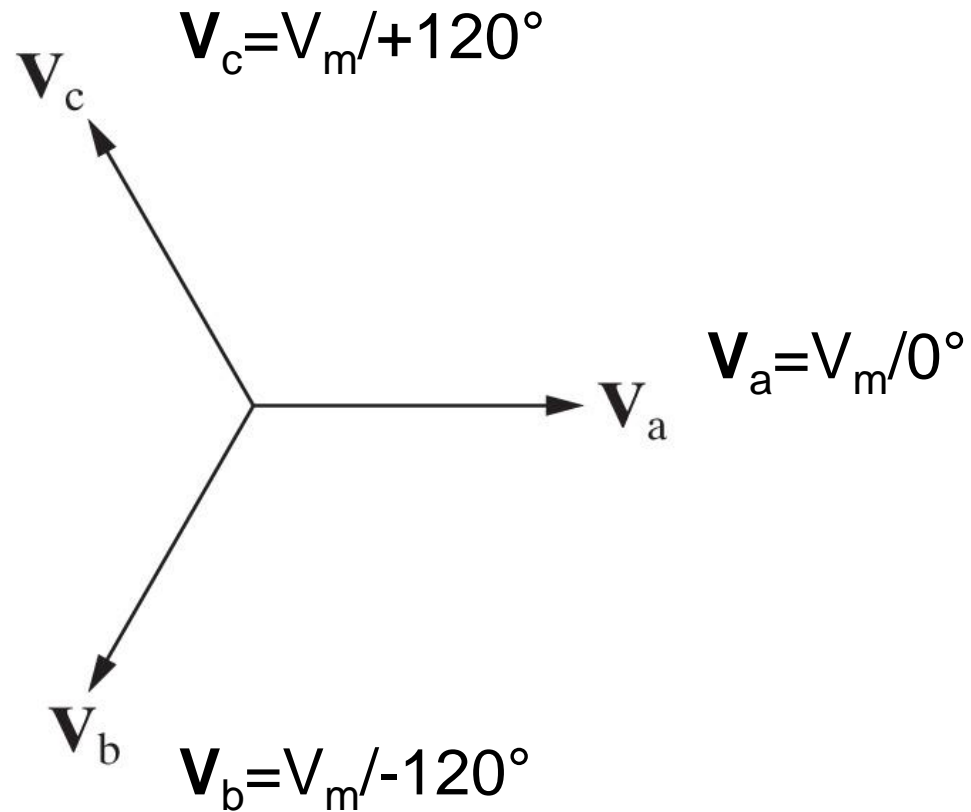


Note that KVL applies $\mathbf{V}_a + \mathbf{V}_b + \mathbf{V}_c = 0$

Three-Phase Voltages

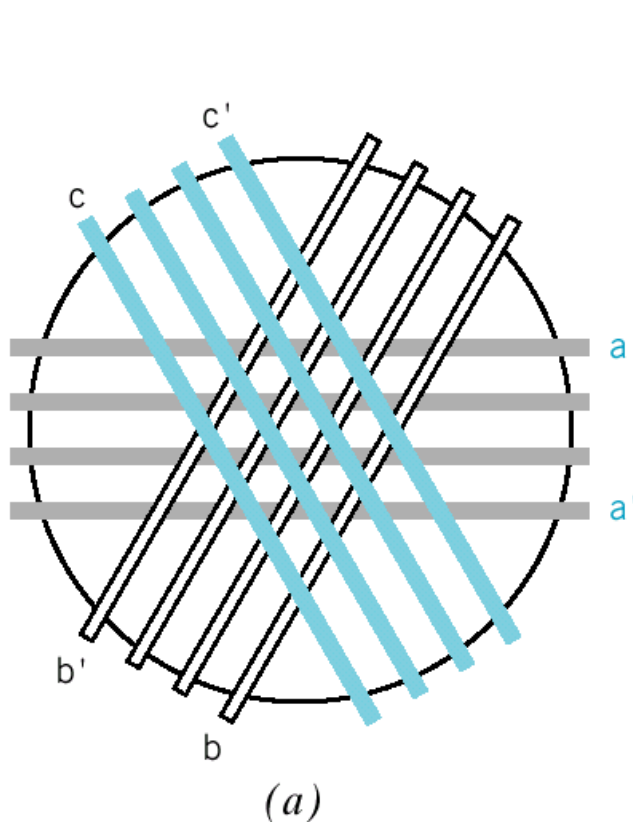

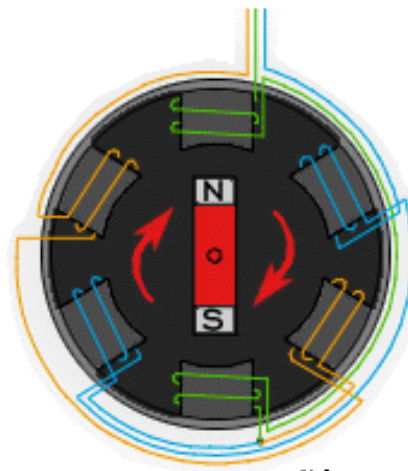
(a) The three windings on a cylindrical drum used to obtain three-phase voltages



$$v_{aa'} = \sqrt{2} V \cos \omega t$$


$$v_{bb'} = \sqrt{2} V \cos(\omega t - 120^\circ)$$
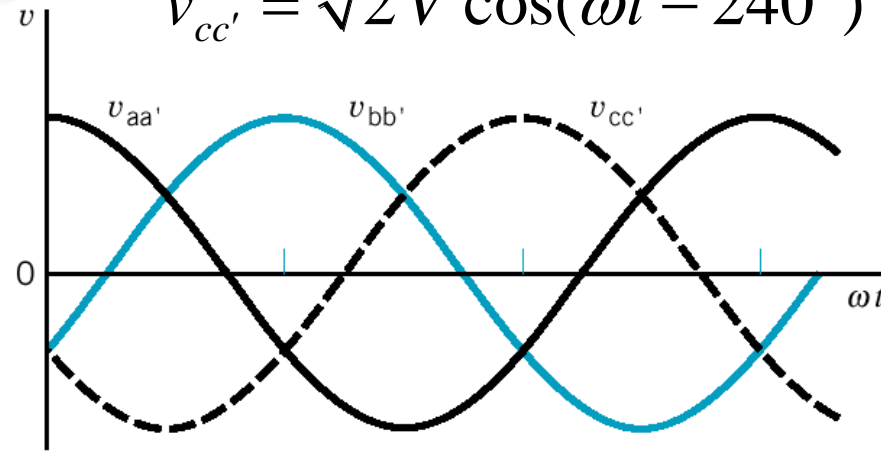
$$v_{cc'} = \sqrt{2} V \cos(\omega t - 240^\circ)$$




(b) Balanced three-phase voltages

Three-Phase Voltages

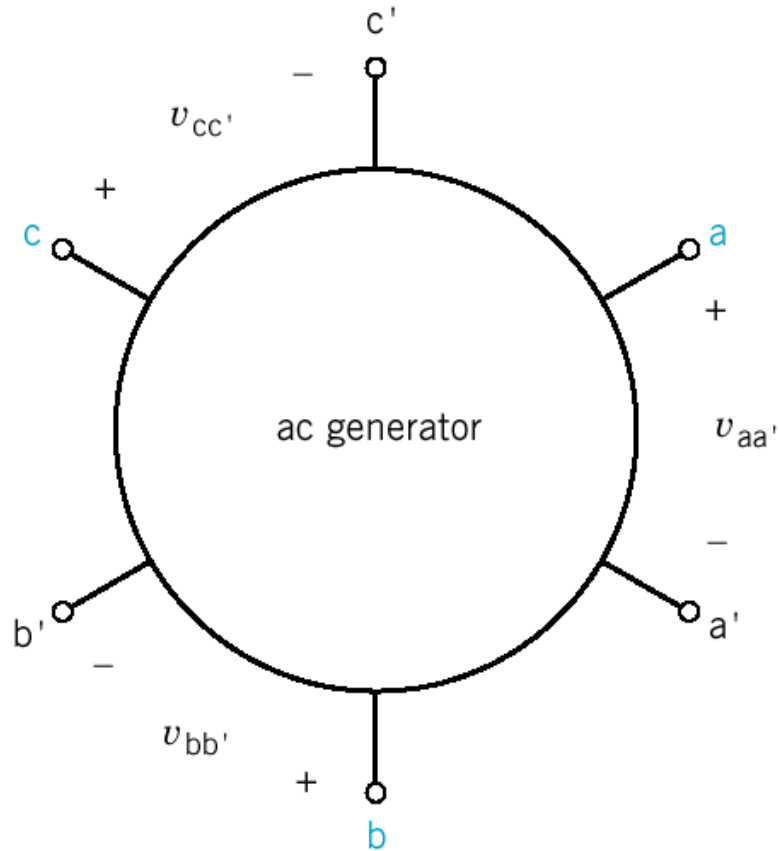

Generator with six terminals

Three-Phase Balanced Voltages

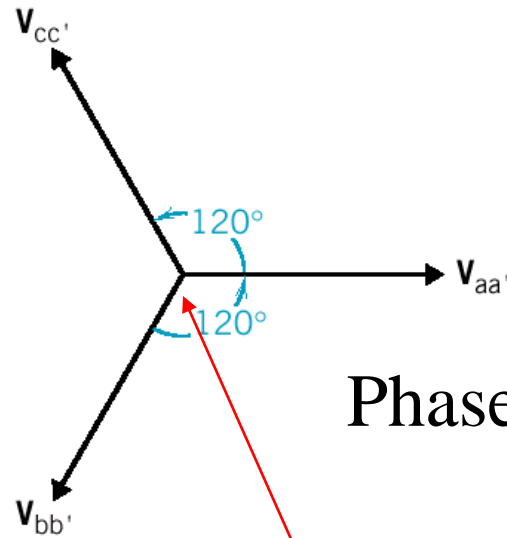


$$V_{aa'} = V \angle 0^\circ$$

$$V_{bb'} = V \angle -120^\circ$$

$$V_{cc'} = V \angle -240^\circ = V \angle +120^\circ$$

Phase sequence or phase rotation is *abc*
Positive Phase Sequence

neutral terminal

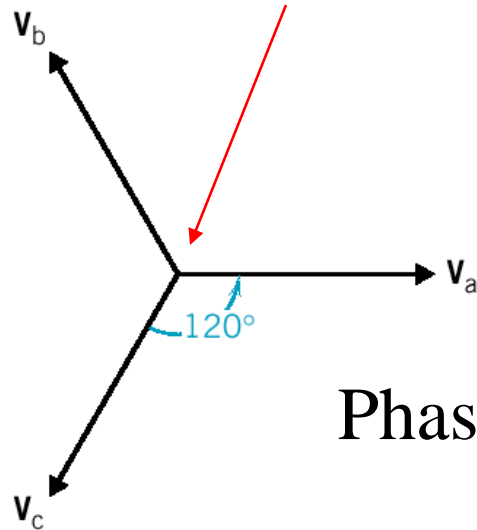


$$V_a = V \angle 0^\circ$$

$$V_c = V \angle -120^\circ$$

$$V_b = V \angle -240^\circ = V \angle +120^\circ$$

Phase sequence or phase rotation is *acb*
Negative Phase Sequence

Two Common Methods of Connection

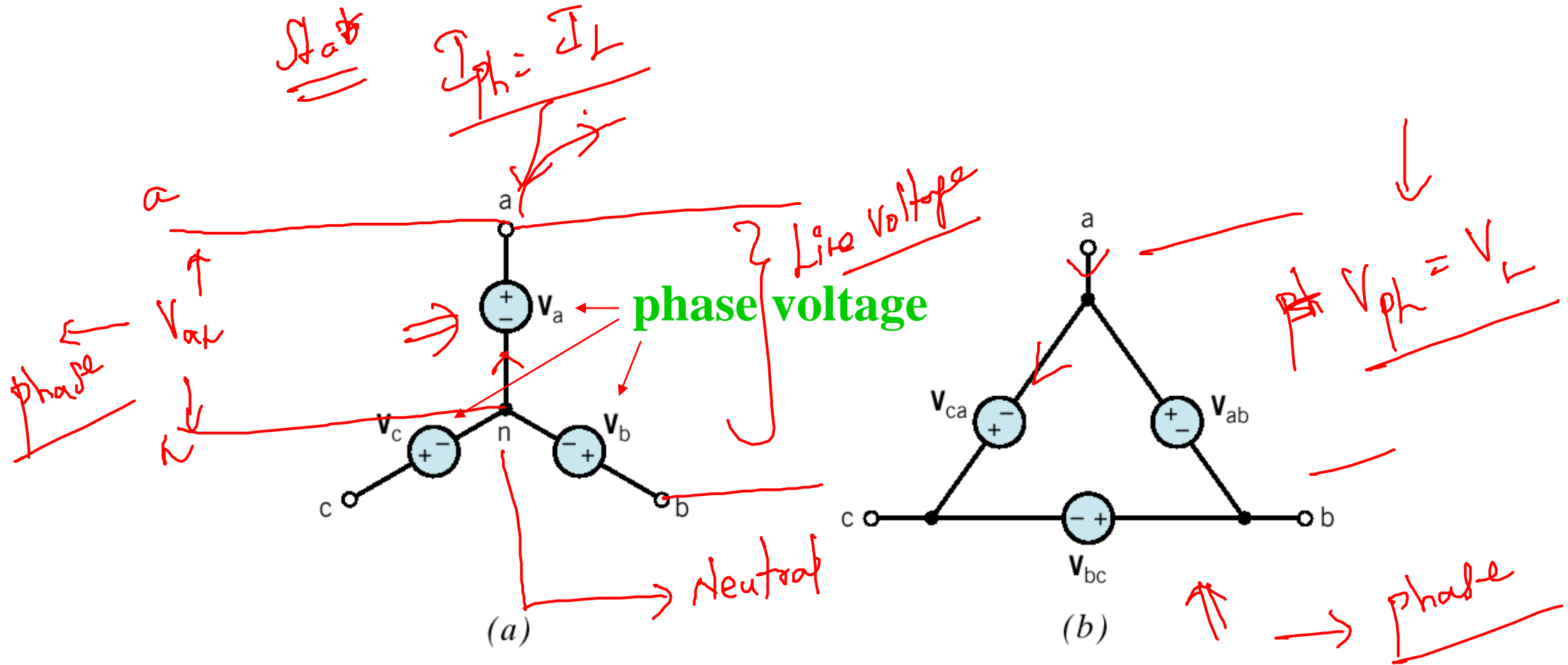


(a) Y-connected sources (b) Δ -connected sources

Star

Delta

Phase and Line Voltages

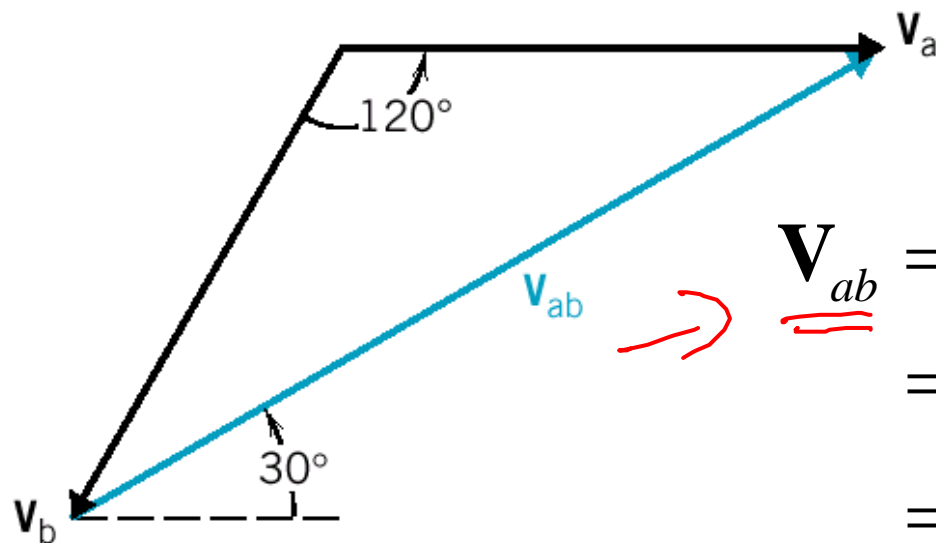

$$\begin{aligned}
 \underline{\underline{V_{ab}}} &= \underline{\underline{V_a}} - \underline{\underline{V_b}} \\
 &= \underline{V_p \angle 0^\circ} - \underline{V_p \angle -120^\circ} \\
 &= V_p - V_p(-0.5 - j0.866)
 \end{aligned}$$

The line-to-line voltage V_{ab} of the Y-connected source

$$V_L = \sqrt{3}V_p \angle 30^\circ$$

Similarly

$$V_{bc} = \sqrt{3}V_p \angle -90^\circ$$

$$V_{ca} = \sqrt{3}V_p \angle -210^\circ$$

Start

$$\begin{aligned}
 V_L &= \sqrt{3} V_{ph} \\
 I_L &= I_{ph}
 \end{aligned}$$

Single and 3-Phase Circuit Comparison

Consider the phase voltages of equal amplitude

$$|\hat{V}_p| = |\hat{V}_{an}| = |\hat{V}_{bn}| = |\hat{V}_{cn}|$$

Show that the line voltages are given by:



$$|\hat{V}_{ab}| = |\hat{V}_{ac}| = |\hat{V}_{bc}| = \sqrt{3}|\hat{V}_p|$$

In general:

$$\hat{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$$

$$\hat{V}_{bc} = \sqrt{3}V_p \angle -90^\circ$$


$$\hat{V}_{ca} = \sqrt{3}V_p \angle -210^\circ$$

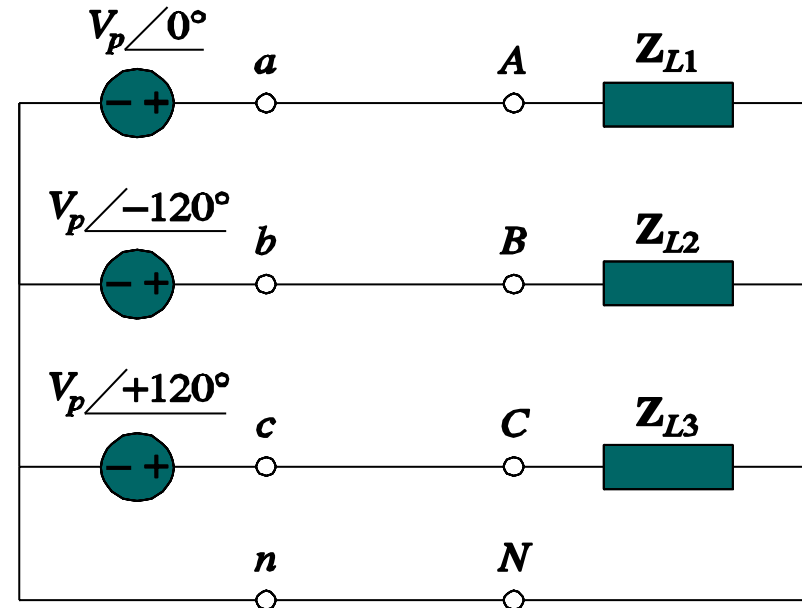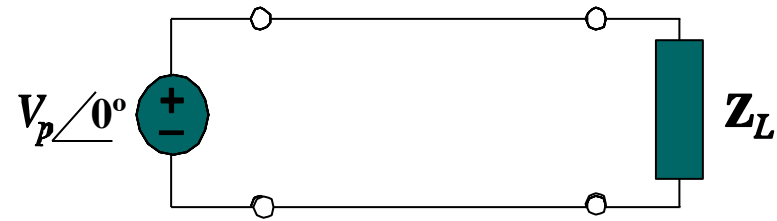

Balanced 3-Phase Voltage Connections

There are 2 ways to connect a Balanced set of sources:

Y (wye)-Connected

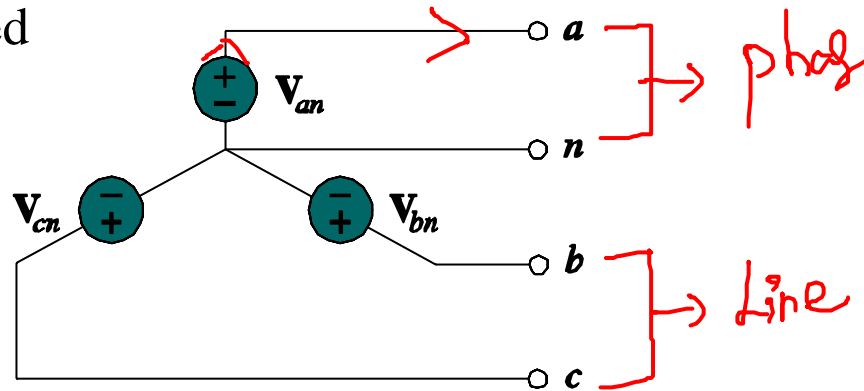

Star

$$I_L = I_{ph}$$


$$V_L = \sqrt{3} \cdot V_{ph}$$

V_{an}
 V_{bn}
 V_{cn}

Power $\rightarrow P = \frac{V I \cos \phi}{\rightarrow}$

$P = \sqrt{3} V_L I_L \cos \phi$

Δ (delta)-Connected

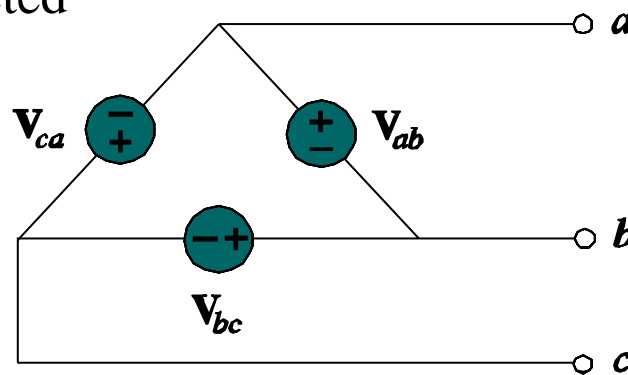

Delta

$$V_{ph} = V_L$$


$$I_L = \sqrt{3} \cdot I_{ph}$$

Balanced Loads


Balanced loads are equal in magnitude and phase.

There 2 ways to connect balanced loads

Y (wye)-Connected

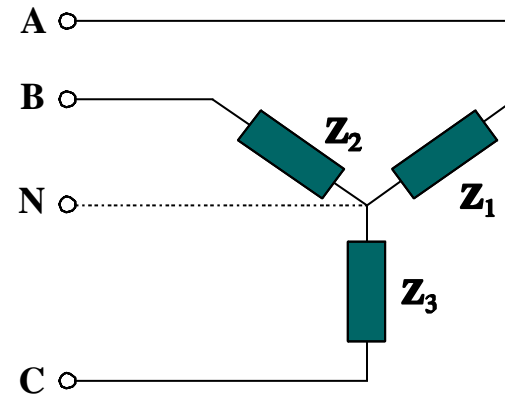

Δ (delta)-Connected

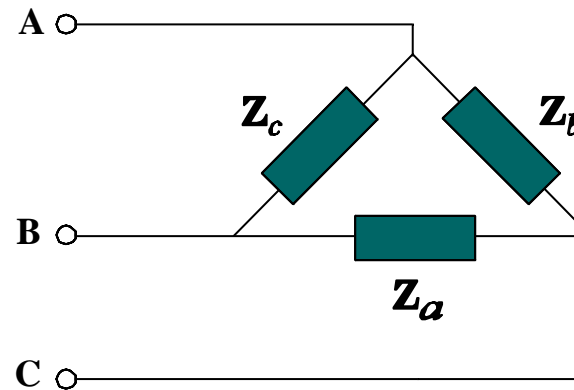

for equivalent loads $Z_{\Delta} = 3Z_Y$

Load-Source Connections


There are 4 possible ways balanced sources and loads can be connected:

- Y Source to Y Load (Y-Y)
- Δ Source to Δ Load (Δ - Δ)
- Y Source to Δ Load (Y- Δ)
- Δ Source to Y Load (Δ -Y)

If not specified, the voltages on the sources will be assumed to be in RMS values.

Balanced Y-Y Connection

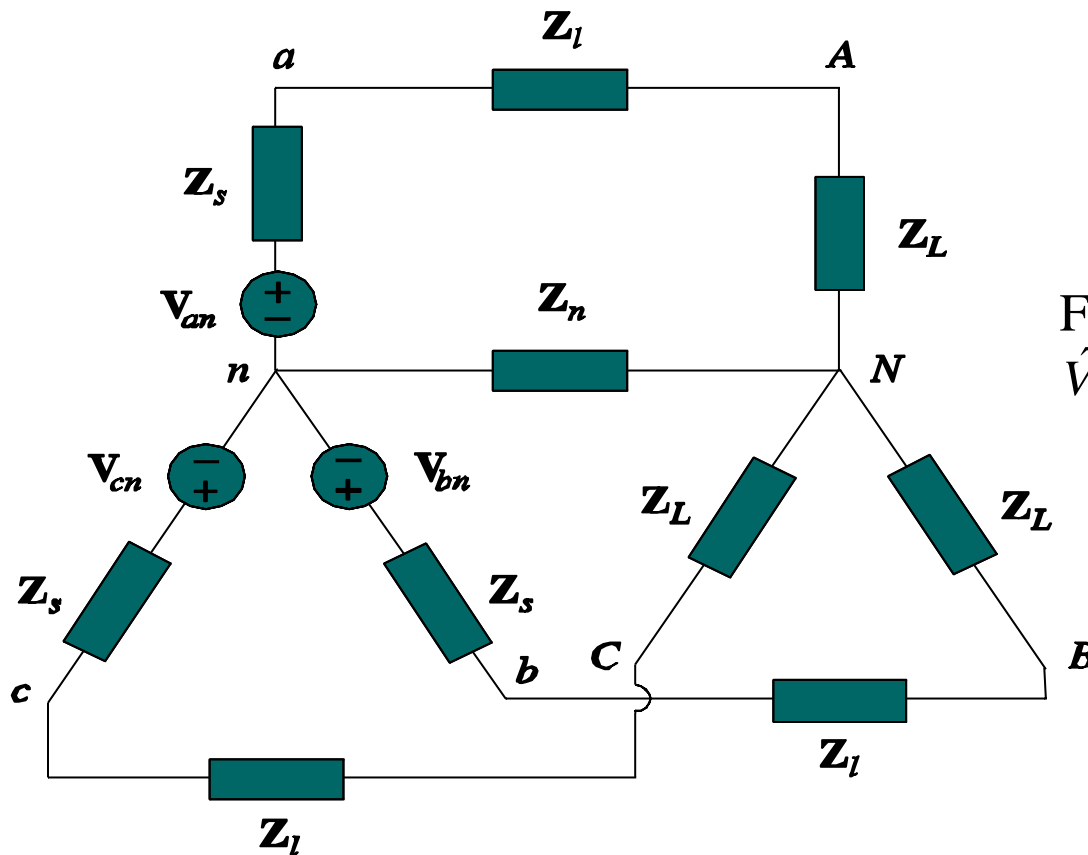The complete Y-Y connection is shown below with impedances listed separately for the source (subscript s), line (subscript l), and load (subscript L).



$$V_p = |\hat{V}_{an}| = |\hat{V}_{an}| = |\hat{V}_{an}|$$

$$V_L = |\hat{V}_{ab}| = |\hat{V}_{bc}| = |\hat{V}_{ca}|$$

For a positive sequence with $\hat{V}_{an} = V_p \angle 0^\circ$, it can be shown that

$$\hat{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$$

$$\hat{V}_{bc} = \sqrt{3}V_p \angle -90^\circ$$


$$\hat{V}_{ca} = \sqrt{3}V_p \angle -210^\circ$$

Balanced Y-Y Connection

Show that the current in each phase can be expressed as:

$$\hat{I}_a = \frac{\hat{V}_{an}}{Z_Y}, \quad \hat{I}_b = \hat{I}_a \angle -120^\circ, \quad \hat{I}_c = \hat{I}_a \angle -240^\circ,$$

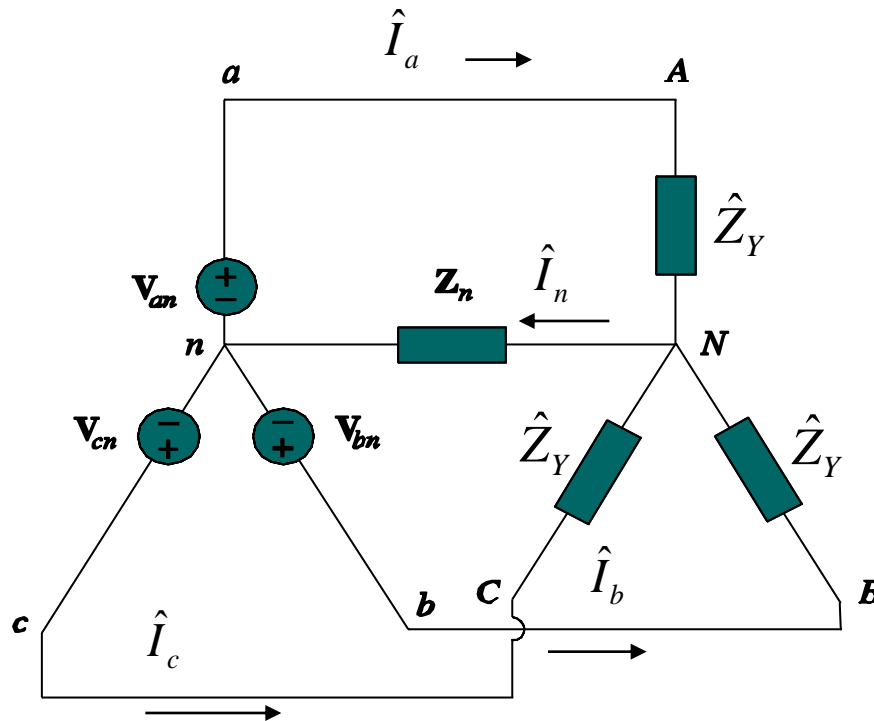and that $\hat{I}_a + \hat{I}_b + \hat{I}_c = \hat{I}_n = 0$



Because of the symmetry of a balanced 3 phase system, the neutral connection can be dropped and the system analyzed on a per phase basis. In a Y-Y connected system, the phase (source or load) and line currents are the same.


Balanced Y-Δ Connection

In this case the line voltages are directly across each load. It can be shown that:

$$\hat{I}_{AB} = \frac{\sqrt{3}\hat{V}_p}{Z_{\Delta}} = \frac{\hat{V}_{ab}}{Z_{\Delta}} = \frac{\hat{V}_{AB}}{Z_{\Delta}}, \quad \hat{I}_{BC} = \hat{I}_{AB} \angle -120^{\circ}, \quad \hat{I}_{CA} = \hat{I}_{AB} \angle -240^{\circ}$$

and the load currents and phase currents are related by:
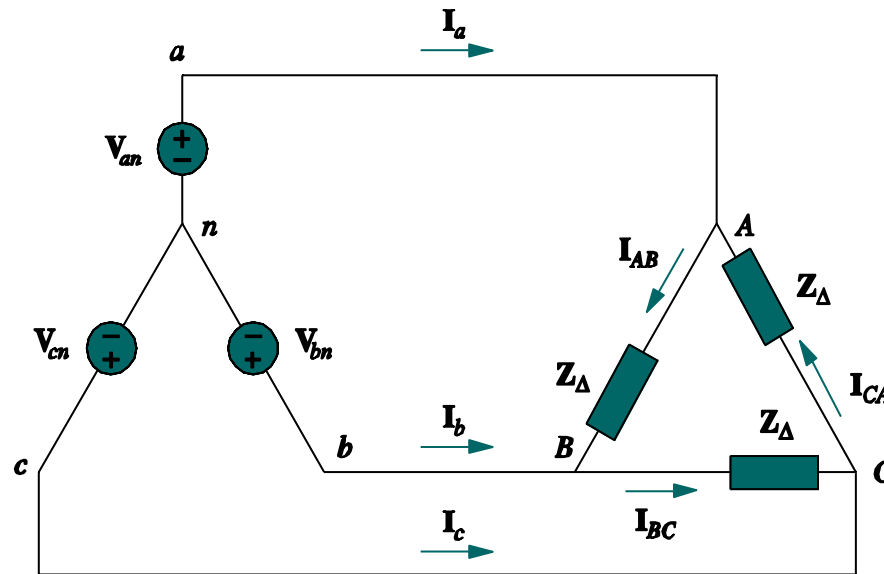
$$\hat{I}_a = \hat{I}_{AB} \sqrt{3} \angle -30^{\circ}$$



Note the Δ-connected load can be converted to a Y-connected load through:

$$\hat{Z}_Y = \frac{\hat{Z}_{\Delta}}{3}$$


Balanced Δ - Δ Connection

In this case the line voltages are the phase voltages and are directly across each load. It can be shown that:

$$\hat{I}_{AB} = \frac{\hat{V}_{ab}}{Z_{\Delta}} = \frac{\hat{V}_{AB}}{Z_{\Delta}}, \quad \hat{I}_{BC} = \hat{I}_{AB} \angle -120^{\circ}, \quad \hat{I}_{CA} = \hat{I}_{AB} \angle -240^{\circ}$$

The line currents can be obtained from the phase currents
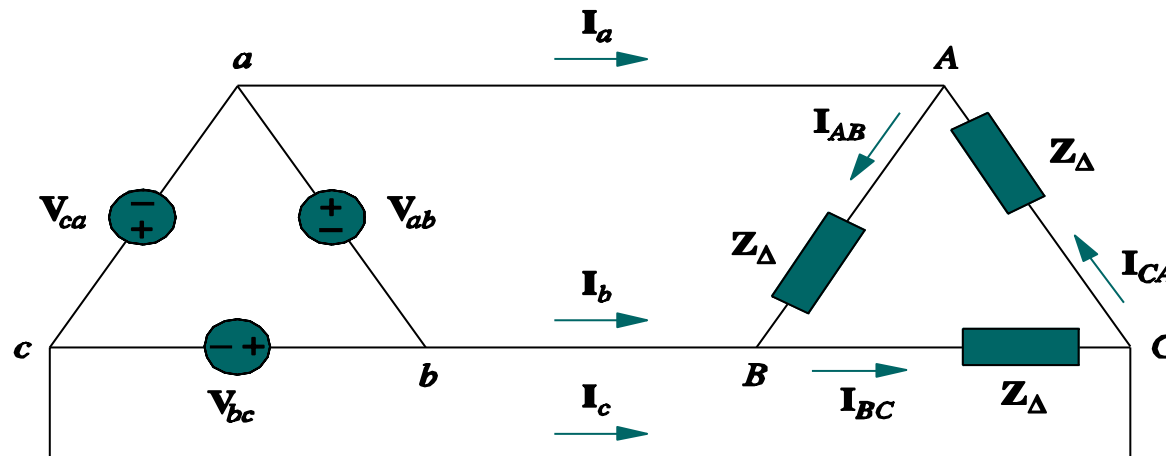
$$\hat{I}_a = \hat{I}_{AB} \sqrt{3} \angle -30^{\circ}$$




Balanced Δ -Y Connection

In this case the phase voltages are across the lines. It can be shown that:

$$\hat{V}_{ab} = V_p \angle 0^\circ, \quad \hat{V}_{bc} = V_p \angle -120^\circ, \quad \hat{V}_{ca} = V_p \angle 120^\circ$$

the line current is related to the phase voltage by:
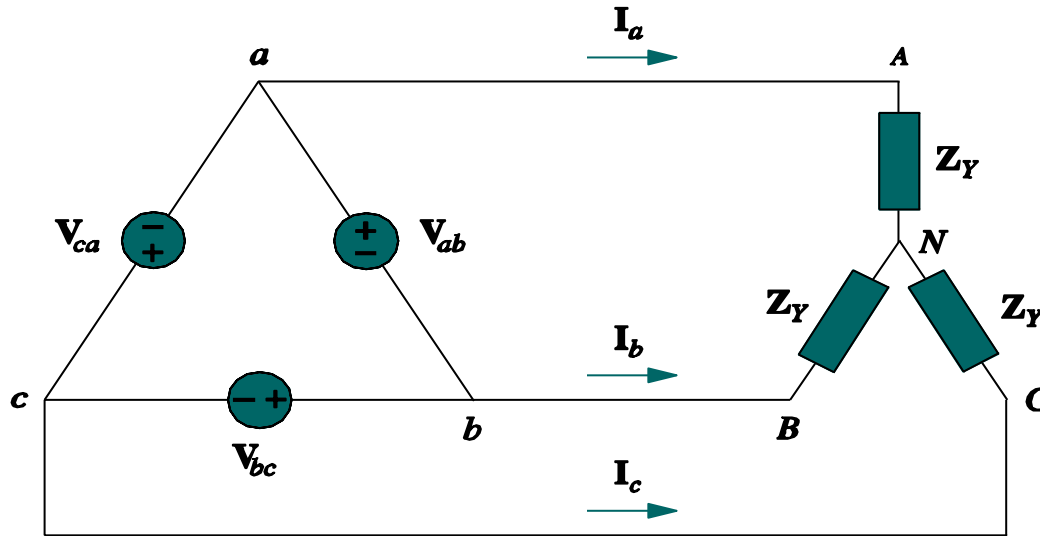
$$\hat{I}_a = \frac{V_{ab}}{\sqrt{3}Z_Y} \angle -30^\circ$$



Note the Δ -connected source can be converted to a Y-connected source through:

$$\hat{V}_{an} = \frac{\hat{V}_{ab}}{\sqrt{3}} \angle -30^\circ$$

Power in Balanced System

Show that the instantaneous power absorbed by a load in a balanced Y-Y system is a constant given by:

$$p(t) = 3V_p I_p \cos(\theta)$$

where the impedance in a single phase is given by:



$$\hat{Z}_Y = Z \angle \theta$$

The complex power per phase is


$$S = V_p I_p \exp(j\theta)$$

Note that average power or real power is the same as the instantaneous power for the 3-phase system.

Electrodynamic Wattmeter

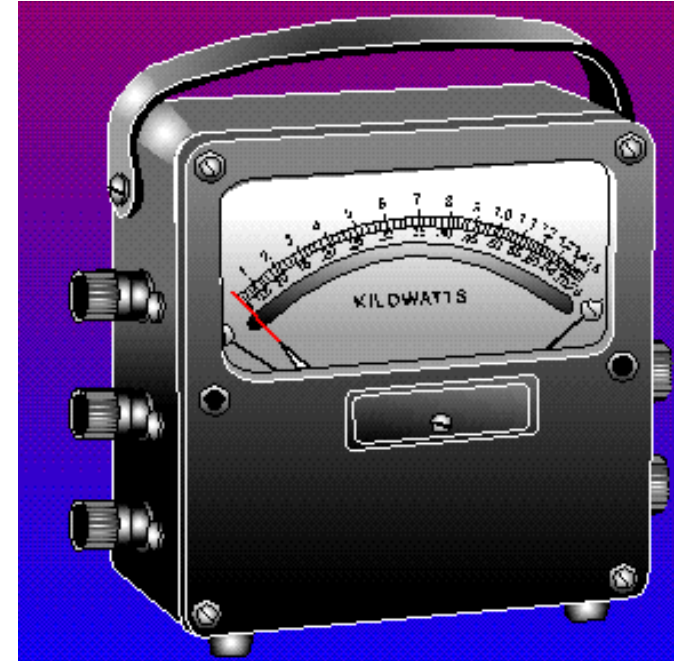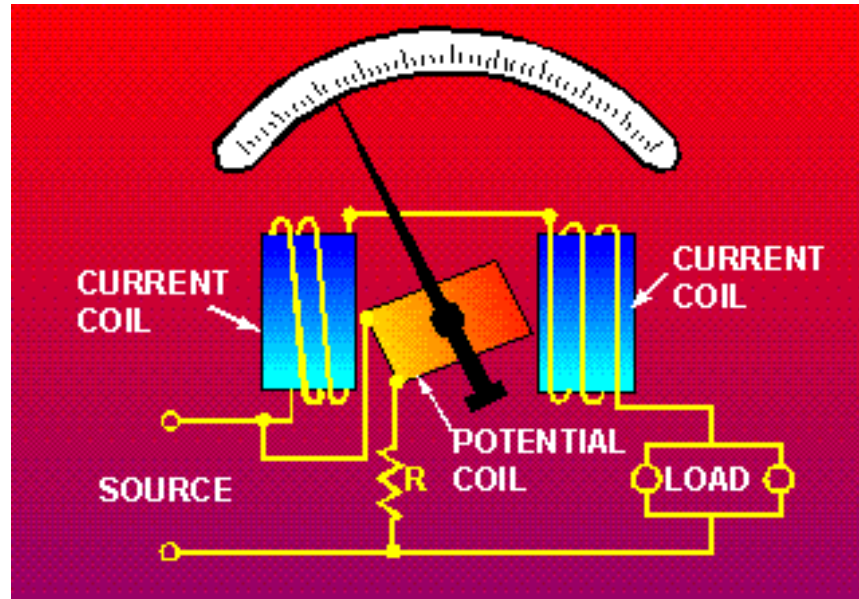

Two-Wattmeter Power Measurement

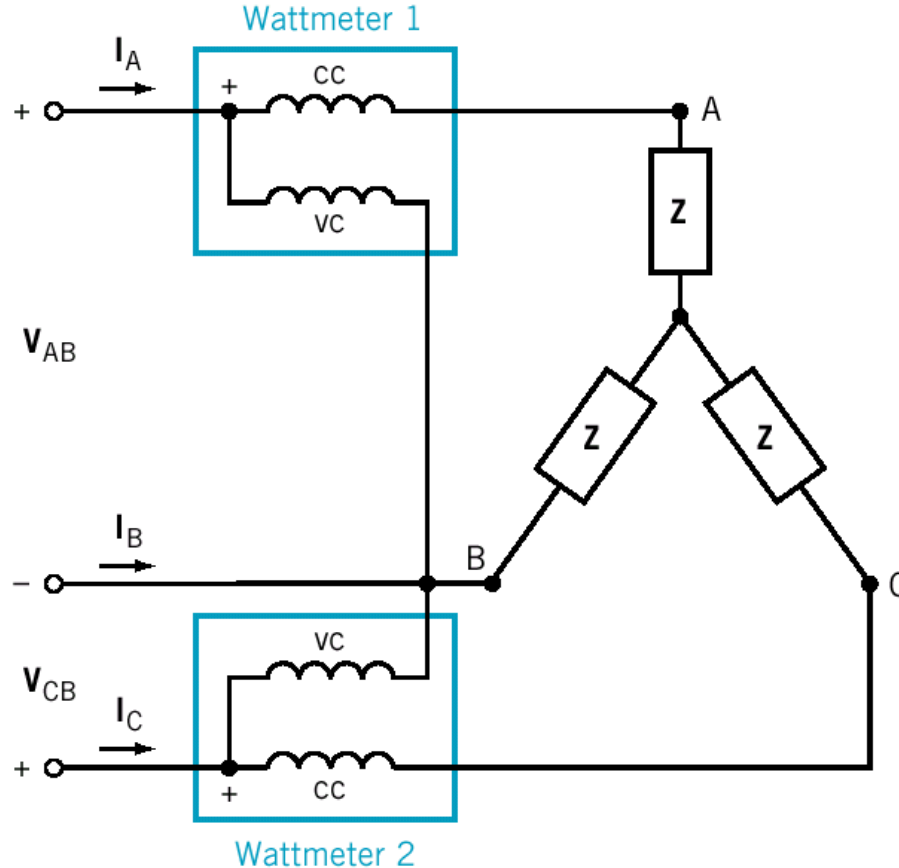

cc = current coil
vc = voltage coil

W1 read

$$P_1 = V_{AB} I_A \cos \theta_1$$

W2 read

$$P_2 = V_{CB} I_C \cos \theta_2$$

For balanced load with *abc* phase sequence

$$\theta_1 = \theta_a + 30^\circ \quad \text{and} \quad \theta_2 = \theta_a - 30^\circ$$

θ_a is the angle between phase current and phase voltage of phase *a*

Two-Wattmeter Power Measurement(cont.)

$$\begin{aligned}P &= P_1 + P_2 \\&= 2V_L I_L \cos \theta \cos 30^\circ \\&= \sqrt{3} V_L I_L \cos \theta\end{aligned}$$

To determine the power factor angle

$$\begin{aligned}P_1 + P_2 &= V_L I_L 2 \cos \theta \cos 30^\circ \\P_1 - P_2 &= V_L I_L (-2 \sin \theta \sin 30^\circ)\end{aligned}$$

$$\frac{P_1 + P_2}{P_1 - P_2} = \frac{V_L I_L 2 \cos \theta \cos 30^\circ}{V_L I_L (-2 \sin \theta \sin 30^\circ)} = \frac{-\sqrt{3}}{\tan \theta}$$

$$\therefore \tan \theta = \sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \quad \text{or} \quad \theta = \tan^{-1} \left(\sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \right)$$

Determine the three-phase power supplied to a delta connected circuit with an impedance of $4 + j6$ ohms in each phase, when a 3-phase, 415 V, 50 Hz is applied across it.

→ Line voltage

$$P = \sqrt{3} V_L I_L \cos \theta$$
$$= \sqrt{3} \times 415 \times 99.81 \times \cos(51.3^\circ) \approx 39.79 \text{ kW}$$

$$\text{Phase Current} = \frac{V}{Z} = \frac{415 \angle 0^\circ}{4 + j6} = \frac{415 \angle 0^\circ}{7.2 \angle 56.3^\circ} = 57.63 \angle -56.3^\circ \text{ (A)}$$

$$\text{Line Current} = I_L = \sqrt{3} I_{ph} = 99.81 \text{ (A)}$$

Example

Three identical coils, each having a resistance of 20Ω and an inductance of 0.5 H connected in (a) star and (b) delta to a three phase supply of 400 V ; 50 Hz . Calculate the current and the total power absorbed by both method of connections.

Exercise

Summary

3 ϕ balanced AC circuits

