

Unit - II

2.14 AC Steady-state Analysis

Dr.Santhosh.T.K.

Syllabus


UNIT – II

14 Periods

DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

AC Steady-state Analysis: AC waveform definitions - Form ~~factor~~ - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits


Instantaneous Electric Power [$p(t)$]

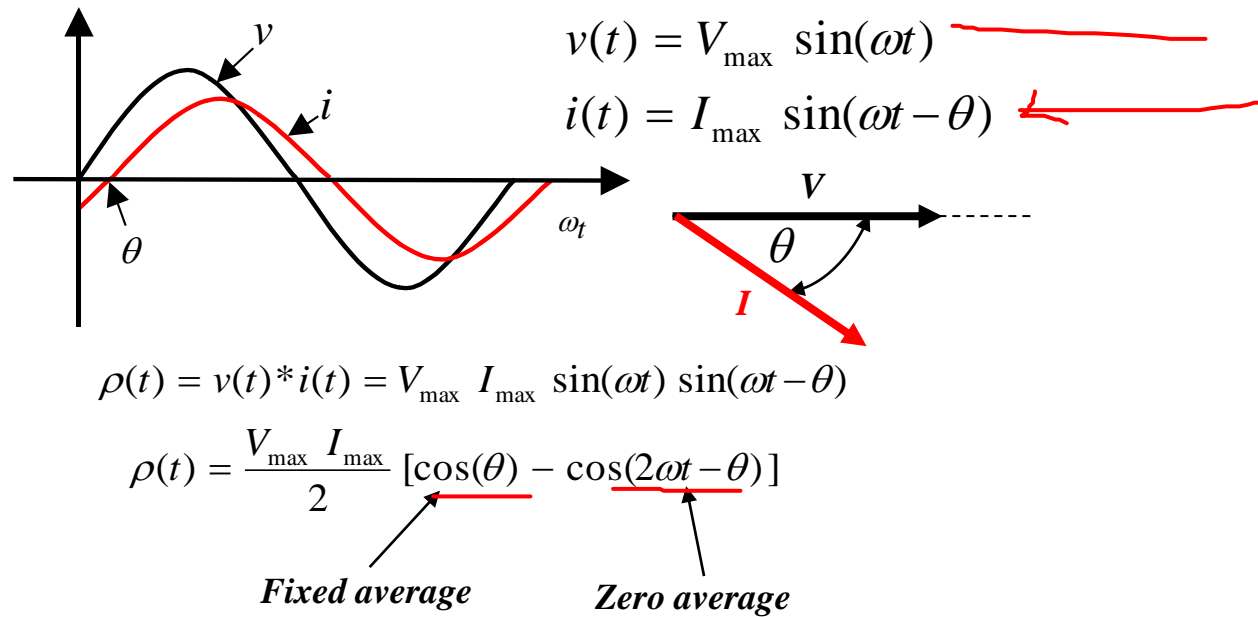


Real & Reactive Power – Time Domain

$$p(t) = \frac{V_{\max} I_{\max}}{2} [\cos(\theta_{vi}) - \cos(2\omega t - \theta_{vi})]$$

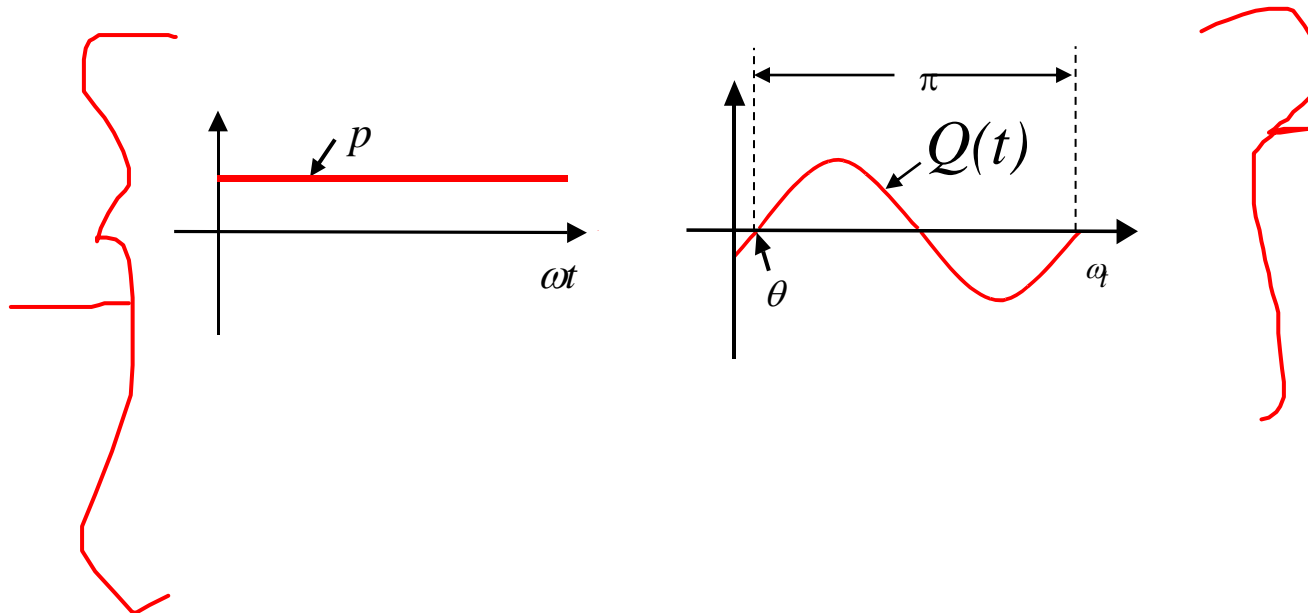
$$p(t) = \underline{P} + \underline{Q(t)}$$



Example: Current Flow

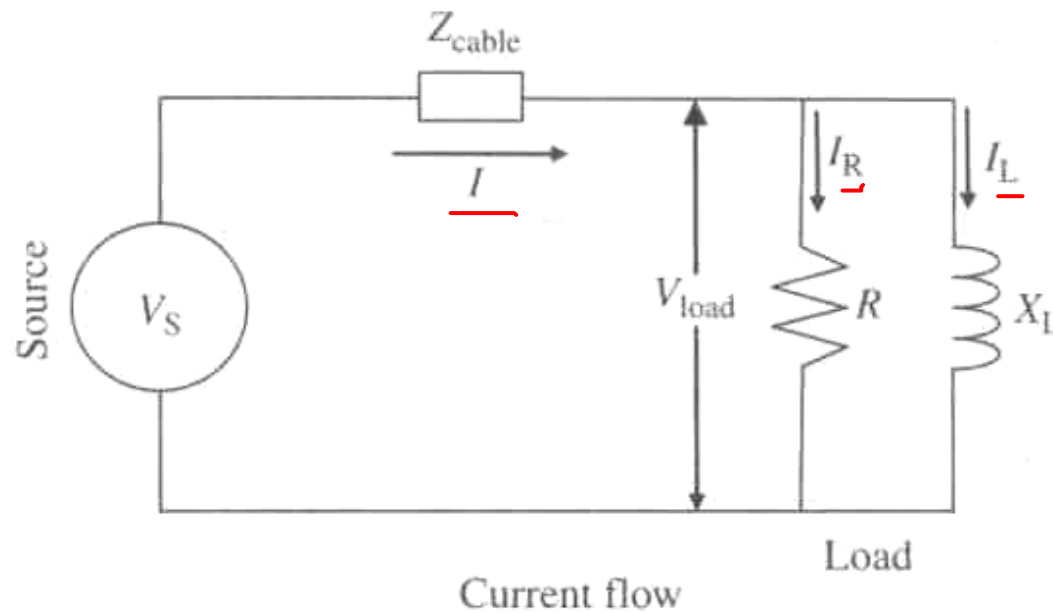

Example: Power Flow

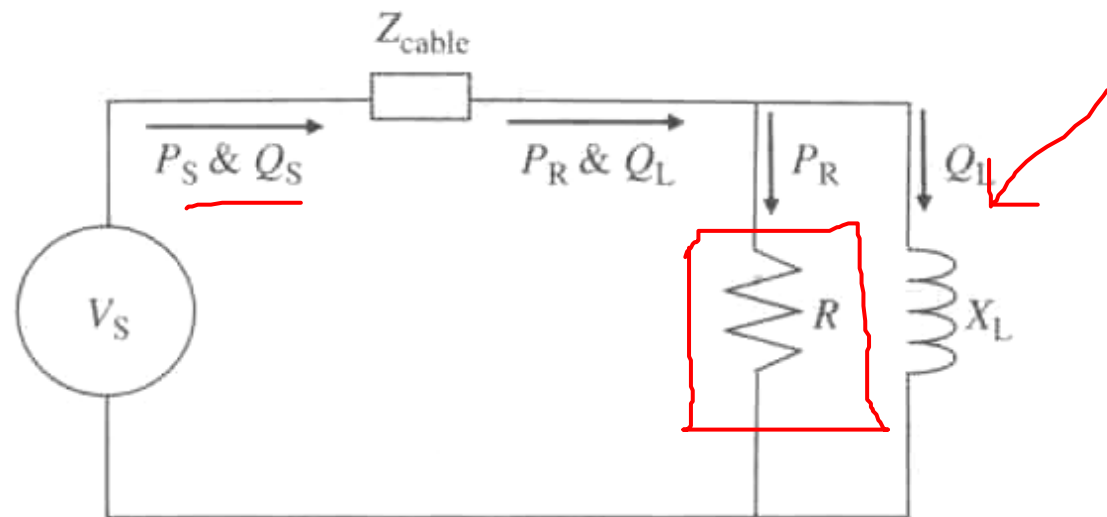

Power flow

Phasors

A sinusoidal voltage/current at a given frequency , is characterized by only two parameters :amplitude an phase

Key Words:


Complex Numbers

Rotating Vector

Phasors

Phasors

E.g. voltage response

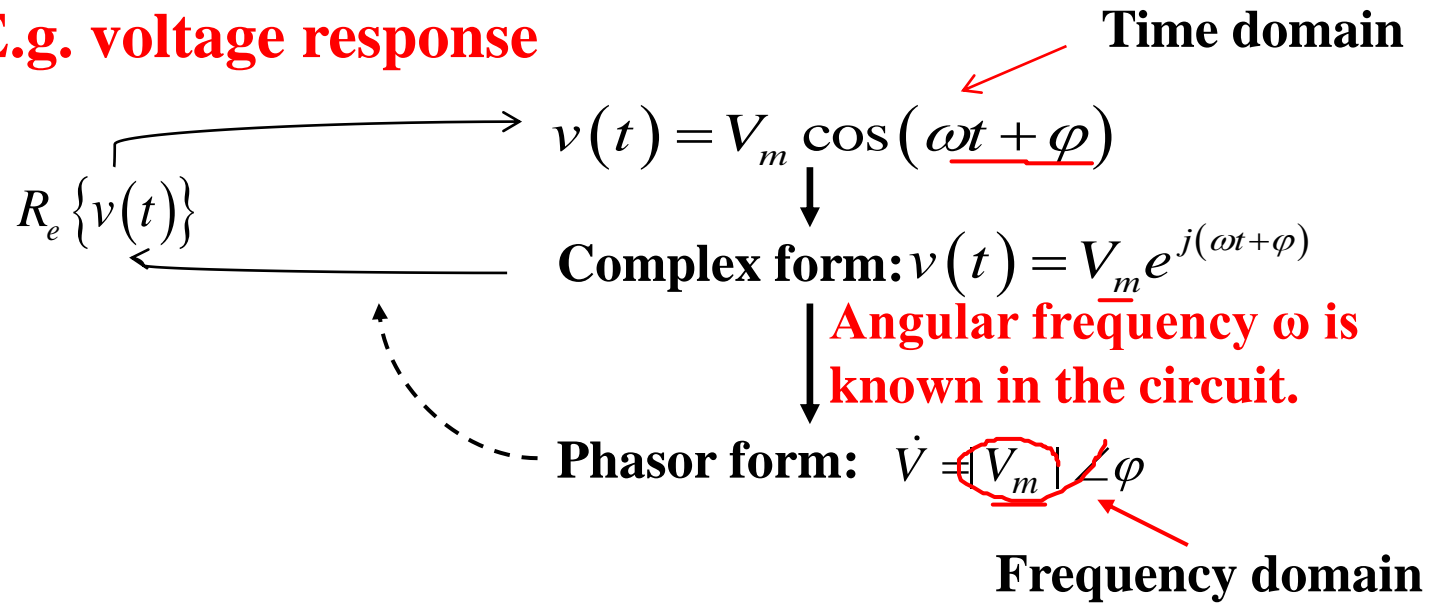

A sinusoidal v/i

$$v(t) = V_m \cos(\omega t + \varphi)$$

Complex transform

Phasor transform

$$\dot{V} = |\underline{V}_m| \angle \varphi$$


By knowing angular frequency ω rads/s.

Sinusoidal Steady State Analysis

Phasors

Rotating Vector
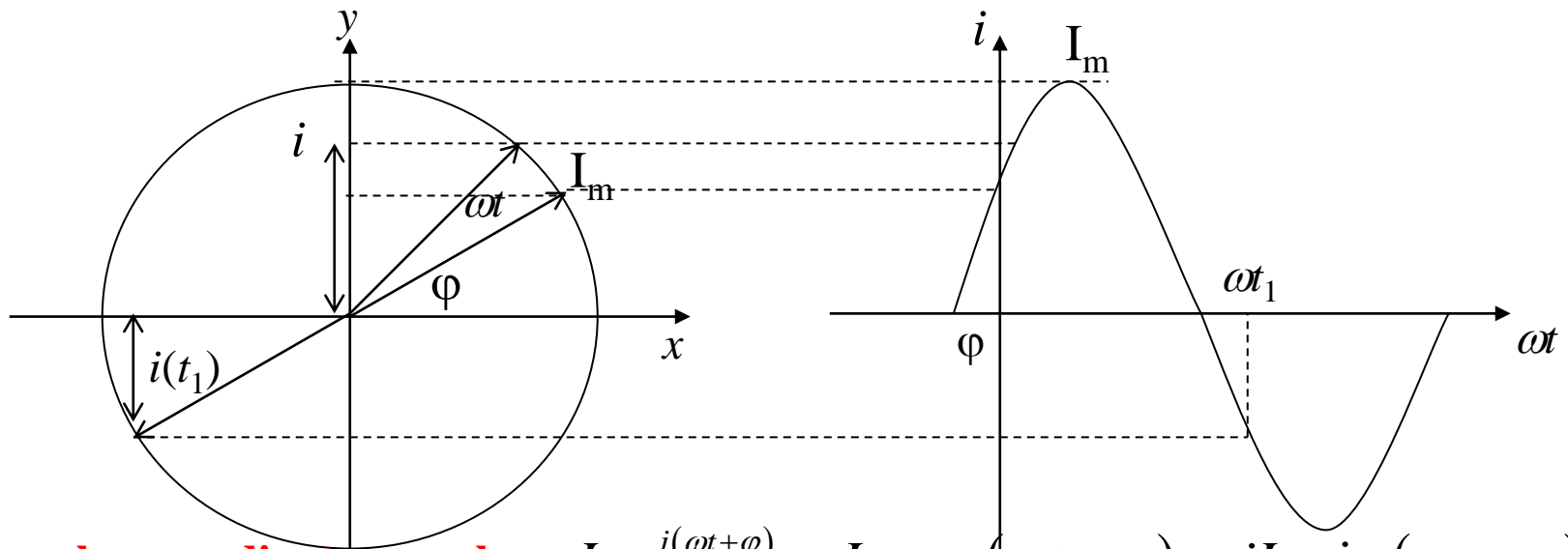
$$\underline{i(t)} = \underline{I_m \sin(\omega t + \varphi)}$$




A complex coordinates number: $\underline{I_m e^{j(\omega t + \varphi)}} = I_m \cos(\omega t + \varphi) + j I_m \sin(\omega t + \varphi)$

Real value: $i(t) = I_m \sin(\omega t + \varphi) = \text{Imag} \left(I_m e^{j(\omega t + \varphi)} \right)$

Sinusoidal Steady State Analysis

Phasors


Rotating Vector

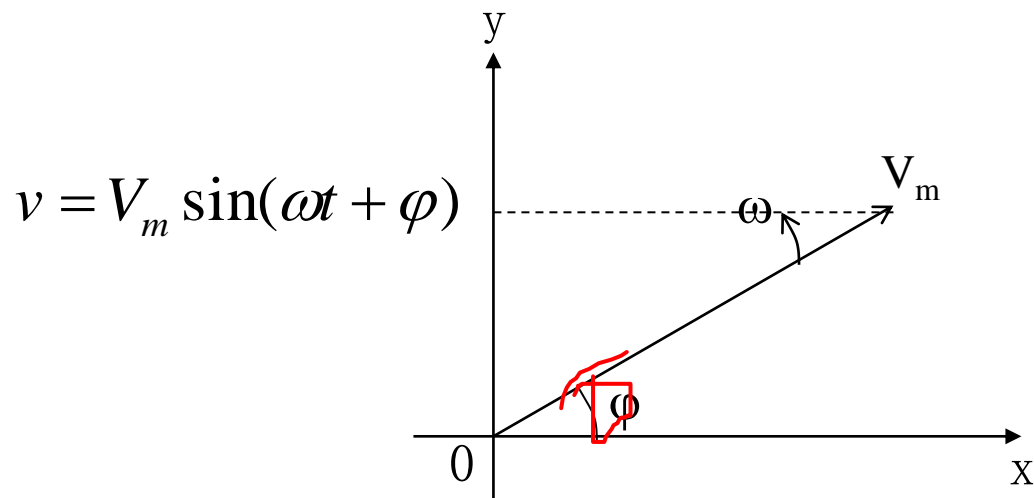

Sinusoidal Steady State Analysis

Phasors

Complex Numbers

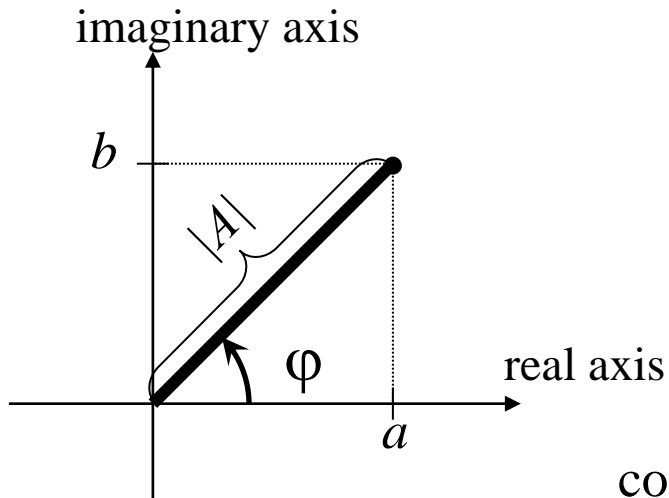

$A = \underline{a} + \underline{j}b$ — Rectangular Coordinates

$$A = |A|(\cos \varphi + j \sin \varphi)$$

$A = \underline{|A|} \underline{e^{j\varphi}}$ — Polar Coordinates

conversion:

$$A = a + jb \rightarrow A = |A|e^{j\varphi}$$

$$\begin{cases} |A| = \sqrt{a^2 + b^2} \\ \varphi = \text{arctg} \frac{b}{a} \end{cases}$$

$$e^{\pm j90^\circ} = \cos 90^\circ \pm j \sin 90^\circ = 0 \pm j = \pm j$$

$$|A|e^{j\varphi} \rightarrow a + jb \quad \begin{cases} a = |A| \cos \varphi \\ b = |A| \sin \varphi \end{cases}$$


Sinusoidal Steady State Analysis

Phasors

Complex Numbers

Arithmetic With Complex Numbers

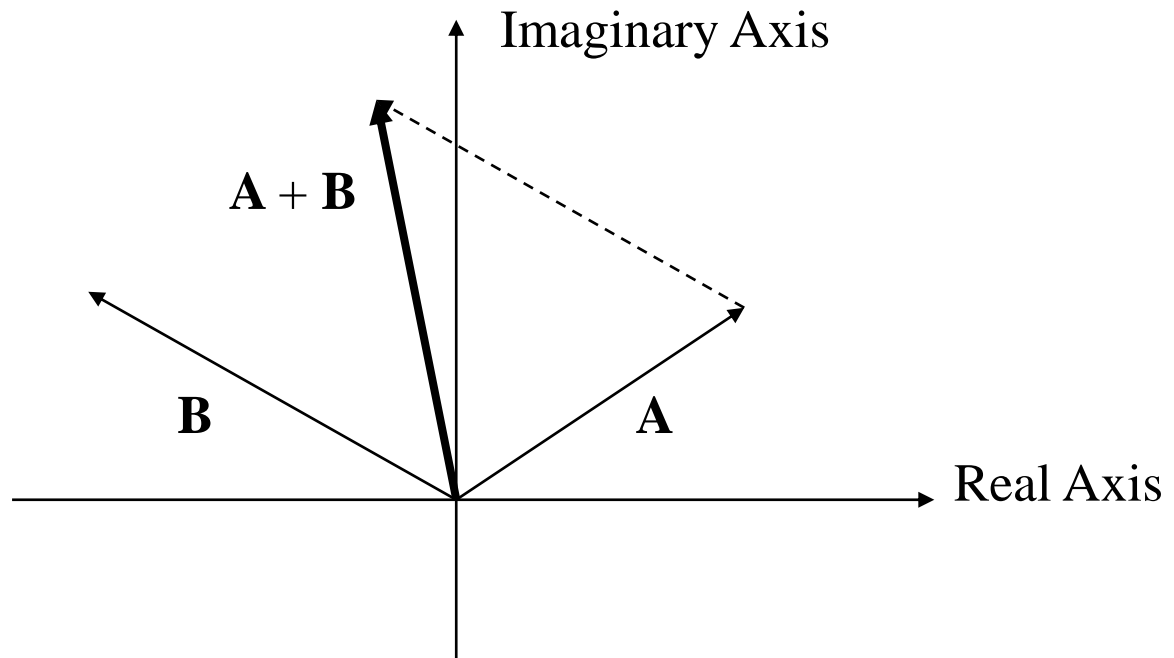Addition: $\underline{A = a + jb}$, $\underline{B = c + jd}$, $\underline{A + B = (a + c) + j(b + d)}$




Sinusoidal Steady State Analysis

Phasors

Complex Numbers

Arithmetic With Complex Numbers

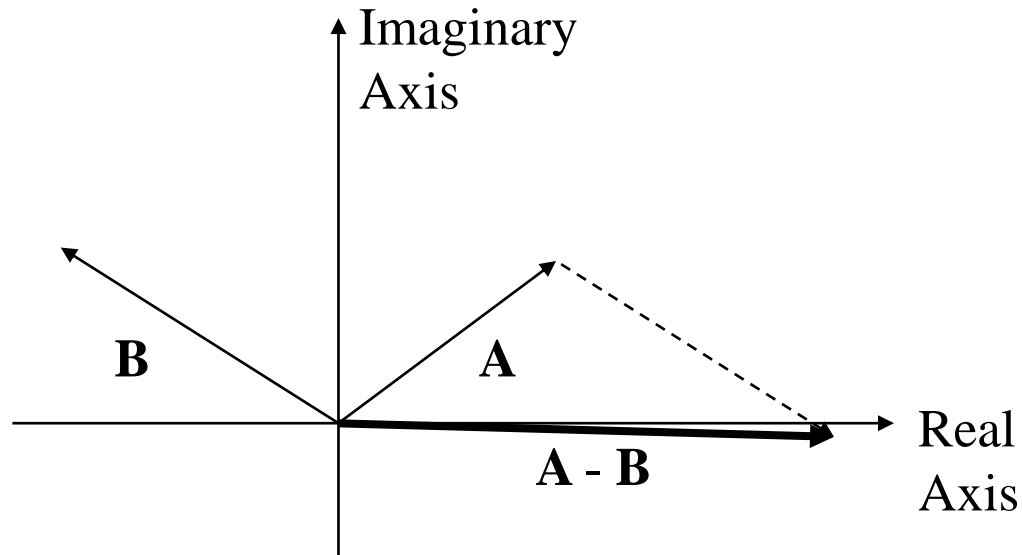Subtraction : $A = \underline{a + jb}$, $B = \underline{c + jd}$, $A - B = (\underline{a - c}) + j(\underline{b - d})$



Sinusoidal Steady State Analysis

Phasors

Complex Numbers

Arithmetic With Complex Numbers

Multiplication : $\mathbf{A} = \underline{A_m} \angle \varphi_A$, $\mathbf{B} = \underline{B_m} \angle \varphi_B$

$$\mathbf{A} \times \mathbf{B} = (\underline{A_m \times B_m}) \angle (\underline{\varphi_A + \varphi_B})$$

Division: $\mathbf{A} = A_m \angle \varphi_A$, $\mathbf{B} = B_m \angle \varphi_B$

$$\mathbf{A} / \mathbf{B} = (A_m / B_m) \angle (\underline{\varphi_A - \varphi_B})$$

Sinusoidal Steady State Analysis

Phasors

Phasors

A phasor is a complex number that represents the magnitude and phase of a sinusoid:

$$i_m \cos(\omega t + \varphi) \iff \dot{I} = I_m \angle \varphi$$

Phasor Diagrams

- A phasor diagram is just a graph of several phasors on the complex plane (using real and imaginary axes).
- A phasor diagram helps to visualize the relationships between currents and voltages.

Sinusoidal Steady State Analysis

Phasors

Complex Exponentials

$$A = |A|e^{j\varphi}$$

$$Ae^{j\omega t} = |A|e^{j(\omega t + \varphi)} = |A|\cos(\omega t + \varphi) + j|A|\sin(\omega t + \varphi)$$

$$\operatorname{Re}\{Ae^{j\omega t}\} = |A|\cos(\omega t + \varphi)$$

- A real-valued sinusoid is the real part of a complex exponential.
- Complex exponentials make solving for AC steady state an algebraic problem.

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Key Words:


I-V Relationship for R, L and C,

Power conversion

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

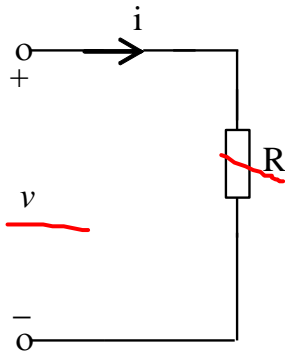
Resistor • $v \sim i$ relationship for a resistor



Suppose $\underline{v} = \underline{V_m} \sin \omega t$

$$\left\{ \underline{i} = \frac{\underline{v}}{\underline{R}} = \frac{\underline{V_m}}{\underline{R}} \sin \omega t = \underline{I_m} \sin \omega t \right.$$

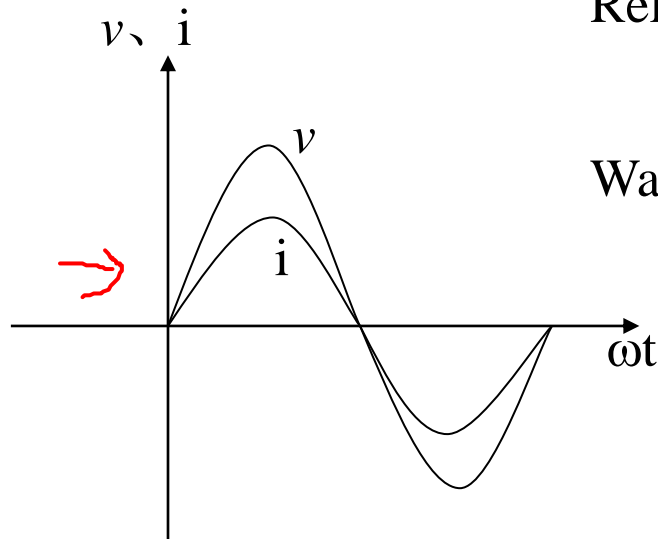Relationship between RMS: $I = \frac{V}{R}$



Wave and Phasor diagrams:

$$\begin{array}{c} \underline{I} \\ \underline{V} \\ I = \frac{V}{R} \end{array}$$

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Resistor • Time domain → frequency domain


$$\begin{array}{lcl} v(t) = V_m \cos(\omega t + \theta) & V(t) = Ri(t) & V_m e^{j(\omega t + \theta)} = RI_m e^{j(\omega t + \phi)} \\ i(t) = I_m \cos(\omega t + \phi) & \xrightarrow{\text{red arrow}} & V_m e^{j\theta} = RI_m e^{j\phi} \\ & & V_m \angle \theta = RI_m \angle \phi \\ & & \dot{V} = R\dot{I} \end{array}$$

With a resistor $\theta = \phi$, $v(t)$ and $i(t)$ are in phase .

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Resistor • Power

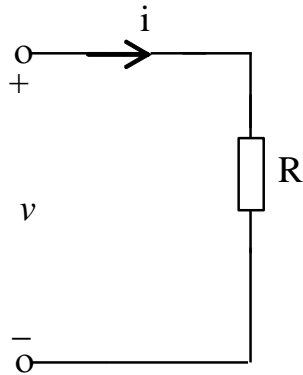

- Transient Power

$$\begin{aligned} \underline{p} &= \underline{v} \underline{i} = V_m \sin \omega t \cdot I_m \sin \omega t = I_m V_m \sin^2 \omega t \\ &= \frac{I_m V_m}{2} (1 - \cos 2\omega t) = IV - IV \cos 2\omega t \end{aligned}$$


Note: I and V are RMS values.

$p > 0$

- Average Power

$$P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T \underline{VI(1 - \cos 2\omega t)} dt = \underline{VI}$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

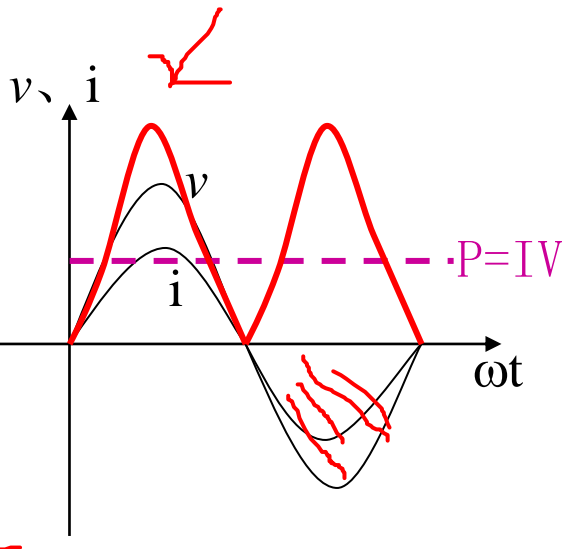

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Resistor

P4.4 , $v = \underline{311}\sin 314t$, $R=10\Omega$, Find \underline{i} and \underline{P} .

$$V = \frac{V_m}{\sqrt{2}} = \frac{311}{\sqrt{2}} = \underline{220}(V)$$


$$I = \frac{V}{R} = \frac{220}{10} = \underline{22}(A)$$

$$i = \underline{22\sqrt{2}} \sin 314t \quad P = IV = 220 \times 22 = 4840(W)$$

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Capacitor • $v \sim i$ relationship

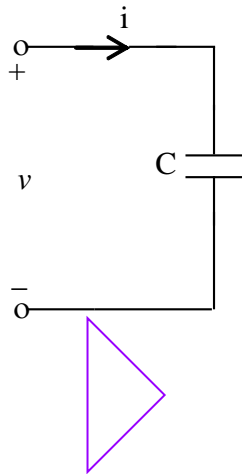

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

Suppose: $v = V_m \sin \omega t$

$$i = \omega C V_m \cos \omega t = \omega C V_m \sin(\omega t + 90^\circ) = I_m \sin(\omega t + 90^\circ)$$

$$I_m = \omega C V_m$$


Relationship between RMS $I = \omega C V = \frac{V}{1/\omega C} = \frac{V}{X_C}$

$$\longrightarrow X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} \quad (\Omega)$$

$$X_C \propto \frac{1}{f}$$

For DC, $f = 0$, $\rightarrow X_C \rightarrow \infty$

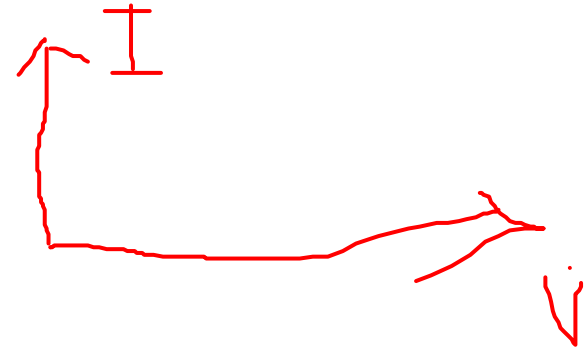$i(t)$ leads $v(t)$ by 90° , or $v(t)$ lags $i(t)$ by 90°




Ch4 Sinusoidal Steady State Analysis

4.3 Phasor Relationships for R, L and C

Capacitor • $v \sim i$ relationship

Wave and Phasor diagrams:

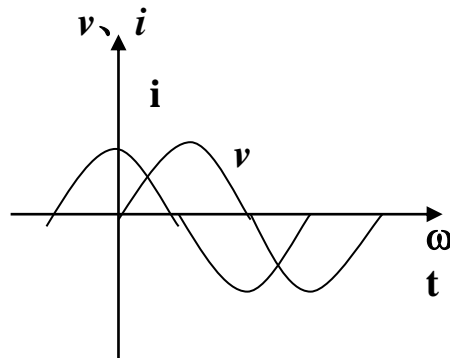

$$\dot{V} = -j\dot{I} X_C$$

A phasor diagram showing the relationship between current \dot{I} and voltage \dot{V} for a capacitor. The horizontal axis is labeled \dot{V} and the vertical axis is labeled \dot{I} . The current phasor \dot{I} is a vertical vector pointing upwards. The voltage phasor \dot{V} is a horizontal vector pointing to the right. The equation $\dot{V} = -j\dot{I} X_C$ is written above the diagram.

Ch4 Sinusoidal Steady State Analysis

4.3 Phasor Relationships for R, L and C

Capacitor • Power

$$p = vi = V_m \sin \omega t \cdot I_m \sin(\omega t + 90^\circ) = \frac{V_m I_m}{2} \sin 2\omega t = \underline{VI \sin 2\omega t}$$

Energy stored:


$$W = \int_0^t v i dt = \int_0^v v \cdot C \cdot \frac{dv}{dt} \cdot dt = \int_0^v C v dv = \frac{1}{2} C v^2$$

$$W_{\max} = \frac{1}{2} C V_m^2 = C V^2$$

Average Power:

$$\underline{P=0}$$
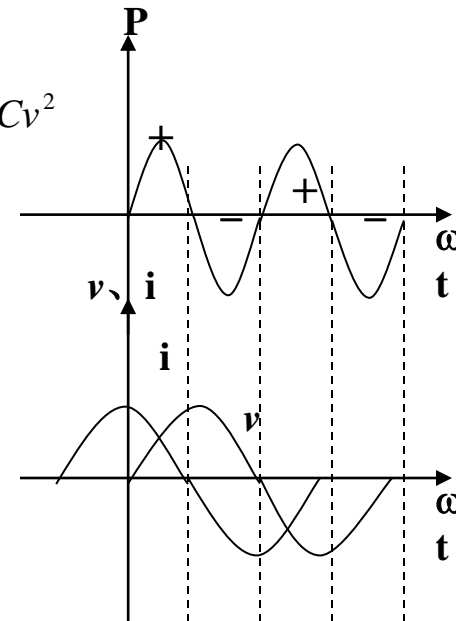
$$\text{Reactive Power } Q = IV = I^2 X_C = \frac{V^2}{X_C} \text{ (Var)}$$



Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Capacitor

P4.7, Suppose $C=20\mu\text{F}$, AC source $v=100\sin\omega t$, Find X_C and I for $f = 50\text{Hz}$, 50kHz .

$$f = 50\text{Hz} \rightarrow X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \underline{159\Omega}$$

$$I = \frac{V}{X_c} = \frac{V_m}{\sqrt{2}X_c} = \underline{0.4443 \text{ A}}$$


$$f = \underline{50\text{KHz}} \rightarrow X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C} = \underline{0.159(\Omega)}$$

$$I = \frac{V}{X_c} = \frac{V_m}{\sqrt{2}X_c} = \underline{444.29 \text{ A}}$$

Ch4 Sinusoidal Steady State Analysis

4.3 Phasor Relationships for R, L and C

Inductor • $v \sim i$ relationship

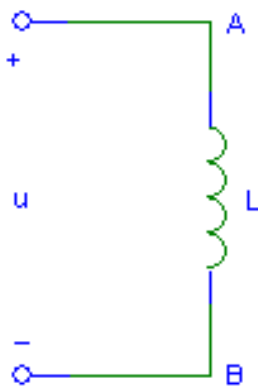

$$v = v_{AB} = L \frac{di}{dt}$$


$$\text{Suppose } i = I_m \sin \omega t$$

$$\begin{aligned} v &= L \frac{di}{dt} = L \frac{d(I_m \sin \omega t)}{dt} = \underline{I_m \omega L} \underline{\cos \omega t} \\ &= I_m \omega L \sin(\omega t + 90^\circ) \\ &= V_m \sin(\omega t + 90^\circ) \end{aligned}$$

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Inductor • $v \sim i$ relationship

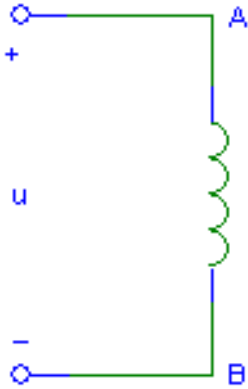

$$v = L \frac{di}{dt} = I_m \omega L \sin(\omega t + 90^\circ) = V_m \sin(\omega t + 90^\circ)$$

$$V_m = I_m \omega L$$

Relationship between RMS: $V = I \omega L$

$$I = \frac{V}{\omega L} \longrightarrow X_L = \omega L = 2\pi f L \quad (\Omega)$$

$$\longrightarrow X_L \propto f$$

For DC, $f = 0$, $\rightarrow X_L = 0$.


\longrightarrow $v(t)$ leads $i(t)$ by 90° , or $i(t)$ lags $v(t)$ by 90°

Ch4 Sinusoidal Steady State Analysis


4.3 Phasor Relationships for R, L and C

Inductor ● $v \sim i$ relationship

Wave and Phasor diagrams:

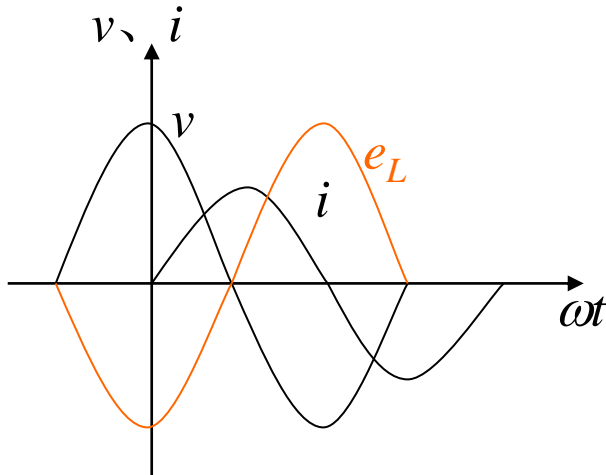

$$\dot{V} = jIX_L$$

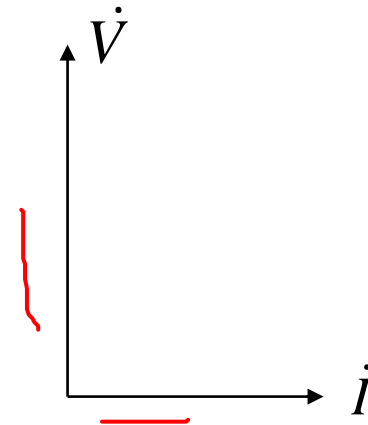

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Inductor • Power


$$p = vi = V_m \sin(\omega t + 90^\circ) I_m \sin \omega t = V_m I_m \cos \omega t \cdot \sin \omega t$$
$$\rightarrow = \frac{V_m I_m}{2} \sin 2\omega t = VI \sin 2\omega t$$

$$\text{Energy stored: } W = \int_0^t v i dt = \int_0^i L i di = \frac{1}{2} L i^2$$

$$W_{\max} = \frac{1}{2} L I_m^2 = LI^2$$

$$\text{Average Power } P = \frac{1}{T} \int_0^T p dt = \frac{1}{T} \int_0^T VI \sin 2\omega t dt = 0$$
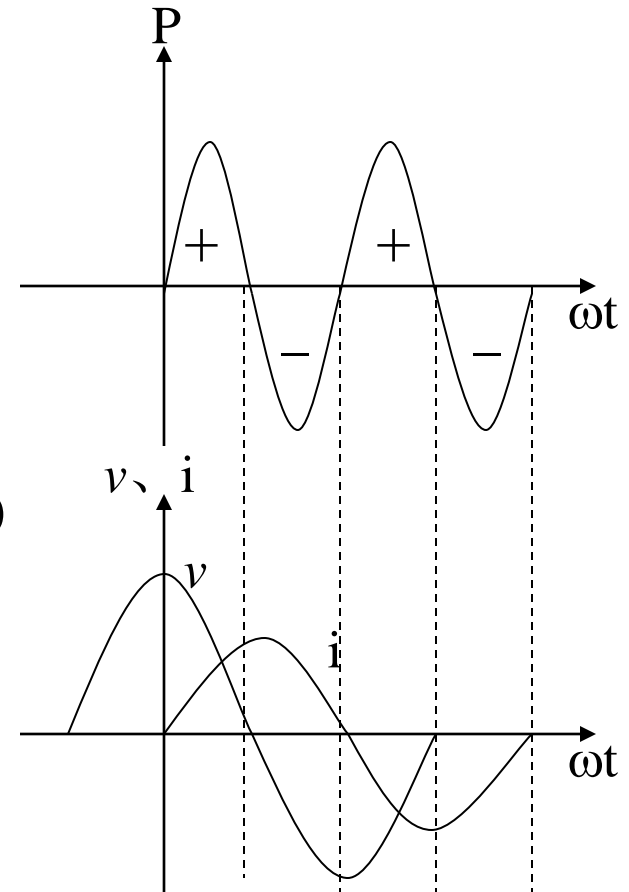
$$\text{Reactive Power } Q = IV = I^2 X_L = \frac{V^2}{X_L} \quad (\text{Var})$$



Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Inductor

P4.5, $L = 10\text{mH}$, $v = 100\sin\omega t$, Find i_L when $f = 50\text{Hz}$ and 50kHz .

$$X_L = 2\pi fL = 2\pi \times 50 \times 10 \times 10^{-3} = 3.14(\Omega)$$

$$I_{50} = \frac{V}{X_L} = \frac{100/\sqrt{2}}{3.14} = 22.5(\text{A})$$

$$i_L(t) = 22.5\sqrt{2} \sin(\omega t - 90^\circ) \text{A}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 10^3 \times 10 \times 10^{-3} = 3140(\Omega)$$

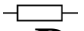
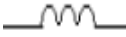

$$I_{50k} = \frac{V}{X_L} = \frac{100/\sqrt{2}}{3.14} = 22.5(\text{mA})$$

$$i_L(t) = 22.5\sqrt{2} \sin(\omega t - 90^\circ) \text{mA}$$

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Review (*v-i relationship*)

	Time domain	Frequency domain
 R	$v = R \cdot i$	$\dot{V} = R \cdot \dot{I}$, v and i are in phase.
 L	$v_L = L \frac{di}{dt}$	$\dot{V} = j\omega L \cdot \dot{I}$, $X_L = \omega L$, v leads i by 90° .
 C	$v_C = C \frac{dv}{dt}$	$\dot{V} = \frac{1}{j\omega C} \cdot \dot{I}$, $X_C = \frac{1}{\omega C}$, v lags i by 90° .

Sinusoidal Steady State Analysis

Phasor Relationships for R, L and C

Summary

- **R:** $X_R = R$ $\Delta\varphi = 0$
- L:** $X_L = \omega L = 2\pi f L \propto f$ $\Delta\varphi = \varphi_v - \varphi_i = \underline{\frac{\pi}{2}}$
- C:** $X_C = \frac{1}{\omega c} = \frac{1}{2\pi f c} \propto \frac{1}{f}$ $\Delta\varphi = \varphi_v - \varphi_i = \underline{-\frac{\pi}{2}}$
- $V = IX$

- **Frequency characteristics of an Ideal Inductor and Capacitor:**

A capacitor is an *open circuit* to DC currents;

A Inducter is a *short circuit* to DC currents.

Sinusoidal Steady State Analysis

Impedance

Complex voltage, Complex current, Complex Impedance

- AC steady-state analysis using phasors allows us to express the relationship between current and voltage using a formula that looks like Ohm's law:

$$\longrightarrow \dot{V} = \dot{I}Z$$

**Z is called
impedance.**

$$\dot{V} = V_m e^{j\varphi_v} = V_m \angle \varphi_v \quad \text{measured in ohms} \\ (\Omega)$$

$$\dot{I} = I_m e^{j\varphi_i} = I_m \angle \varphi_i$$

$$Z = \frac{\dot{V}}{\dot{I}} = \frac{V_m}{I_m} e^{j(\varphi_v - \varphi_i)} = |Z| e^{j\varphi} = |Z| \angle \varphi$$

Sinusoidal Steady State Analysis

Impedance

Complex Impedance

$$Z = \frac{\dot{V}}{\dot{I}} = \frac{V_m}{I_m} e^{j(\varphi_v - \varphi_i)} = |Z| e^{j\varphi} = |Z| \underline{\angle \varphi}$$

- Complex impedance describes the relationship between the voltage across an element (expressed as a phasor) and the current through the element (expressed as a phasor)
- Impedance is a complex number and is **not** a phasor (why?).
- Impedance depends on frequency

Sinusoidal Steady State Analysis

Impedance

Complex Impedance

Resistor—The impedance is R

$$Z_R = R \quad \Delta\phi = 0; \text{ or } Z_R = R \angle 0$$

Capacitor—The impedance is $1/j\omega C$

$$Z_c = \frac{1}{\omega C} e^{-j\frac{\pi}{2}} = \frac{-j}{\omega C} = -jX_c \quad \bullet \quad Z_c = \frac{1}{\omega C} \angle -90^\circ$$

r

$$(\Delta\phi = \phi_v - \phi_i = -\frac{\pi}{2})$$

Inductor—The impedance is $j\omega L$

$$Z_L = \omega L e^{j\frac{\pi}{2}} = j\omega L = jX_L \quad \bullet \quad Z_L = \omega L \angle 90^\circ$$

r


$$(\Delta\phi = \phi_v - \phi_i = \frac{\pi}{2})$$

Sinusoidal Steady State Analysis


Impedance

Complex Impedance

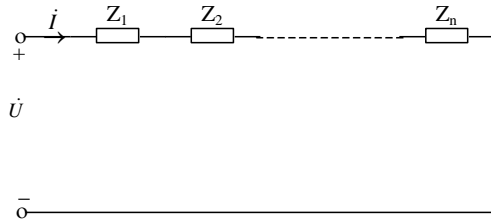Impedance in series/parallel can be combined as resistors.


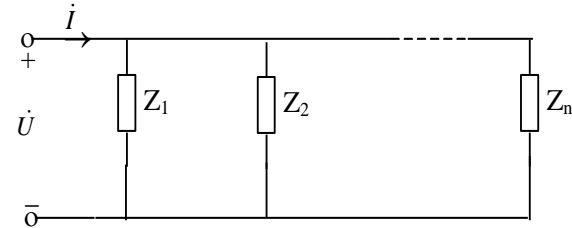
$$Z = Z_1 + Z_2 + \dots + Z_n = \sum_{k=1}^n Z_k$$



$$\frac{1}{Z} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n} = \sum_{k=1}^n \frac{1}{Z_k}$$

Voltage divider:

$$\dot{V}_i = \dot{V} \frac{Z_i}{\sum_{k=1}^n Z_k}$$

Current divider:


$$\dot{I}_1 = \dot{I} \frac{Z_2}{Z_1 + Z_2} \quad \dot{I}_2 = \dot{I} \frac{Z_1}{Z_1 + Z_2}$$

Practice Problem

Impedance

Complex Impedance

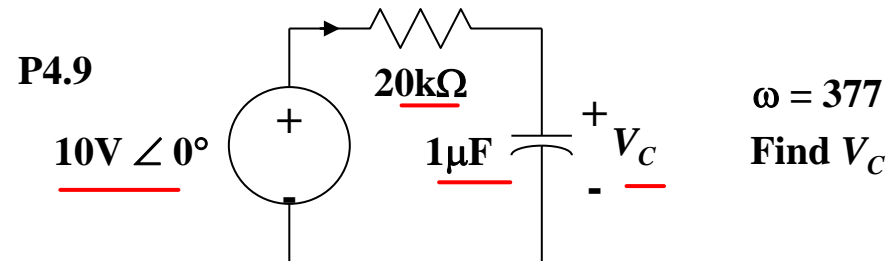Phasors and complex impedance allow us to use Ohm's law with complex numbers to compute current from voltage and voltage from current



Summary

- Steady-state analysis
- R,L,C