

Unit - II

2.10 DC Transient Analysis – RC Circuit

Dr.Santhosh.T.K.

Syllabus

UNIT – II


14 Periods

DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

AC Steady-state Analysis: AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits

NATURAL RESPONSE OF AN RC CIRCUIT

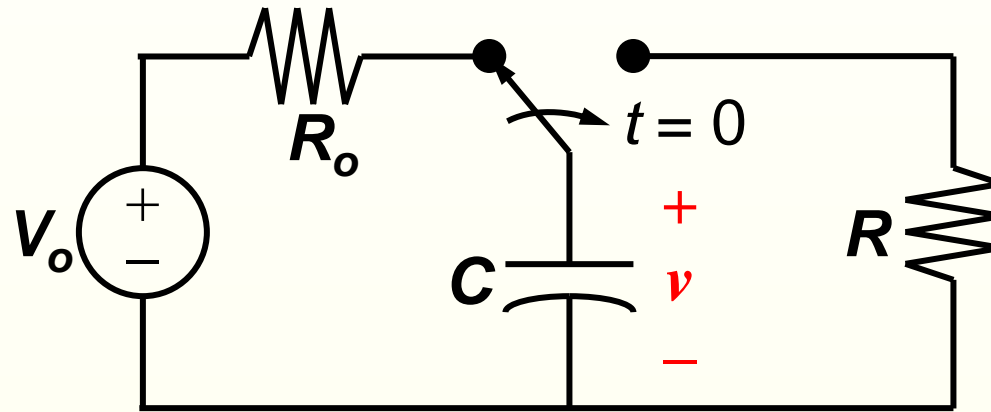- Consider the following circuit, for which the switch is closed for $t < 0$, and then opened at $t = 0$:




Notation:

- 0^- is used to denote the time just prior to switching
- 0^+ is used to denote the time immediately after switching.

Solving for the voltage ($t \geq 0$)

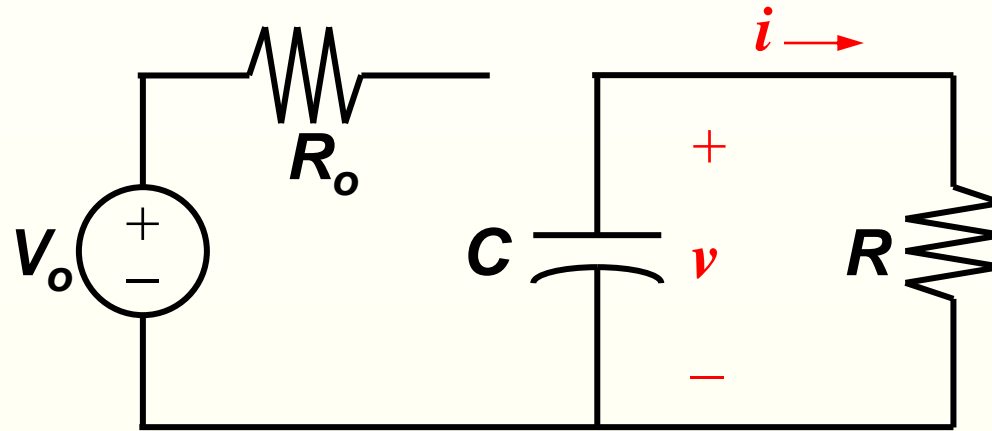- For $t \leq 0$, $v(t) = V_o$
- For $t > 0$, the circuit reduces to



Continue

- Applying KCL to the RC circuit:

$$i_C + i_R = 0 \longrightarrow (1)$$

$$C \frac{dv(t)}{dt} + \frac{v(t)}{R} = 0 \longrightarrow (2)$$

$$\frac{dv(t)}{dt} + \frac{v(t)}{RC} = 0 \longrightarrow (3)$$

$$\frac{dv(t)}{dt} = -\frac{v(t)}{RC} \longrightarrow (4)$$

$$\frac{dv(t)}{v(t)} = -\frac{1}{RC} dt \longrightarrow (5)$$

Continue

- From equation (5), let say:

$$\frac{dx}{x} = -\frac{1}{RC} dy \longrightarrow (6)$$

- Integrate both sides of equation (6):

$$\int_{V_o}^{v(t)} \frac{1}{x} du = -\frac{1}{RC} \int_0^t dy \longrightarrow (7)$$

- Therefore:

$$\ln \frac{v(t)}{V_o} = -\frac{t}{RC} \longrightarrow (8)$$

Continue

- Hence, the voltage is:

$$v(t) = v(0)e^{-t/RC} = V_o e^{-t/RC}$$

- Using Ohm's law, the current is:

$$i(t) = \frac{v(t)}{R} = \frac{V_o}{R} e^{-t/RC}$$

Continue

- The power dissipated in the resistor is:

$$p(t) = vi_R = \frac{V_o^2}{R} e^{-2t/RC}$$

- The energy absorb by the resistor is:

$$w = \frac{1}{2} CV_o^2 (1 - e^{-2t/RC})$$

Continue

- The time constant for the RC circuit equal the product of the resistance and capacitance,

- Time constant, $\tau = RC$ sec

- The expressions for voltage, current, power and energy using time constant concept:

$$v(t) = V_o e^{-t/\tau}$$

$$i(t) = \frac{V_o}{R} e^{-t/\tau}$$

$$p(t) = \frac{V_o^2}{R} e^{-2t/\tau}$$

$$w(t) = \frac{1}{2} C V_o^2 (1 - e^{-2t/\tau})$$

- For the case of capacitor, two important observation can be made,

1) capacitor behaves like an open circuit when being supplied by dc source


(From, $i_c = Cdv/dt$, when v is constant, $dv/dt = 0$.

When current in circuit is zero, the circuit is open circuit.)

2) in capacitor, the voltage is continuous / stays the same that is, $V_c(0^+) = V_c(0^-)$

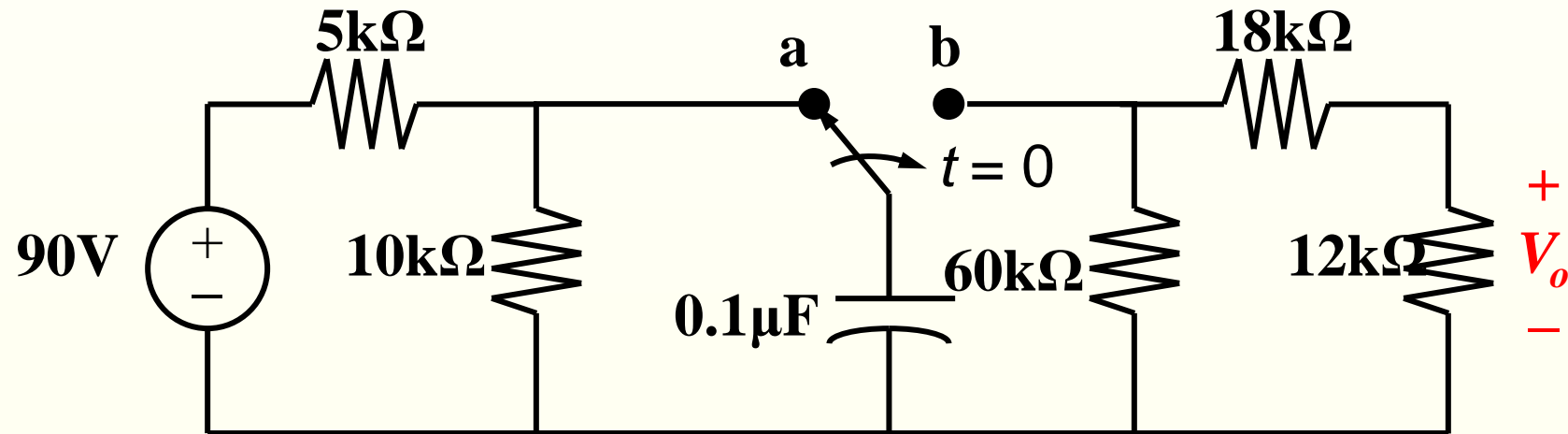
Example

The switch has been in position *a* for a long time. At Time $t = 0$, the switch moves to *b*. Find the expressions for the $v_c(t)$, $i_c(t)$ and $v_o(t)$ and hence sketch them for $t = 0$ to $t = 5\tau$.



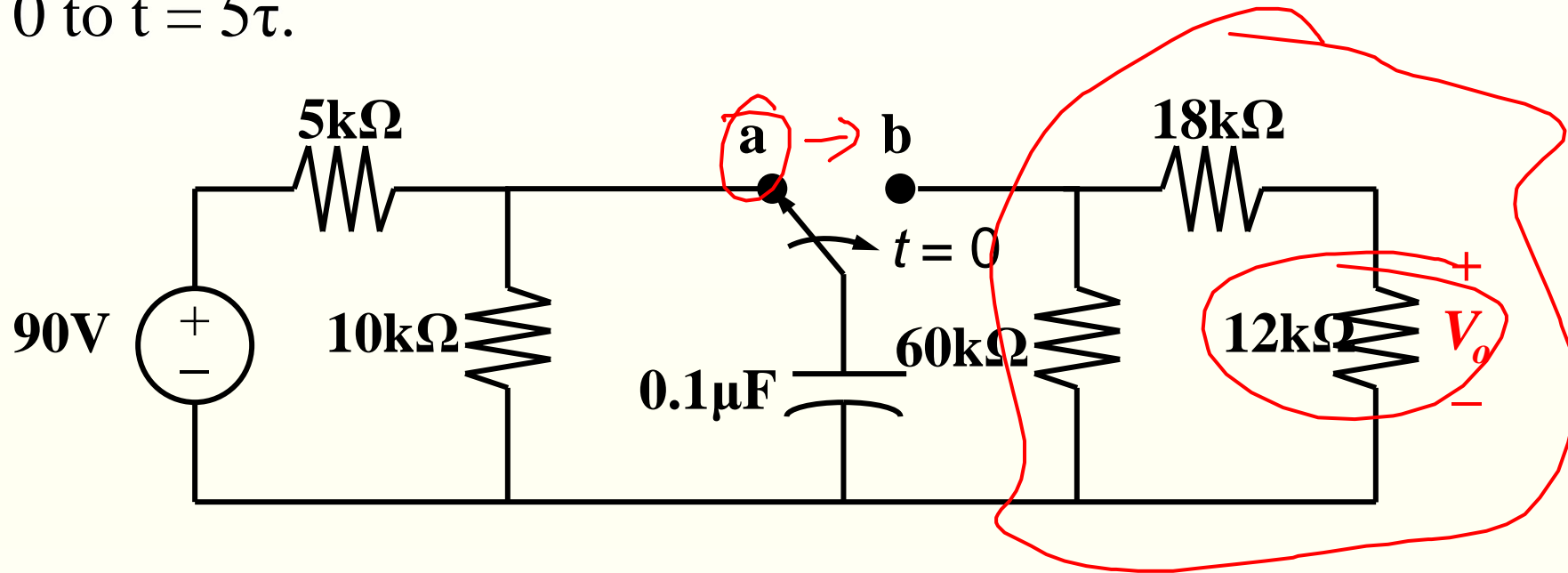Example


The switch has been in position *a* for a long time. At Time $t = 0$, the switch moves to *b*. Find the expressions for the $v_c(t)$, $i_c(t)$ and $v_o(t)$ and hence sketch them for $t = 0$ to $t = 5\tau$.



Solution

Step 1:

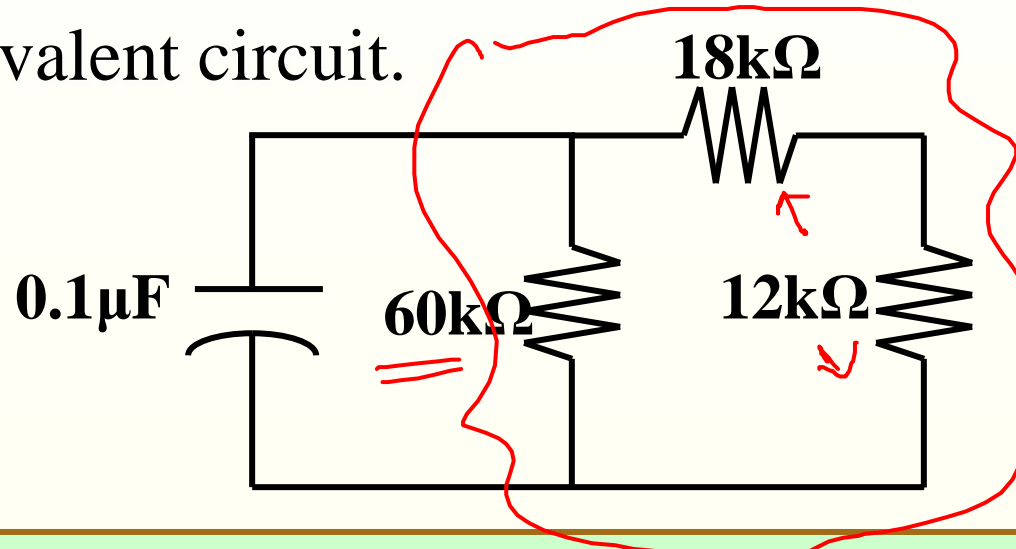Find t for $t > 5\tau$ that is when the switch was at a . Draw the equivalent circuit.




$$R_T = (18\text{k}\Omega + 12\text{k}\Omega) // 60\text{k}\Omega = 20\text{k}\Omega$$

$$\tau = R_T C = 20 \times 10^3 \times 0.1 \times 10^{-6} = 2\text{ms}$$

Step 2:

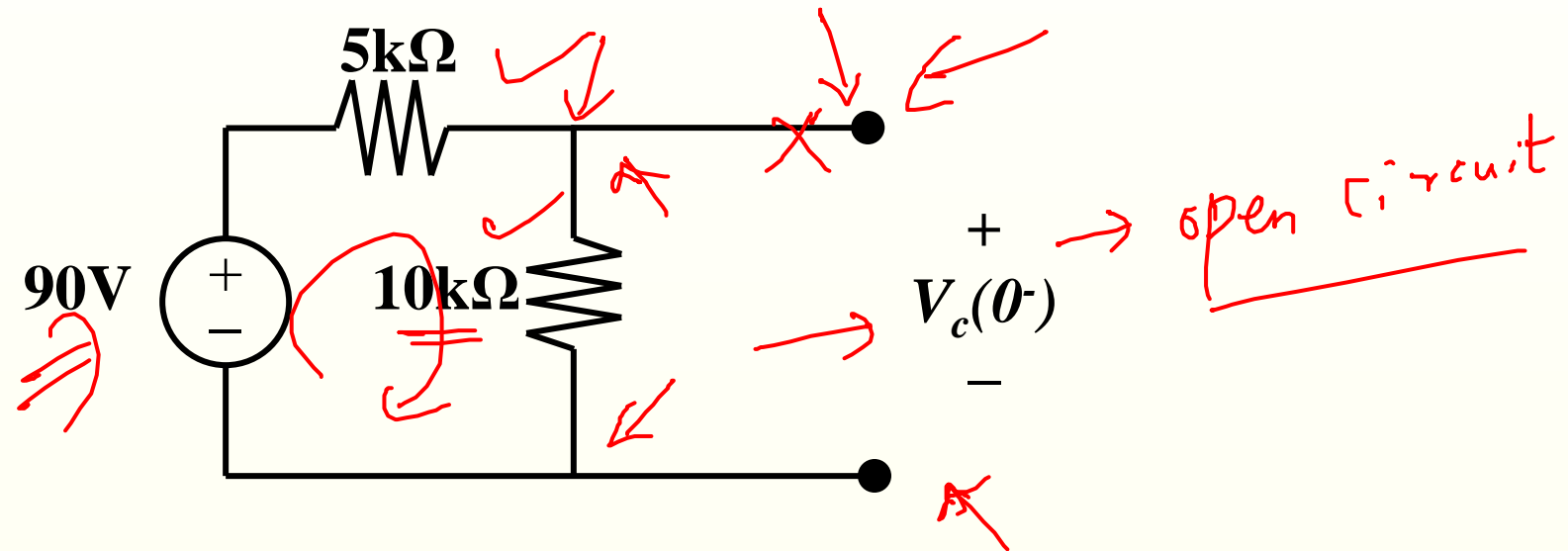
At $t = 0$, the switch was at a . the capacitor behaves like
An open circuit as it is being supplied by a constant
source.



$$v_c(0^-) = \frac{10}{15} \times 90 = 60V$$

Step 3:

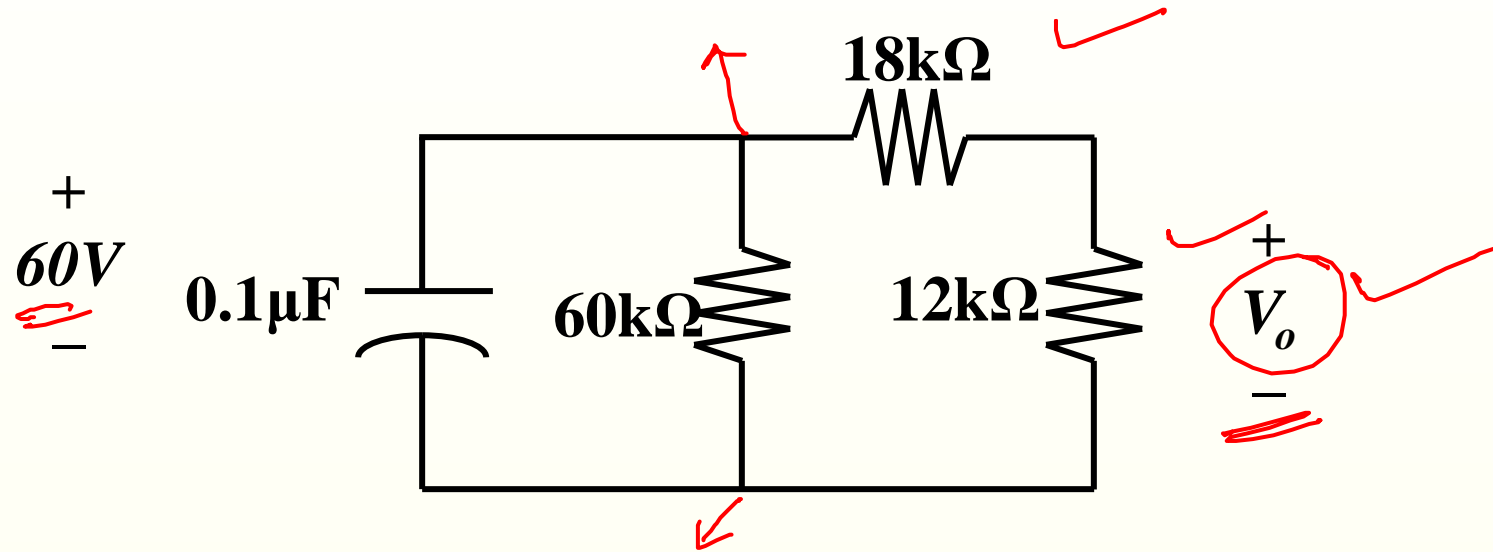At $t = 0^+$, the instant when the switch is at b .



The voltage across capacitor remains the same at this particular instant.

$$v_c(0^+) = v_c(0^-) = 60V$$

Using voltage divider rule,

$$V_o(0^+) = \frac{12}{30} \times 60 = 24V$$

Hence;

$$v_c(t) = 60e^{-500t} V$$

$$v_o(t) = 24e^{-500t} V$$

$$i_c(t) = -0.03e^{-500t} A$$

Comparison of RL & RC Circuit

No	RL circuit	RC circuit
1	$\tau = \frac{L}{R}$	$\tau = RC$
2	Inductor behaves like a short circuit when being supplied by dc source for a long time	Capacitor behaves like an open circuit when being supplied by dc source for a long time
3	Inductor current is continuous $i_L(0^+) = i_L(0^-)$	Voltage across capacitor is continuous $v_C(0^+) = v_C(0^-)$

Summary




Transient

→ why?
→ How?

→ Response

Exercise

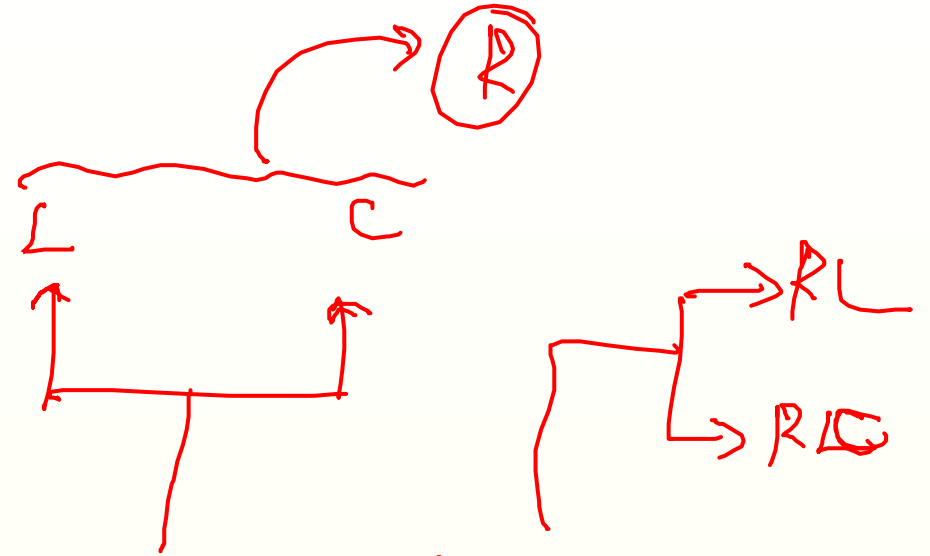

Natural response

Forced response

→ Source