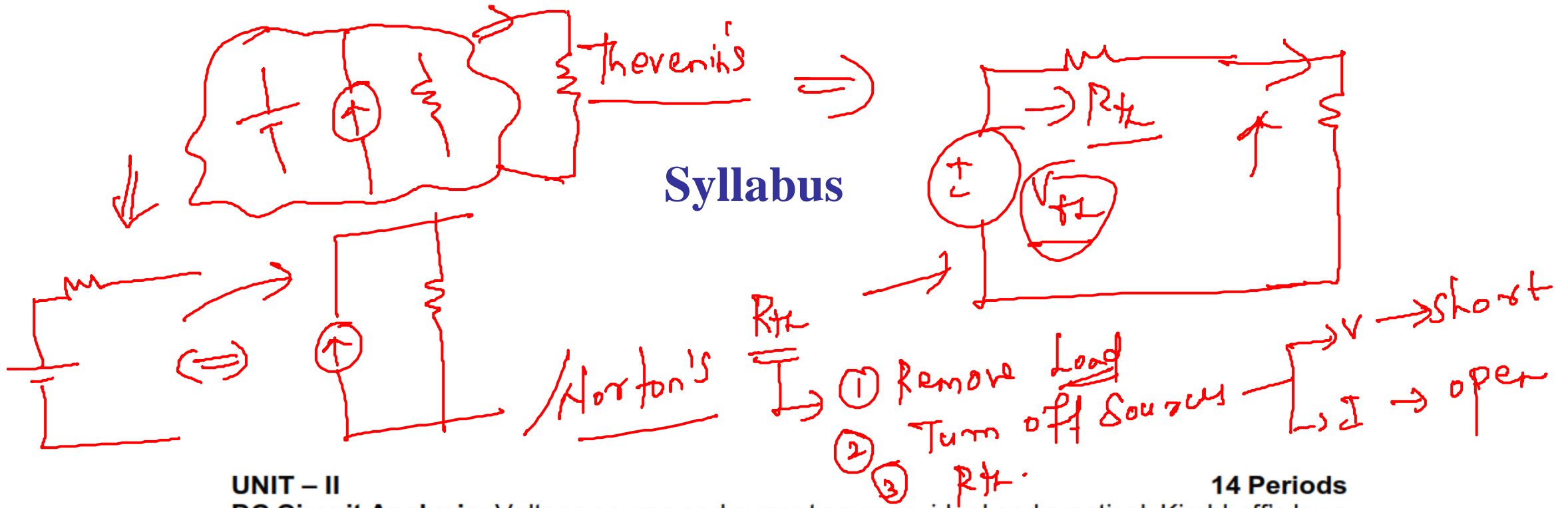


Unit - II

2.8 Norton's theorem and Maximum Power Transfer Theorem

Dr.Santhosh.T.K.

Syllabus




UNIT – II


DC Circuit Analysis: Voltage source and current sources, ideal and practical, Kirchhoff's laws and applications to network solutions using mesh analysis, - Simplifications of networks using series- parallel, Star/Delta transformation, DC circuits-Current-voltage relations of electric network by mathematical equations to analyse the network (Superposition theorem, Thevenin's theorem, Maximum Power Transfer theorem), Transient analysis of R-L, R-C and R-L-C Circuits.

14 Periods


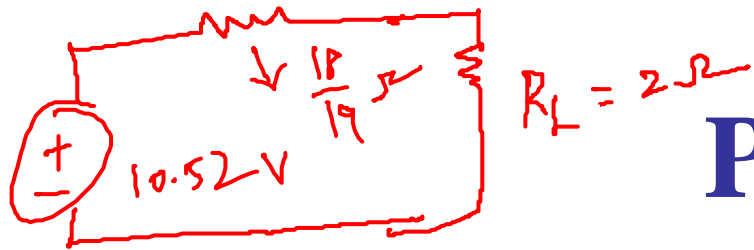
AC Steady-state Analysis: AC waveform definitions - Form factor - Peak factor - study of R-L - R-C -RLC series circuit - R-L-C parallel circuit - phasor representation in polar and rectangular form - concept of impedance - admittance - active - reactive - apparent and complex power - power factor, Resonance in R-L-C circuits - 3 phase balanced AC Circuits



Practice Problem

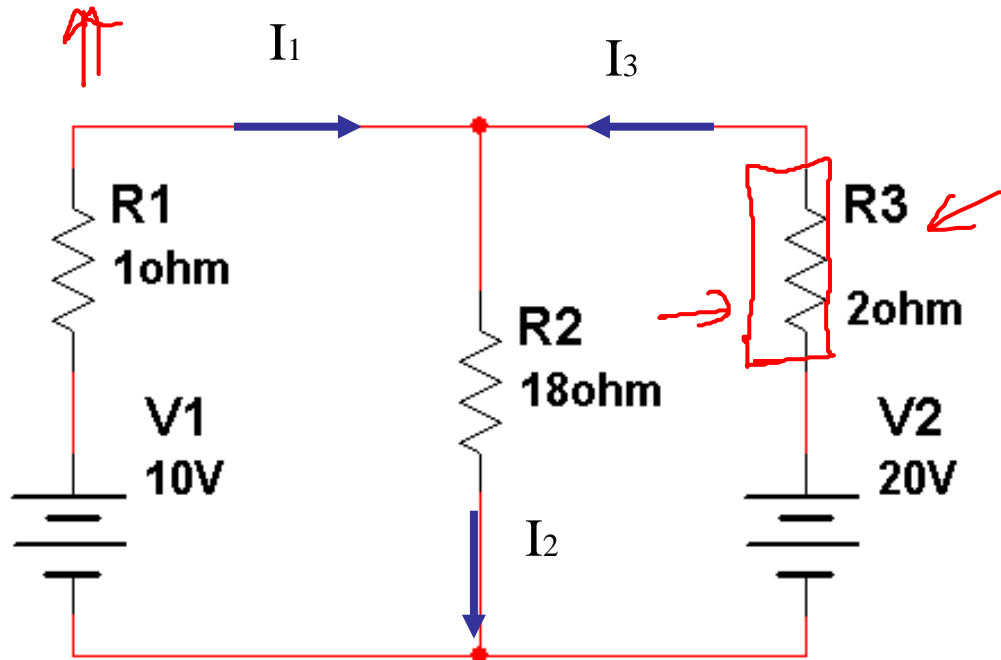

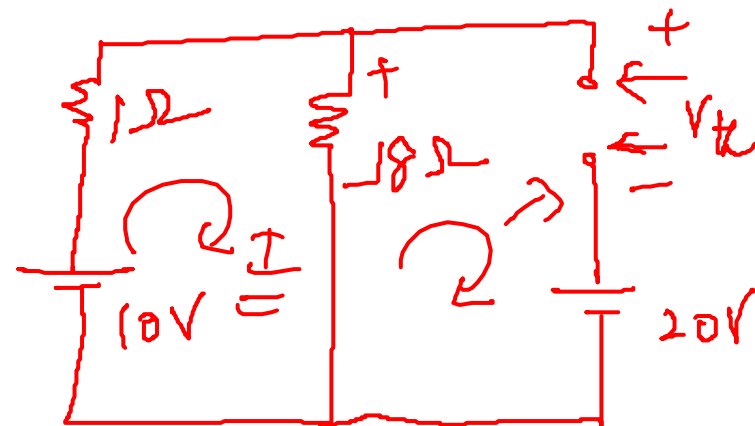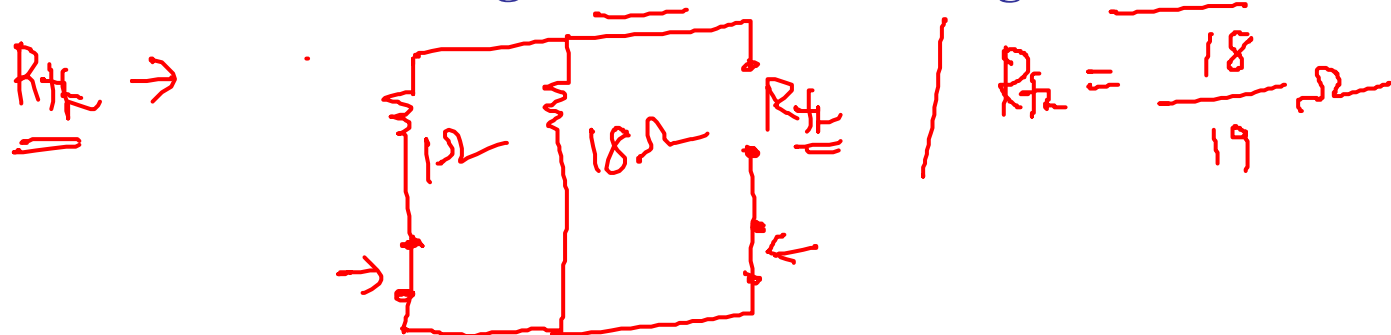Find the current through 2 ohm resistor using Thevenin's theorem



$$I = \frac{V}{R} = \frac{10}{18+1} = \frac{10}{19} \text{ A}$$

$$V_{18\Omega} = \frac{10}{19} \times 18 \text{ V}$$

Let V_L

$$+V_{18\Omega} - V_{th} - 20 = 0$$


$$V_{th} = V_{18\Omega} - 20$$

$$= \frac{180}{19} - 20$$

$$V_{th} = -10.52 \text{ (V)}$$


Norton's Theorem

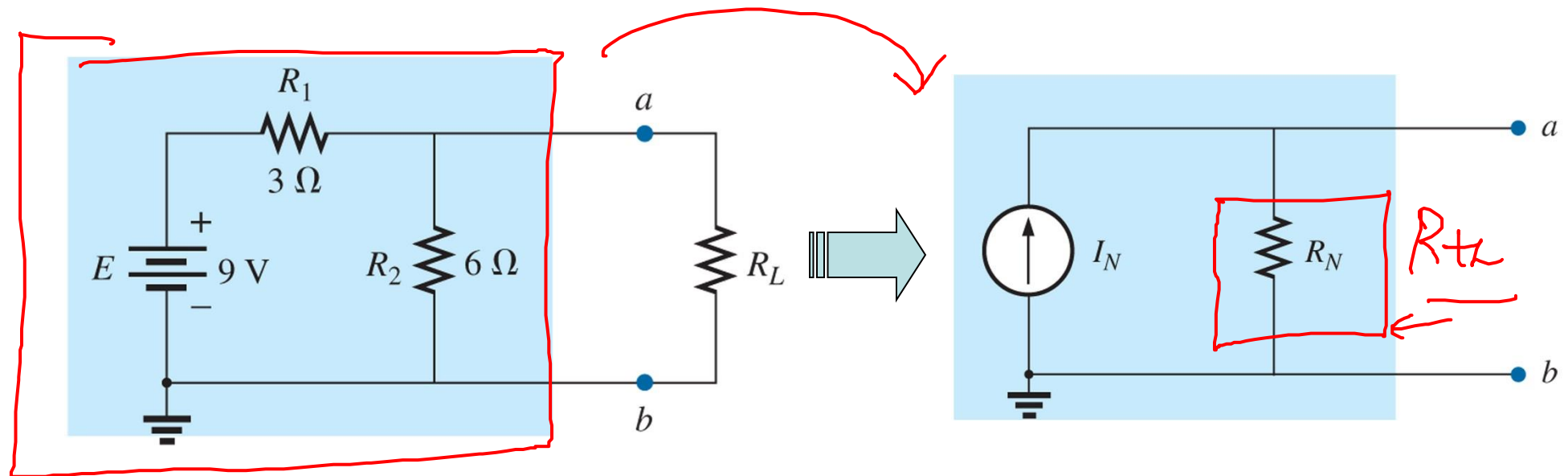- The theorem states that,
 - ⌘ Any two-terminal linear bilateral dc network can be replaced by an equivalent circuit consisting of a current and a parallel resistor.




Norton's Theorem Procedure

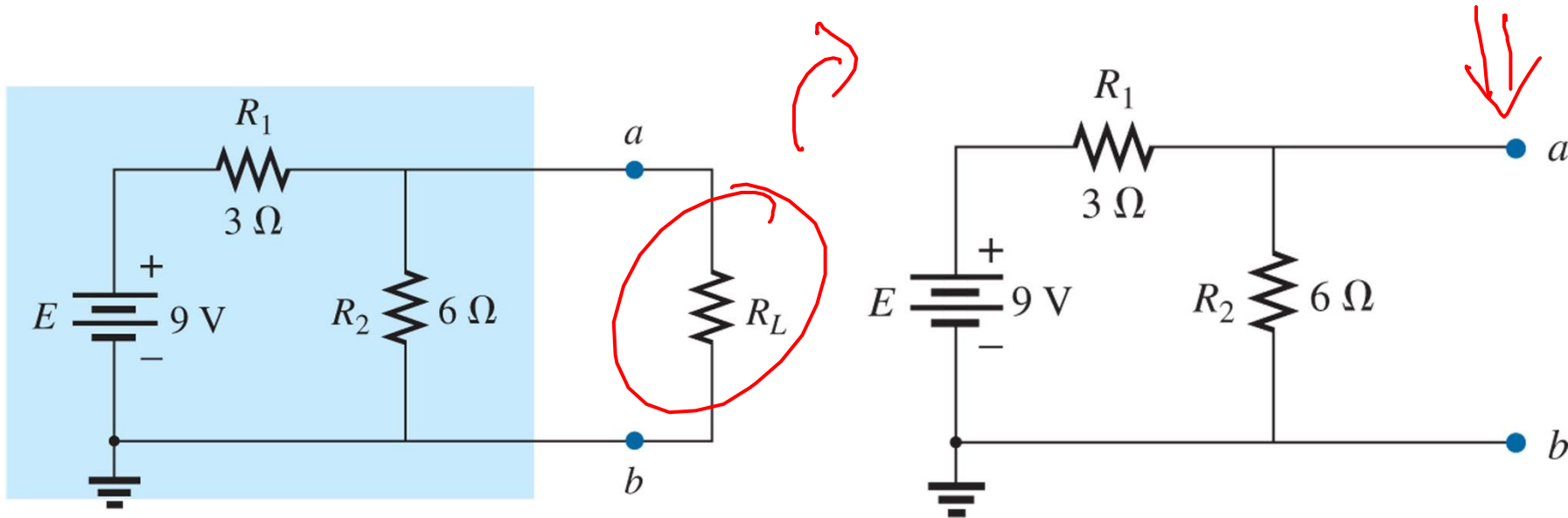- Step 1: Remove the portion of the network across which the Norton equivalent circuit is found.
- Step 2: Mark the terminal as a and b. We have an open circuit across terminal a and b.



Norton's Theorem Procedure

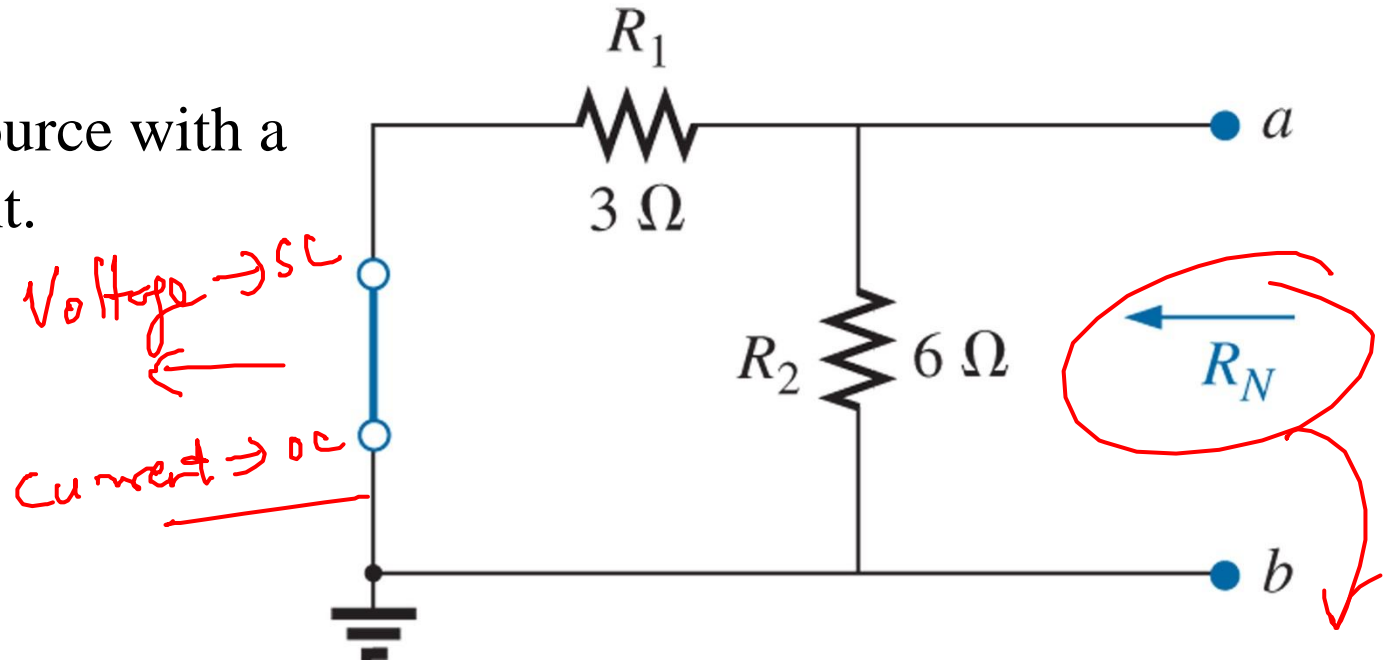- Step 3:
 - Replace the voltage source with a short-circuit equivalent.
 - Calculate the R_N



$$R_N = R_1 \parallel R_2 = \frac{3 \times 6}{3 + 6} = 2\ \Omega$$

I_N


V_{th} \rightarrow

Prevents

Norton's Theorem Procedure


- Step 4: Indicate the short circuit connection between the terminal a and b.
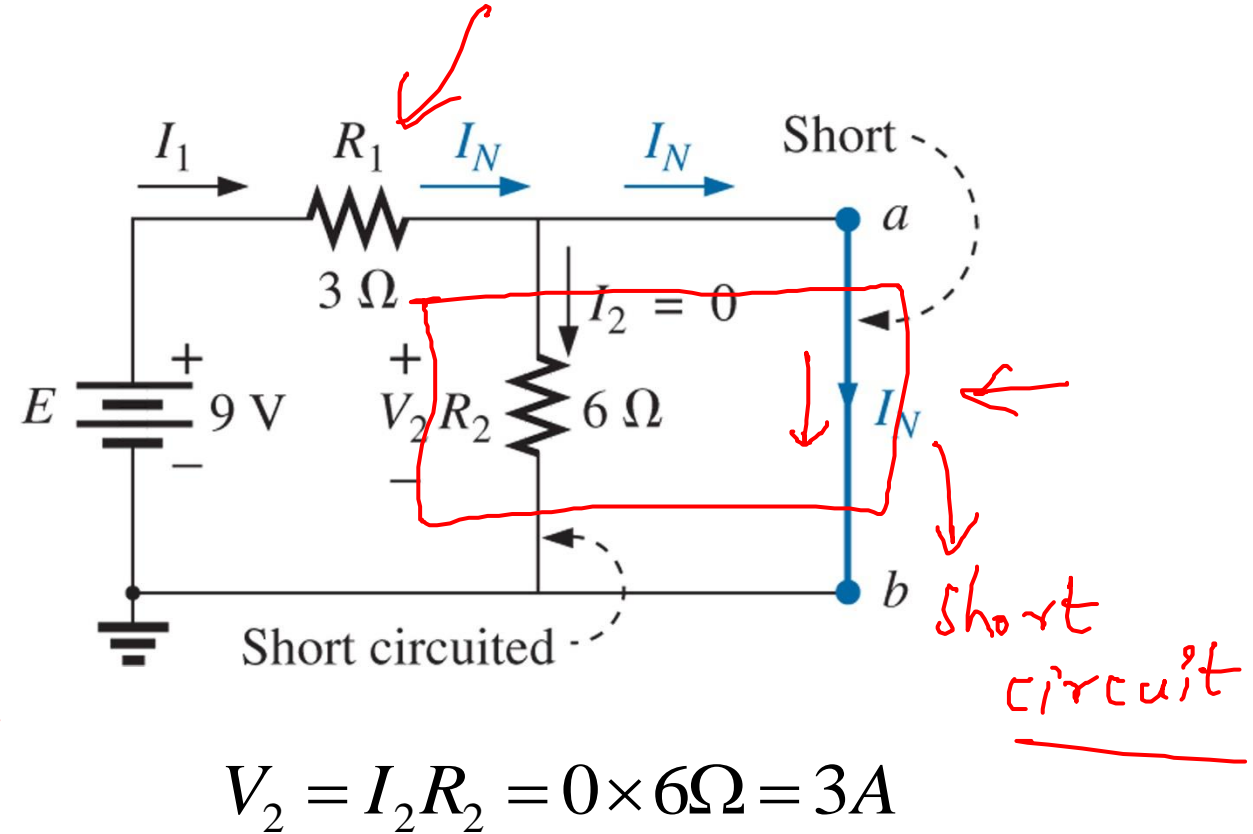
$$I_N = \frac{E}{R_1} = \frac{9V}{3\Omega} = \underline{\underline{3A}}$$




Norton's Theorem Procedure

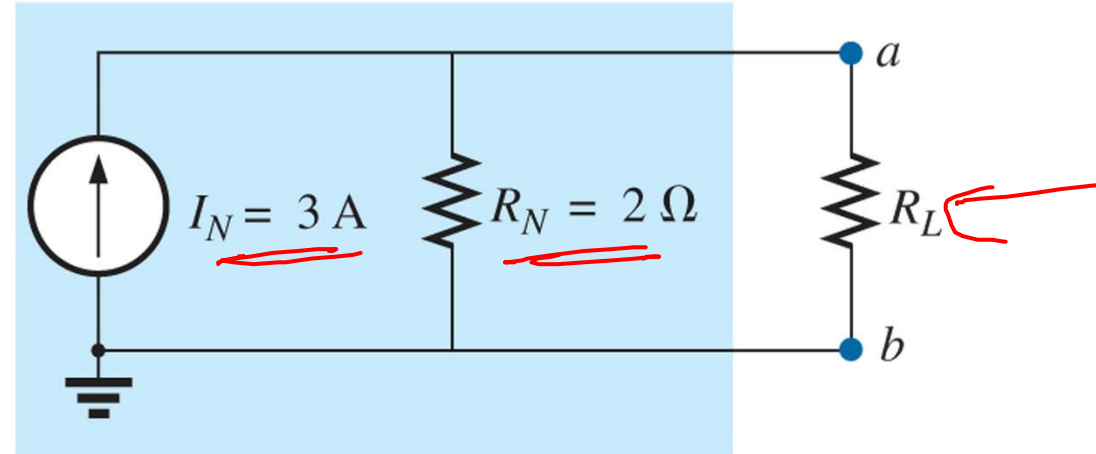Step 5: Draw the norton equivalent circuit.




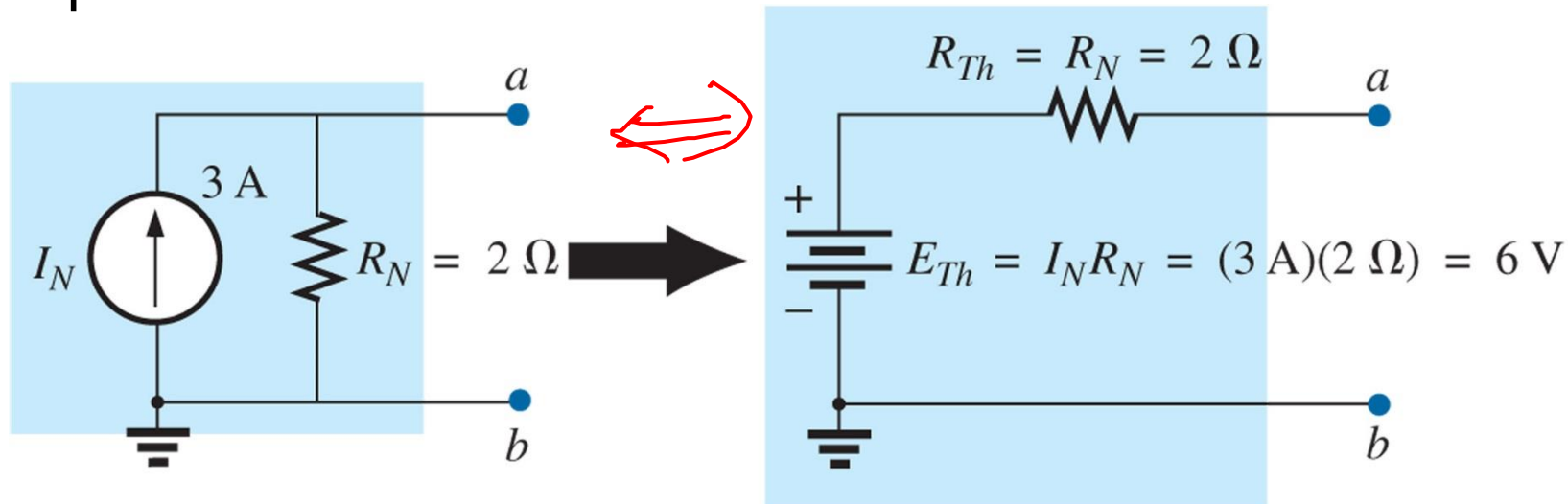Converting the Norton equivalent circuit to a Thevenin equivalent circuit.



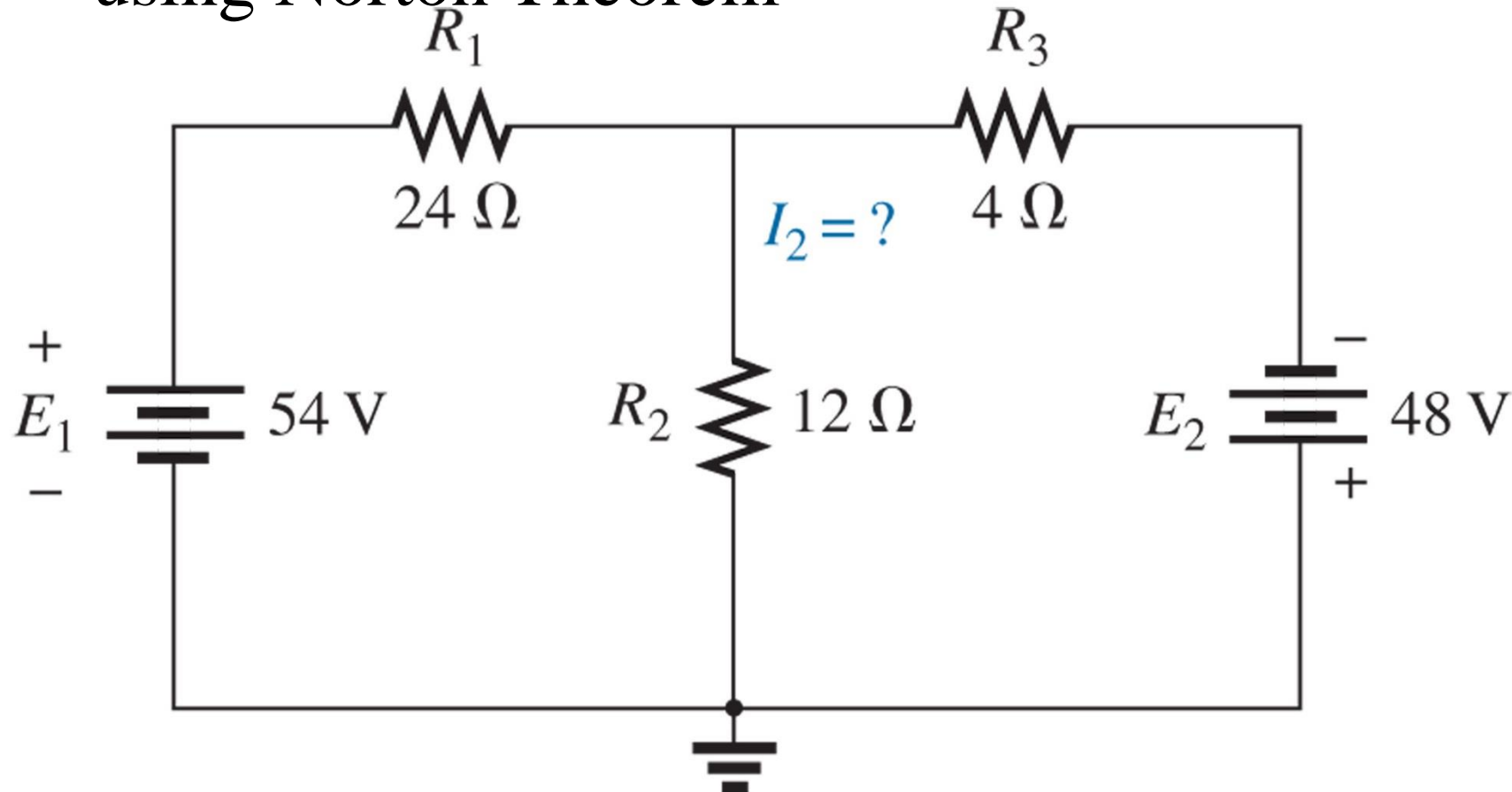Exercise

- Determine the current in the $12\ \Omega$ resistor using Norton Theorem




Maximum Power Transfer Theorem

⌘ The maximum power transfer theorem states the following:

A load will receive maximum power from a network when its total resistive value is exactly equal to the Thévenin resistance of the network applied to the load. That is,

$$R_L = R_{Th}$$

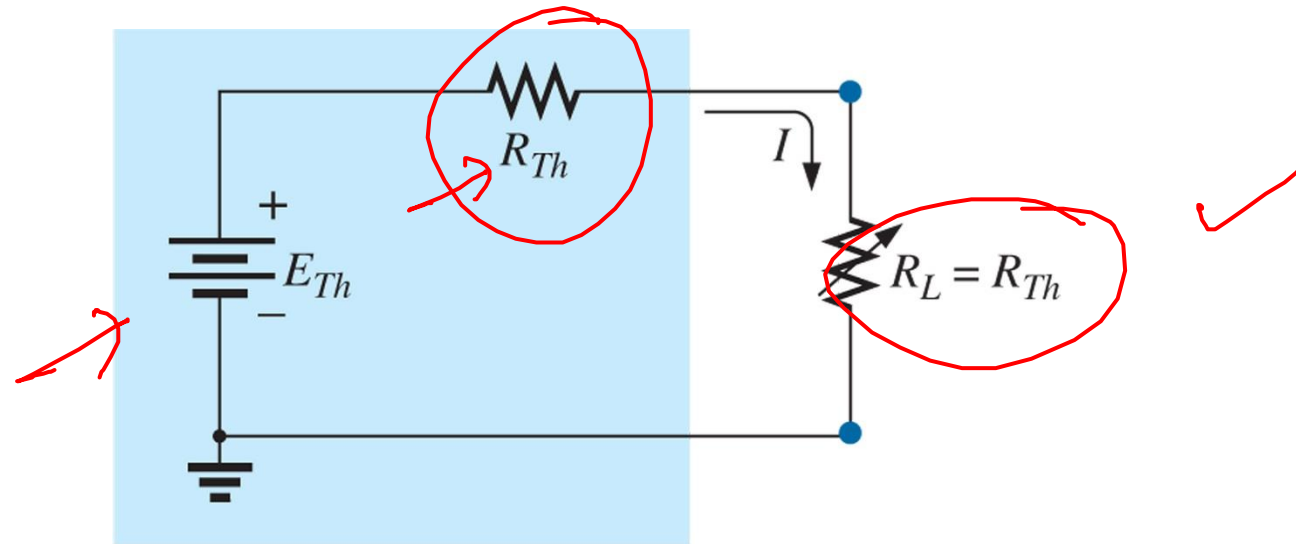- For the Thevenin equivalent circuit like the figure below, when the load is equal to the Thevenin resistance, the load will receive maximum power from the network



- With $R_L = R_{Th}$, the maximum power delivered to the load can be determined by first finding the current:


$$I_L = \frac{E_{Th}}{R_{Th} + R_L} = \frac{E_{Th}}{R_{Th} + R_{Th}} = \frac{E_{Th}}{2R_{Th}}$$

$$I = \frac{V}{R} = \frac{E_{Th}}{R_{Th} + R_L}$$




$$P_L = I^2 R_L = \left(\frac{E_{Th}}{2R_{Th}} \right)^2 R_{Th} = \frac{E_{Th}^2 R_{Th}}{4R_{Th}^2}$$

$$R_{Th} = R_L$$
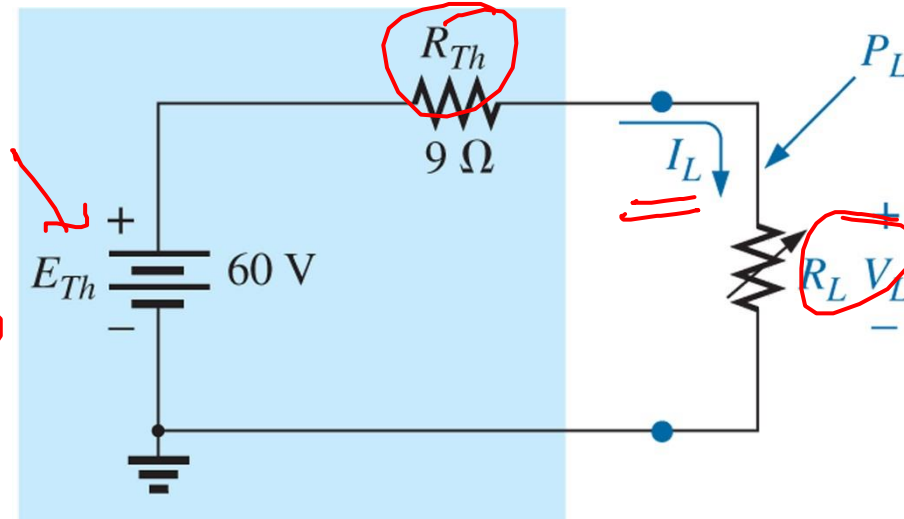
$$P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}}$$




P_L versus R_L for the network

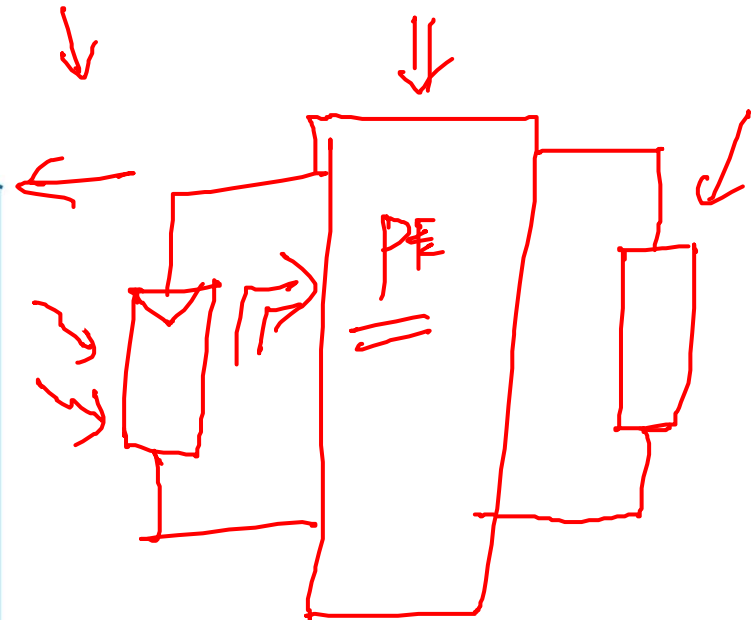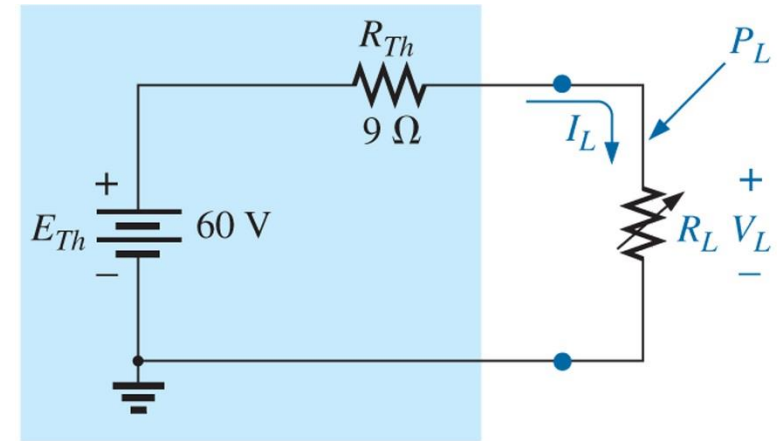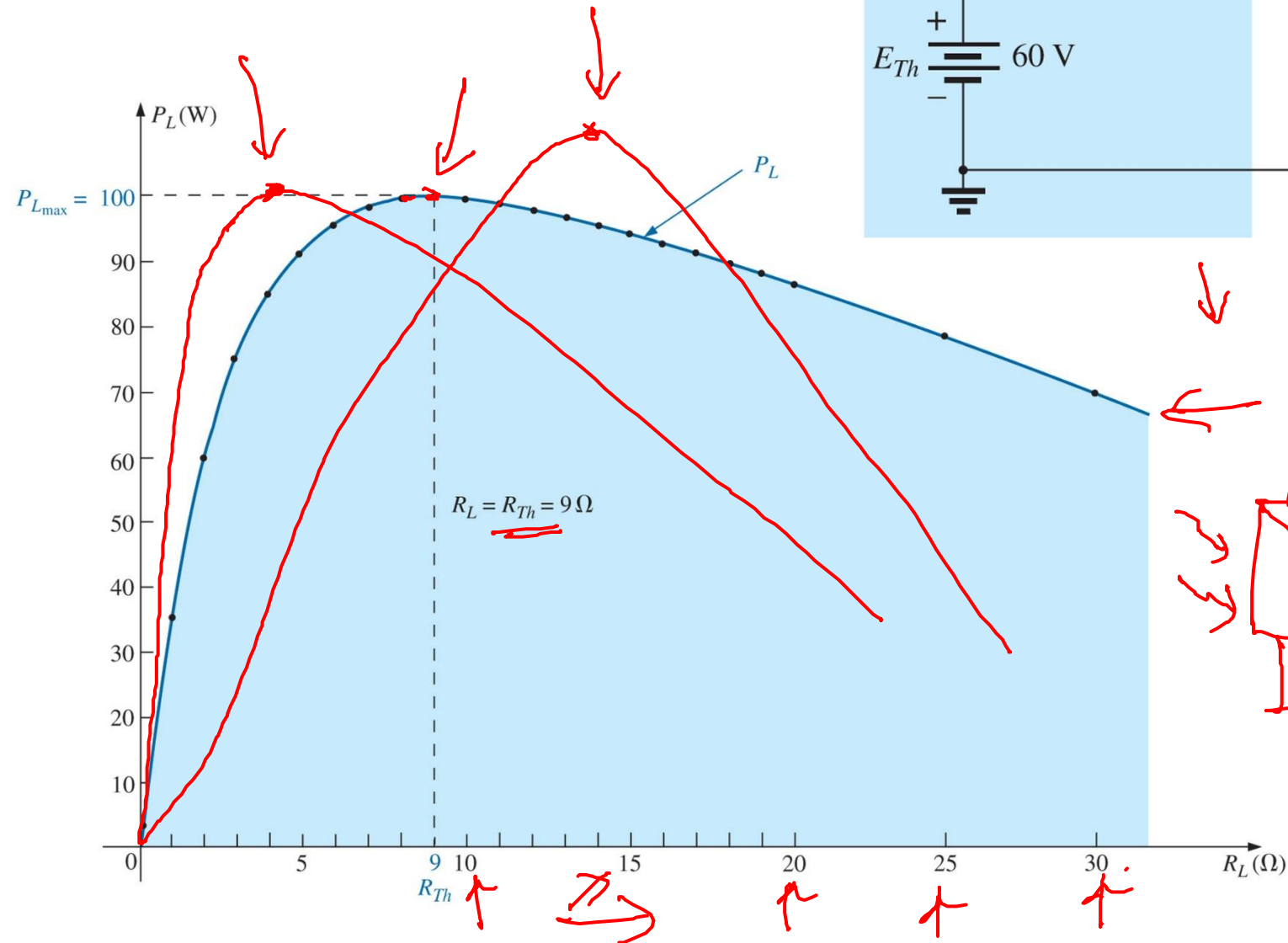

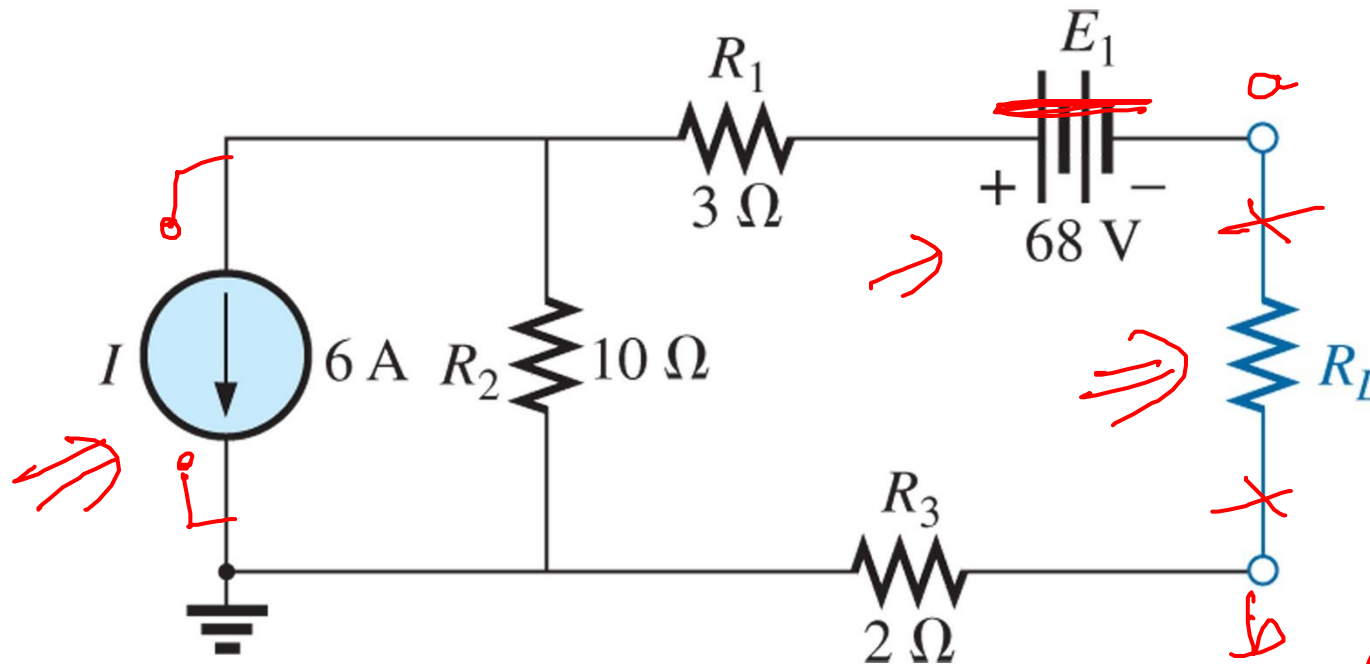Example

- For the circuit below, determine
 - The value of the load resistor, R_L , which would give the maximum power transfer.
 - The maximum power transferred to the load



To find R_{th}

- ① Remove load
- ② Turn off sources
└ $V \rightarrow \text{sc}$
└ $I \rightarrow \text{oc}$
- ③ R_{th}

Example 9.4

- The Thevenin resistance

is
$$R_{Th} = R_1 + R_2 + R_3$$

$$= 3 + 10 + 2 = 15\Omega$$



so that

$$R_L = R_{Th} = \underline{15\Omega} \quad \leftarrow$$

- Determine the Thevenin voltage

$$V_1 = V_3 = 0$$
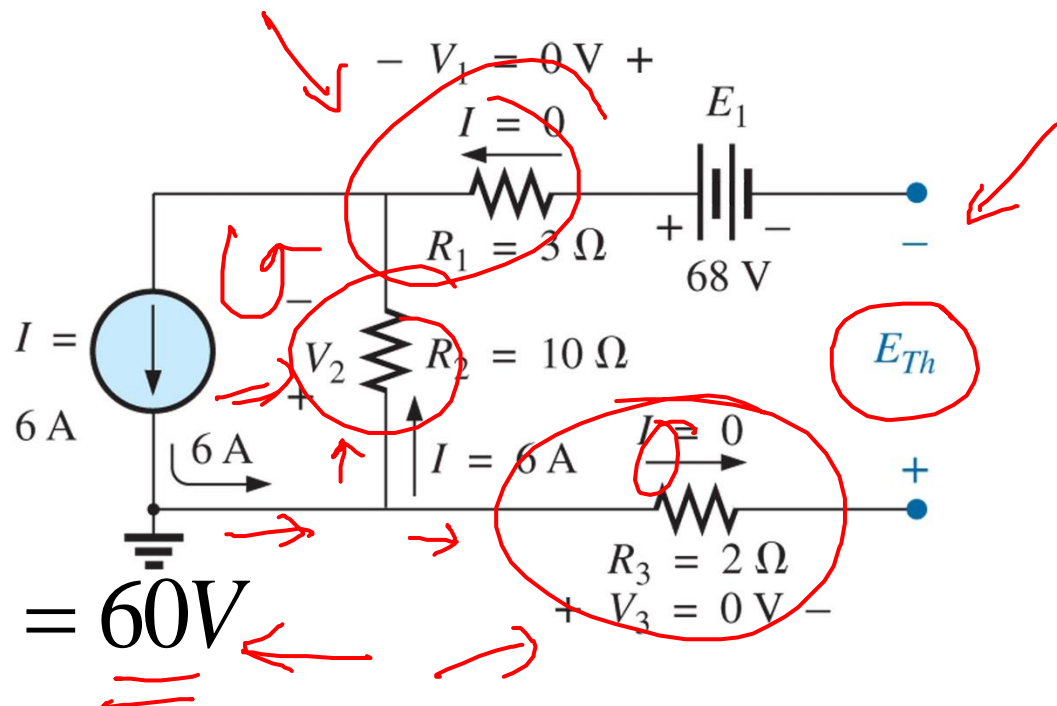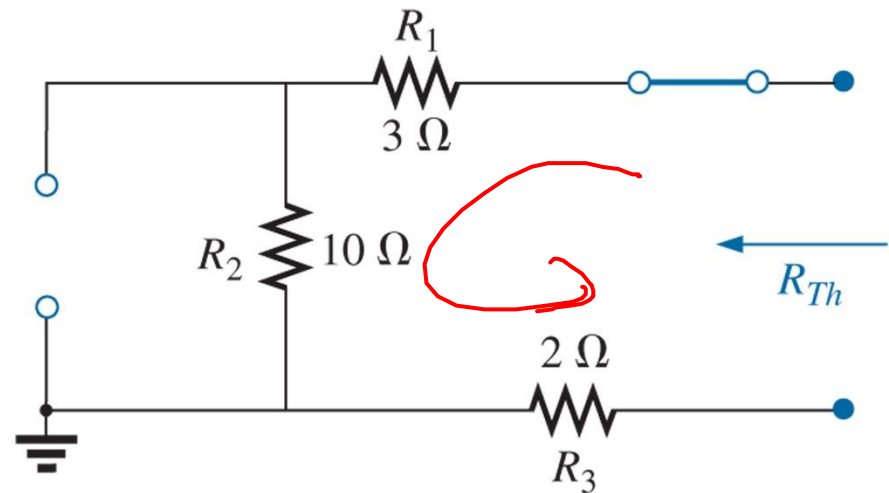
$$V_2 = I_2 R_2 = IR_2 = \underline{6 \times 10} = \underline{60V}$$



Example

$$+E_{th} + V_3 - V_2 + V_1 - E_1 = 0$$

$$E_{th} - V_2 - E_1 = 0$$


$$E_{th} - 60 - 68 = 0$$

- Applying KVL

$$-V_2 - E_1 + E_{Th} = 0$$

$$E_{Th} = V_2 + E_1 = 60 + 68 = 128V$$
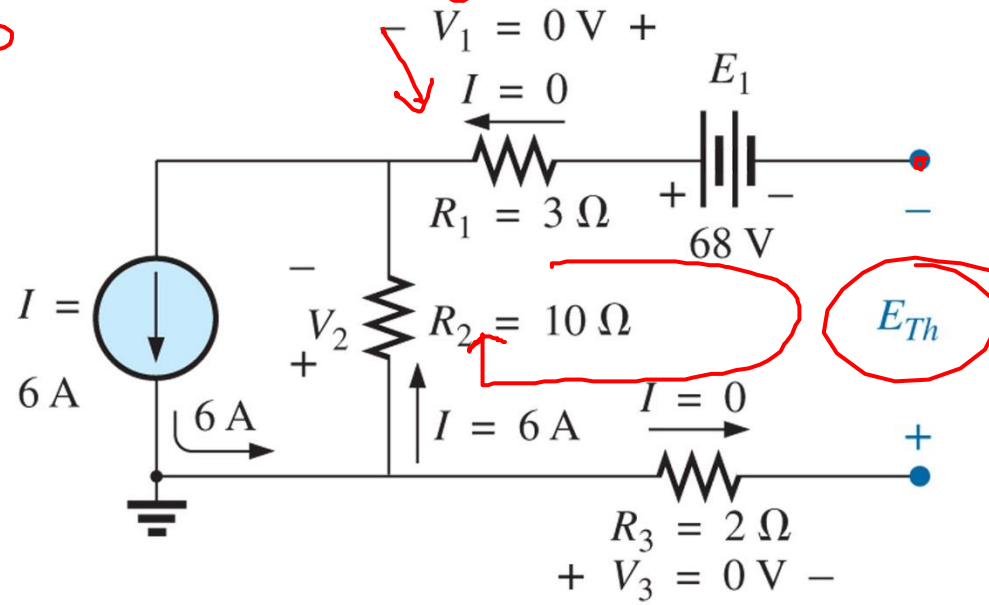
$$P_{L_{max}} = \frac{E_{Th}^2}{4R_{Th}} = \frac{128^2}{4(15\Omega)} = 273.07W$$



Summary

→ Thevenin's → Norton's

