

# Unit - III 3.4 Ideal Transformer, Losses and Efficiency

Dr.Santhosh.T.K.



# World's Largest Transformer



- SIEMENS's <u>transformer factory</u> in Nuremberg (Germany) to China
- 1,100KV transformer for the world's largest HVDC project in China
- capacity of 587 MVA
- Transformer size: 37.5 x 12 x 14.4 (m)
- Weight ~ 900 tons







# **Syllabus**

UNIT – III 10 Periods

Principles of Electro Magnetics and Electro-mechanics: Electricity and Magnetism - magnetic field and faraday's law - self and mutual inductance - Ampere's law - Magnetic circuit - Magnetic material and B-H Curve – Single phase transformer - principle of operation - EMF equation - voltage ratio - current ratio – KVA rating - Electromechanical energy conversion – Elementary generator and motors.

## Ideal Transformers

#### • Zero leakage flux:

-Fluxes produced by the primary and secondary currents are confined within the core

#### The windings have no resistance:

- Induced voltages equal applied voltages


#### The core has infinite permeability

- Reluctance of the core is zero
- Negligible current is required to establish magnetic flux

  Primary


#### • Loss-less magnetic core


- No hysteresis or eddy currents

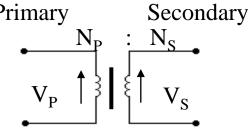

Symbol for ideal transformer

# Ideal transformer

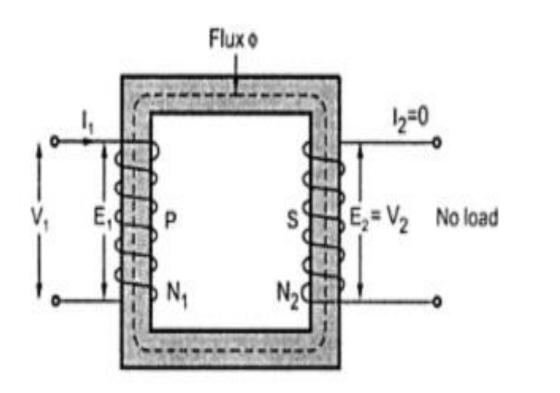

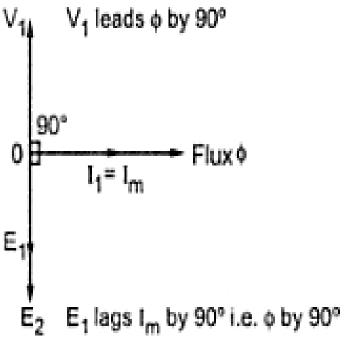

```
V_1 – supply voltage;
```

V<sub>2</sub>- output voltgae;

I<sub>m</sub>- magnetising current;

E<sub>1</sub>-self induced emf;

I<sub>1</sub>- noload input current;

I<sub>2</sub>- output current

E<sub>2</sub>- mutually induced emf

# **Transformer Equations**

Using Faraday's law, expressions for the primary and secondary voltages is as follows.

$$V_2 = N_2 \frac{d\Phi}{dt}. \qquad V_1 = N_1 \frac{d\Phi}{dt}.$$

Dividing the above equations we get,

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}.$$

Assuming that there is no power loss,

$$\begin{aligned} V_2I_2 &= V_1I_1.\\ \frac{V_2}{V_1} &= \frac{I_1}{I_2} = \frac{N_2}{N_1} = K. \quad \text{K - transformation ratio} \end{aligned}$$

# EMF Equation of a transformer

Let  $N_1$  = No. of primary turns

 $N_2$  = No. of secondary turns

 $\phi_m$ = Maximum flux density in transformer core in Weber

 $=B_{\rm m}A$  where  $B_{\rm m}$ -> flux density in the transformer core

A -> cross sectional Area of the transformer In an EMF equation, flux increases from its zero value to maximum value  $\Phi_{\rm m}$  in one quarter of cycle

Average rate of change of flux = 
$$\Phi_m/(1/4f)=4f \Phi_m$$
 wb/sec .....(1)

The average value of emf induced / turn =  $4f \Phi_m$  .....(2)

If flux  $\Phi_m$  varies sinusoid ally, then R.M.S value of induced EMF is obtained by multiplying the average value with form factor.

# EMF Equation of a transformer -contd

Form factor=R.M.S value/Average value = 
$$Vm/\sqrt{2}$$
 .....(3)  
= 1.11 (for sine wave)

R.M.S value of EMF/turn=
$$1.11*4f\Phi_{\rm m}$$
 volts .....(4)


Now,

R.M.S value of the induced EMF in the whole primary winding = (induced EMF/turn)\*No of primary turns.

$$E_1 = 4.44 f N_1 \Phi_m$$
 .....(5)

IIIy,

$$E_2 = 4.44 f N_2 \Phi_m$$
 .....(6)

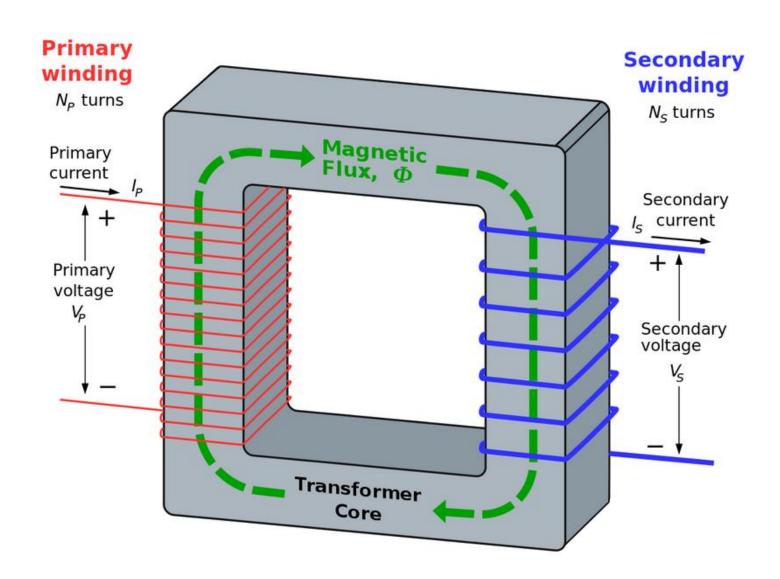

## EMF equation of transformer - contd

If  $i_p$  is sinusoidal, the flux produced also sinusoidal, i.e

$$\Phi = \Phi_m \sin 2\pi ft \qquad \dots (7)$$

therefore 
$$v_1 = N_1 \frac{d(\Phi_m \sin 2\pi ft)}{dt}$$

$$v_1 = N_1 2\pi f \Phi_m \cos 2\pi f t = N_1 2\pi f \Phi_m \sin (2\pi f t + \pi/2)$$
 .....(8)

The peak value = 
$$V_{pm} = N_1 2\pi f \Phi_m$$
 .....(9)

and  $v_1$  is leading the flux by  $\pi/2$ .

The rms value 
$$V_1 = \frac{V_{1m}}{\sqrt{2}} = 0.707 \times N_1 2\pi f \Phi_m = 4.44 N_1 f \Phi_m$$
 .....(10)

# Voltage regulation of Transformer

Voltage regulation = 
$$\frac{\text{no-load voltage} - \text{full-load voltage}}{\text{no-load voltage}}$$

recall 
$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

Secondary voltage on no-load  $V_2 = V_1 \left( \frac{N_2}{N_1} \right)$ 

V<sub>2</sub> is a secondary terminal voltage on full load

Substitute we have 
$$V_1 \left( \frac{N_2}{N_1} \right) - V_2$$
Voltage regulation = 
$$\frac{V_1 \left( \frac{N_2}{N_1} \right) - V_2}{V_1 \left( \frac{N_2}{N_1} \right)}$$

## Transformer Efficiency

Transformer efficiency is defined as (applies to motors, generators and

transformers):

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

Copper I<sup>2</sup>R losses

Hysteresis losses

Eddy current losses

Therefore, for a transformer, efficiency may be calculated using the following:

$$\eta = \frac{V_S I_S \cos \theta}{P_{Cu} + P_{core} + V_S I_S \cos \theta} x 100\%$$

# All day efficiency


All day efficiency is defined as the ratio of total energy output of transformer to thetotal energy input in 24 hours.

ordinary commercial efficiency = 
$$\frac{\text{out put in watts}}{\text{input in watts}}$$

$$\eta_{all \, \text{day}} = \frac{\text{output in kWh}}{\text{Input in kWh}} (for 24 \text{ hours})$$

•All day efficiency is always less than the commercial efficiency
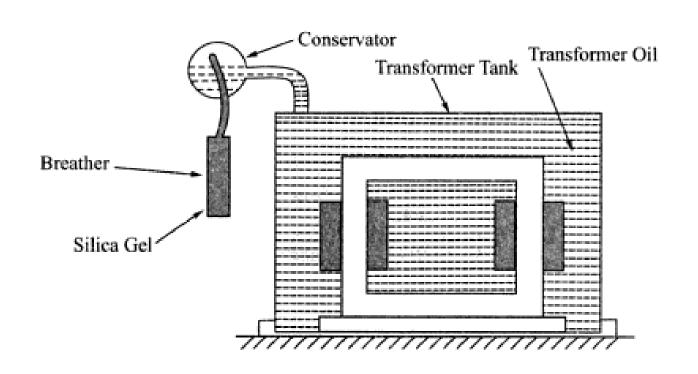
#### Transformer with conservator and breather





#### Parts of a transformer

#### Conservator

- · Oil is stored in the conservator
- It prevents the oil from moisture contact in air during the expansion and contraction.


#### Breather

- It is a device which contains silica gel crystals.
- The gel absorbs the moisture in the atmosphere when the oil expands and contracts.


#### Explosive Vent

- It bursts when pressure inside the transformer becomes excessive and protects the transformer from damage.
- Transformer Tank filled with transformer Oil

## Transformer-No load condition

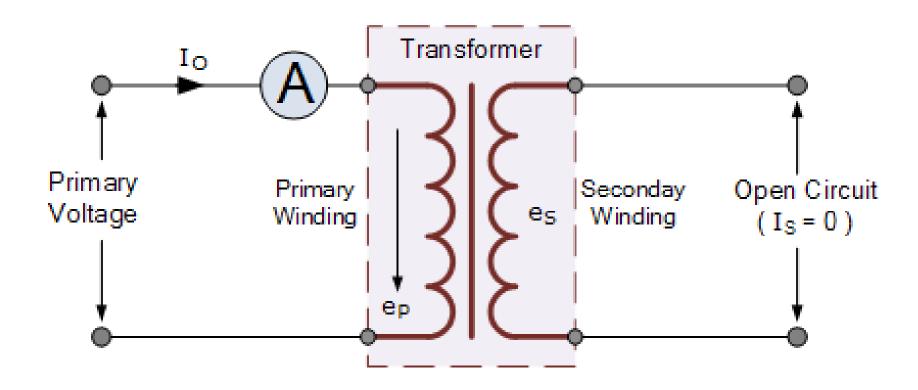


# Phasor diagram: Transformer on No-load

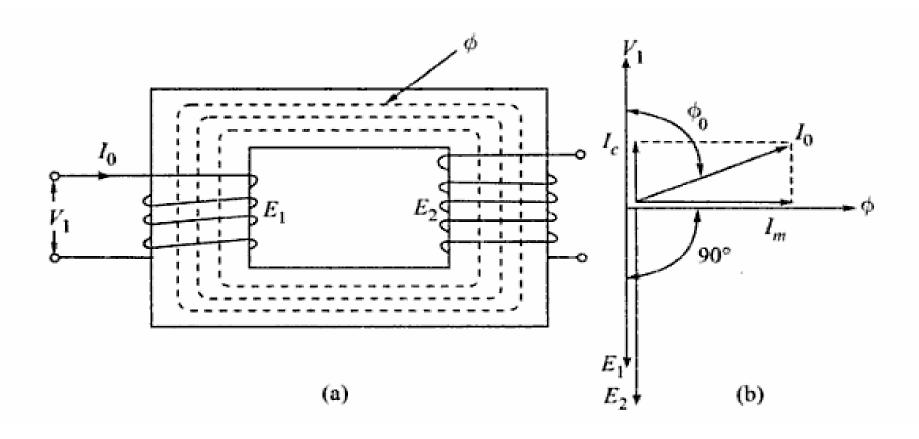


(a) Transformer on no-load (b) Phasor diagram of a transformer on no-load

# Transformer – On load condition

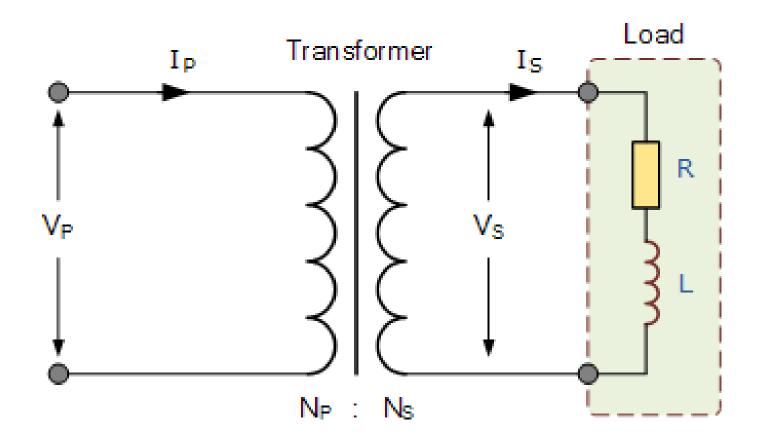

Given that the intermediate current is 1 A, what is the current through the lightbulb?

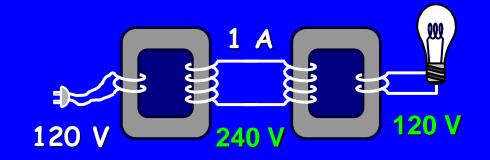- 1) 1/4 A
- 2) 1/2 A
- 3) 1 A
- 4) 2 A
- 5) 5 A




Given that the intermediate current is 1 A, what is the current through the lightbulb?

- 1) 1/4 A
  2) 1/2 A
  3) 1 A
  4) 2 A
  - 5) 5 A

Powerin = Powerout

 $240 \text{ V} \times 1 \text{ A} = 120 \text{ V} \times ???$ 


The unknown current is 2 A.

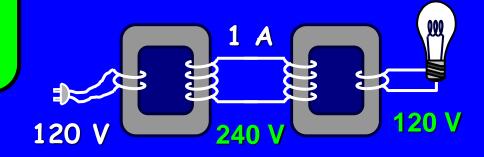

A 6 V battery is connected to one side of a transformer.

Compared to the voltage drop across coil A, the voltage across coil B is:

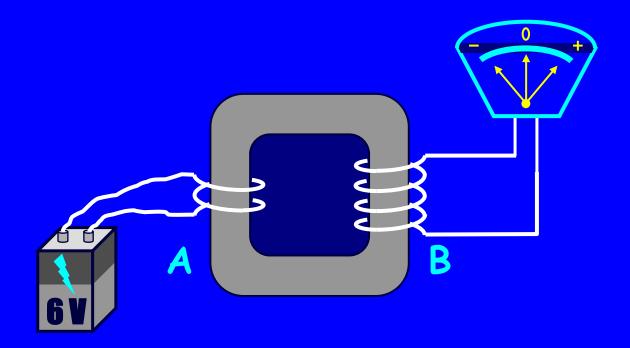- 1) greater than 6 V
- 2) 6 V
- 3) less than 6 V
- 4) zero



A 6 V battery is connected to one side of a transformer.

Compared to the voltage drop across coil A, the voltage across coil B is:

- 1) greater than 6 V
- 2) 6 V
- 3) less than 6 V
- 4) zero

The voltage across B is zero.
Only a changing magnetic flux induces an emf. Batteries can provide only dc current.

1. A 250 kVA, 11 000 V/400 V, 50 Hz single-phase transformer has 80turns on the secondary. Calculate: (a) the approximate values of the primary and secondary currents; (b) the approximate number of primary turns; (c) the maximum value of the flux.

2. The maximum flux density in the core of a 250/3000-volt, 50 Hz transformer is 1.2 Wb/m^2. If the EMF per turn is 8 V, determine (i) primary and secondary turns

# Voltage regulation of Transformer

Voltage regulation = 
$$\frac{\text{no-load voltage} - \text{full-load voltage}}{\text{no-load voltage}}$$

recall 
$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$

Secondary voltage on no-load  $V_2 = V_1 \left( \frac{N_2}{N_1} \right)$ 

V<sub>2</sub> is a secondary terminal voltage on full load

Substitute we have 
$$V_1 \left( \frac{N_2}{N_1} \right) - V_2$$
Voltage regulation = 
$$\frac{V_1 \left( \frac{N_2}{N_1} \right) - V_2}{V_1 \left( \frac{N_2}{N_1} \right)}$$

## Transformer Efficiency

Transformer efficiency is defined as (applies to motors, generators and

transformers):

$$\eta = \frac{P_{out}}{P_{in}} \times 100\%$$

$$\eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

Copper I<sup>2</sup>R losses

Hysteresis losses

Eddy current losses

Therefore, for a transformer, efficiency may be calculated using the following:

$$\eta = \frac{V_S I_S \cos \theta}{P_{Cu} + P_{core} + V_S I_S \cos \theta} x 100\%$$

# Losses in a transformer

Core or Iron loss:

$$W_h = \eta B_{max}^{1.6} fV watt$$

$$W_e = \eta B_{max}^2 f^2 t^2 \ watt$$

Copper loss:

Total Copper loss = 
$$I_1^2 R_1 + I_2^2 R_2$$


4. In a 25-kVA, 2000/200 V single phase transformer, the iron and full-load copper losses are 350 and 400 W respectively. Calculate the efficiency at unity power factor at full load.


5. In a 25-kVA, 2000/200 V single phase transformer, the iron and full-load copper losses are 350 and 400 W respectively. Calculate the efficiency with unity power factor at half full-load.

# Summary

- Ideal Transformer
- Problems
  - EMF equation
  - Magnetic Circuits
  - Efficiency
  - Losses

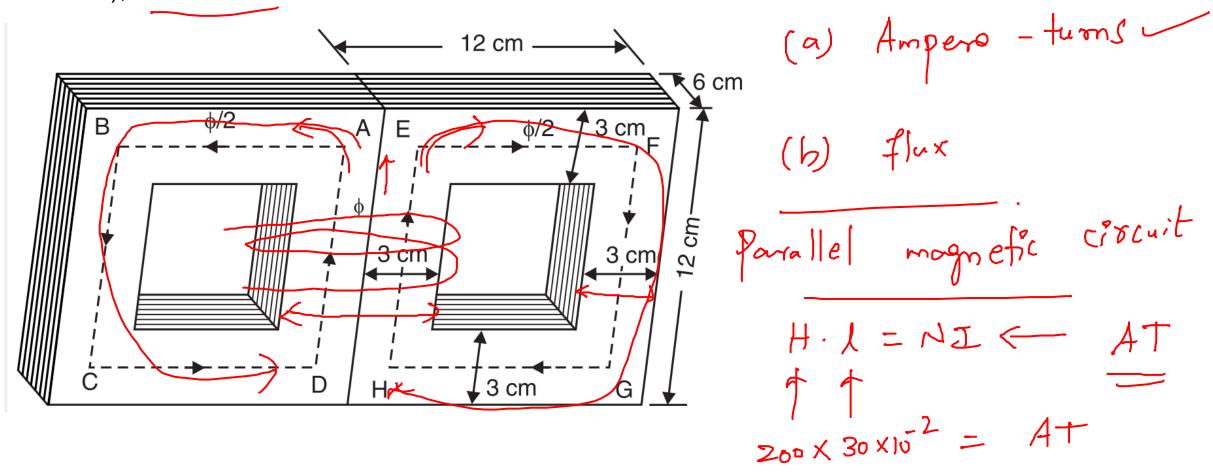3. A transformer core made of annealed steel sheet has the form and dimensions shown in Figure. A coil of N turns is wound on the central limb. The average length of magnetic circuit (i.e. path ABCDA or path EFGHE) is 30 cm. Determine the ampere-turns of the coil required to produce a flux density of 1 Wb/m 2 in the central leg. What will be the total amount of flux in the central leg and in each outside leg? Given that for annealed sheet steel (from B-H curve), H = 200 AT/m at 1 Wb/m 2.



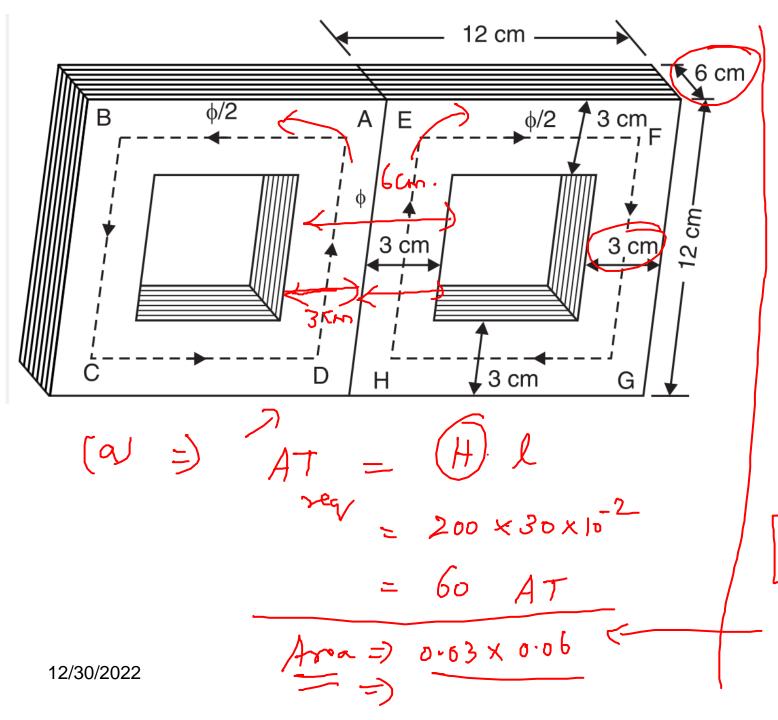

B. = 
$$\frac{4}{h}$$
 $A = \frac{4}{h}$ 
 $A =$