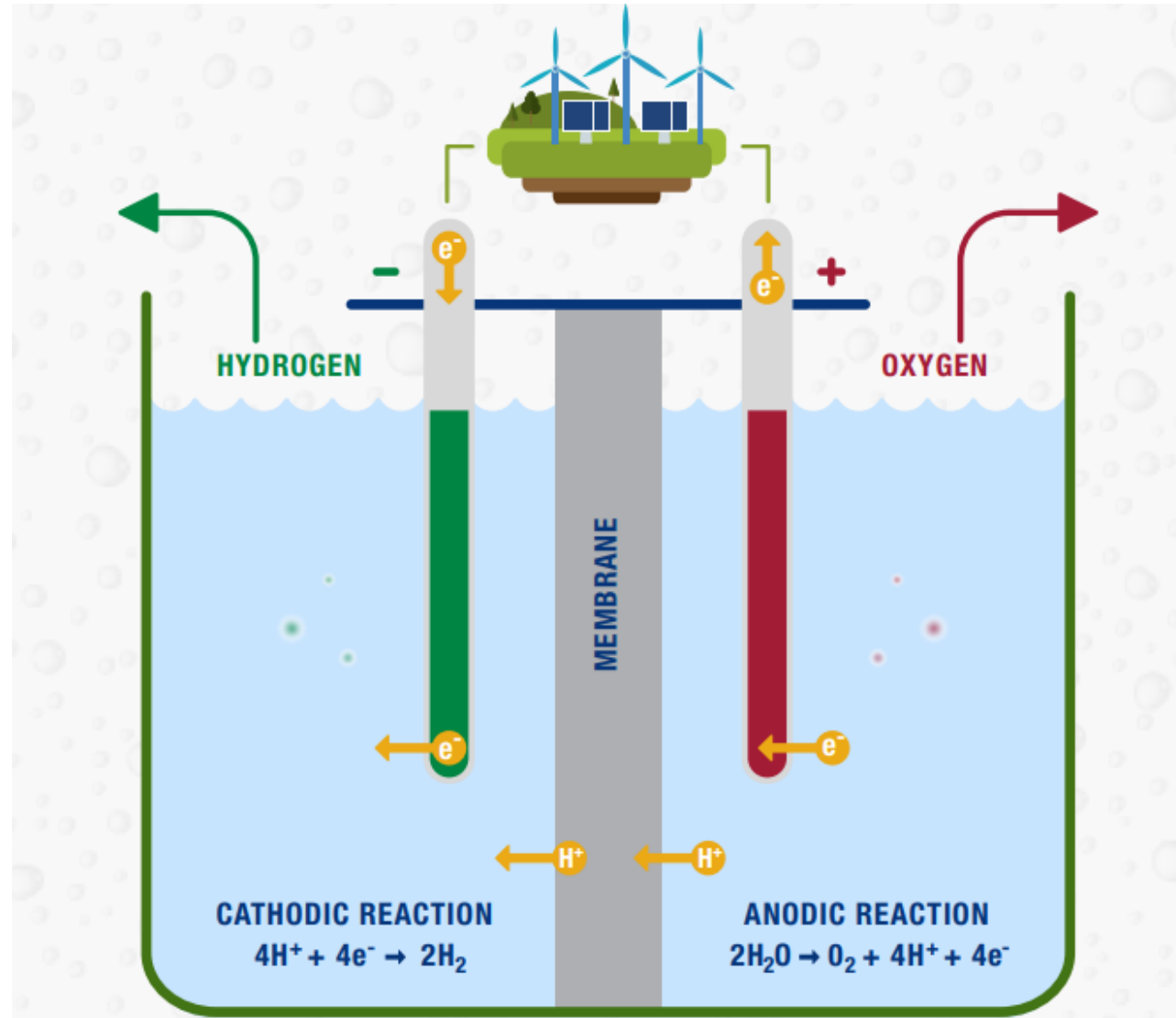


## Unit - III

### 3.6 Generator Types and Elementary Motors

Dr.Santhosh.T.K.

# Green Hydrogen



**ENERGY IN 1 KILOGRAM  
OF HYDROGEN**



**ENERGY IN 1 GALLON  
OF GASOLINE**

**HYDROGEN**

**1 KILOGRAM = 60 MILES**

**GAS**

**1 GALLON = 25 MILES**



# Syllabus


## UNIT – III

10 Periods


**Principles of Electro Magnetism and Electro-mechanics:** Electricity and Magnetism - magnetic field and faraday's law - self and mutual inductance - Ampere's law - Magnetic circuit - Magnetic material and B-H Curve – Single phase transformer - principle of operation - EMF equation - voltage ratio - current ratio – KVA rating - Electromechanical energy conversion – Elementary generator and motors.

**DC Generator**



**Actual DC Generator**

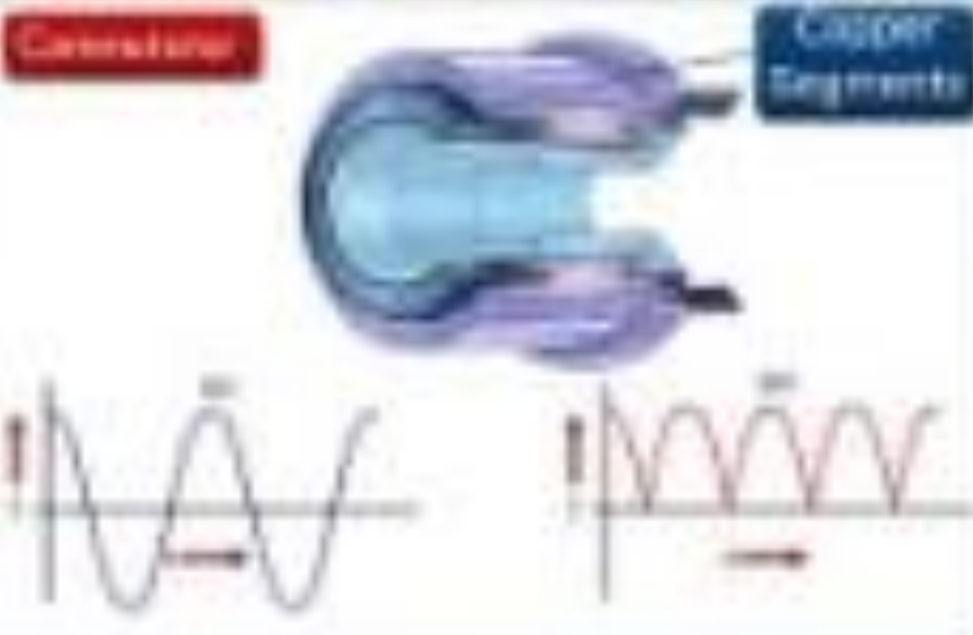

**Construction**



**Copper Segments**




- It facilitates the collection of current from the armature conductors.
- It converts the AC current into **unidirectional current**.
- It is of cylindrical structure and is built up of **slip rings** and **segments** of high conductivity.
- Segments are insulated from each other by thin layers of mica.

# Generators

D.C Generators

A.C Generators  
(Alternators)

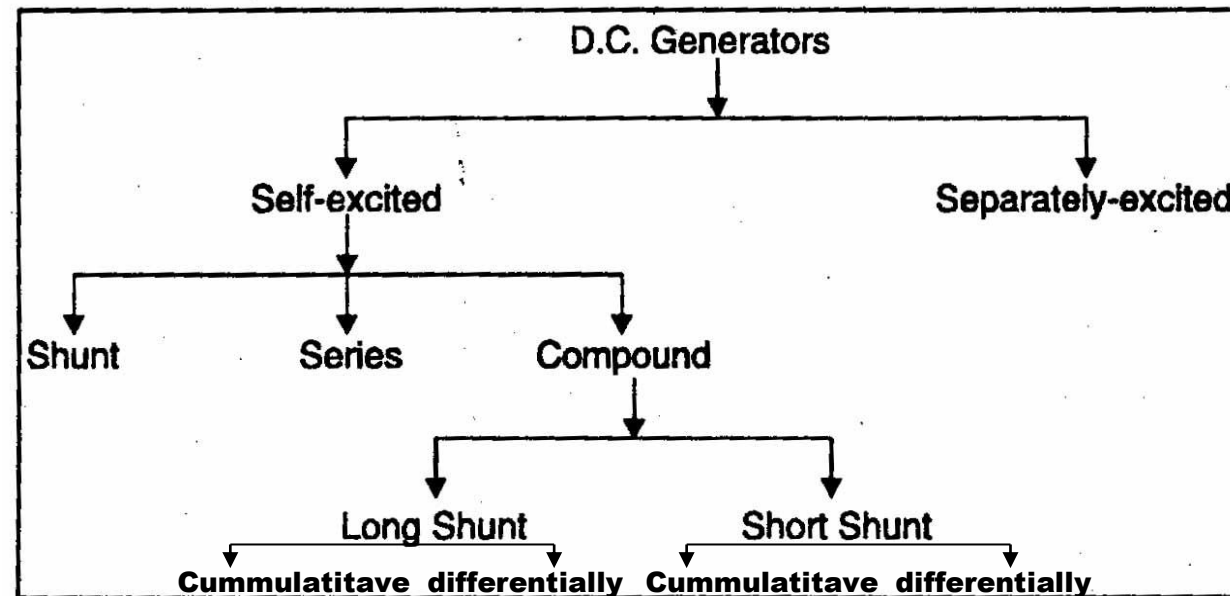

# Types of Generators

1) Separately excited generators

2) Self excited generators

i) shunt wound


ii) series wound

iii) compound wound

a) long shunt


b) short shunt

# Classification of Generators

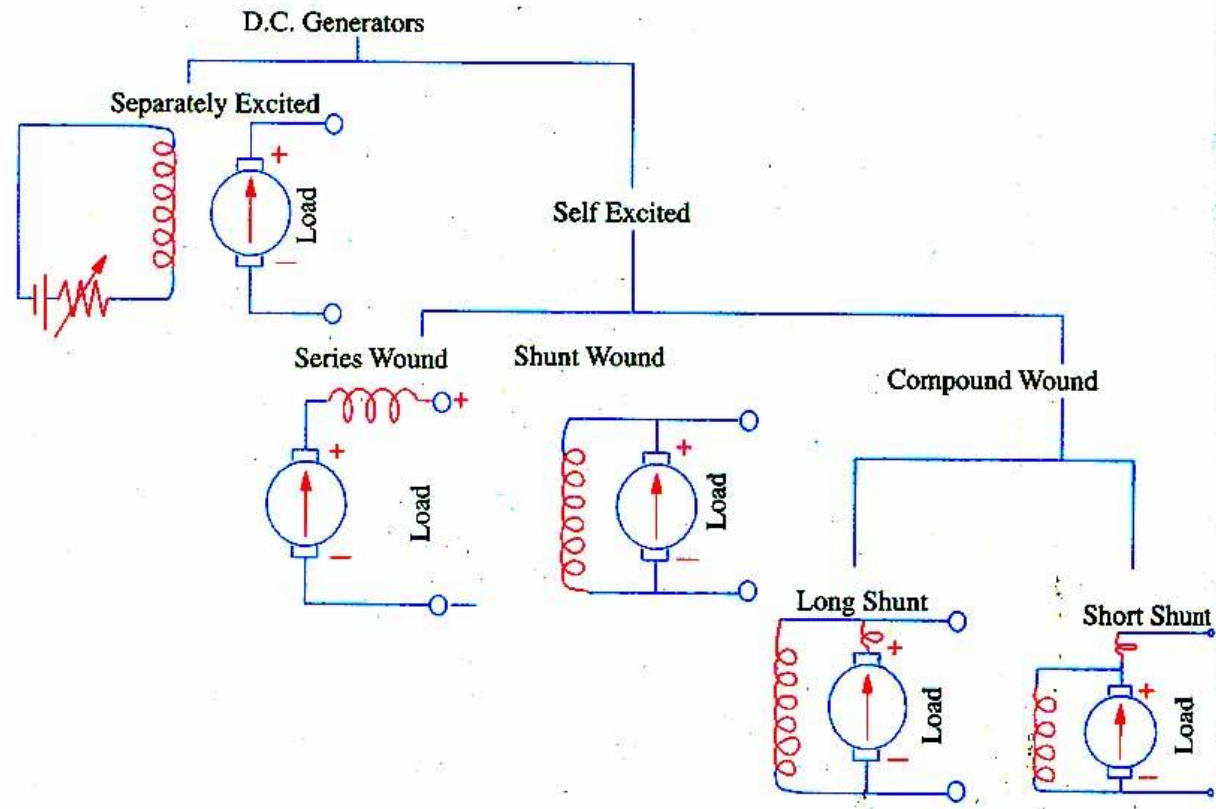




# Separately Excited Generators

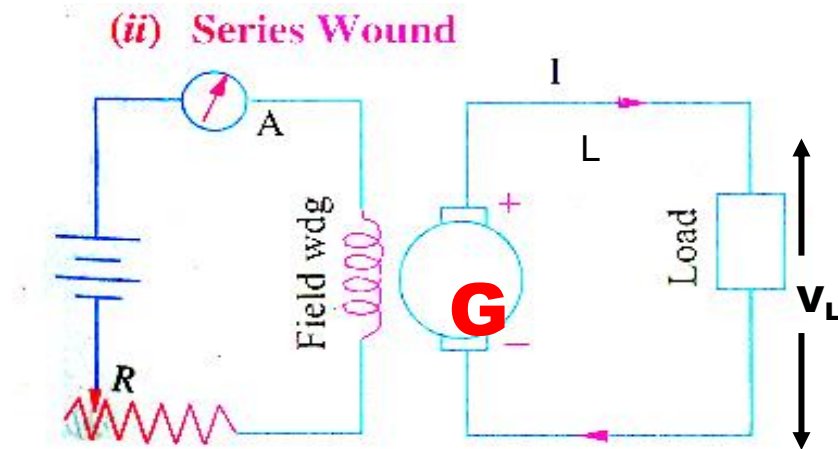

$$I_a = I_L$$

$$E = V_t + I_a R_a + BCD$$

# shunt wound

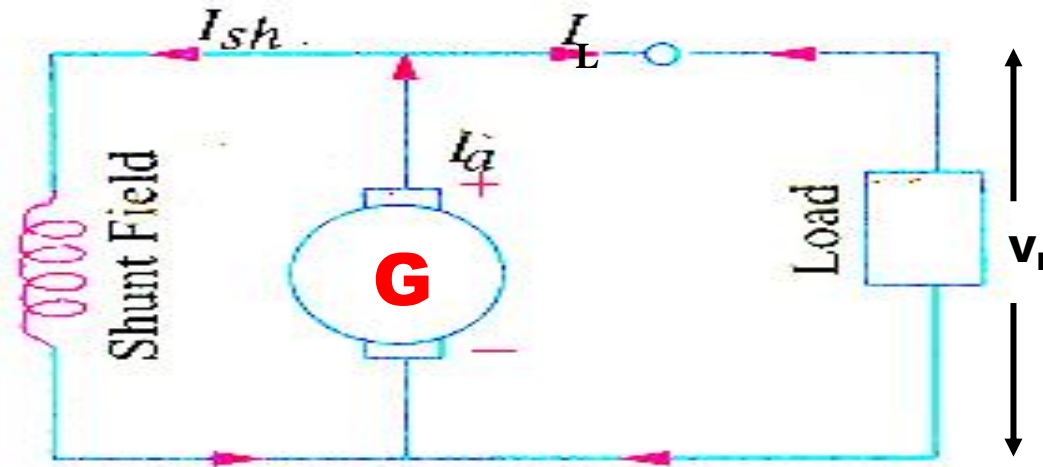

shunt generator

(a)

$$\begin{aligned}
 I_L &= I_a - I_{sh} \\
 I_a &= I_L + I_{sh} \\
 E_g &= V_L + I_a R_a + \text{B.C.D.} \quad (\text{Brush contact drop}) \\
 V_L &= R_{sh} \cdot I_{sh} = I_L \cdot R_L \\
 I_L &= \frac{\text{Load (in watts)}}{V_L} \\
 R_L &= \text{load resistance}
 \end{aligned}$$

## series wound



Series generator

(b)

$$I_L = I_a = I_{se}$$

$$E_g = V_L + I_a R_a + I_{se} R_{se}$$



$$= V_L + I_a (R_a + R_{se})$$

$$V_L = I_L \cdot R_L$$

# compound wound

long shunt

short shunt

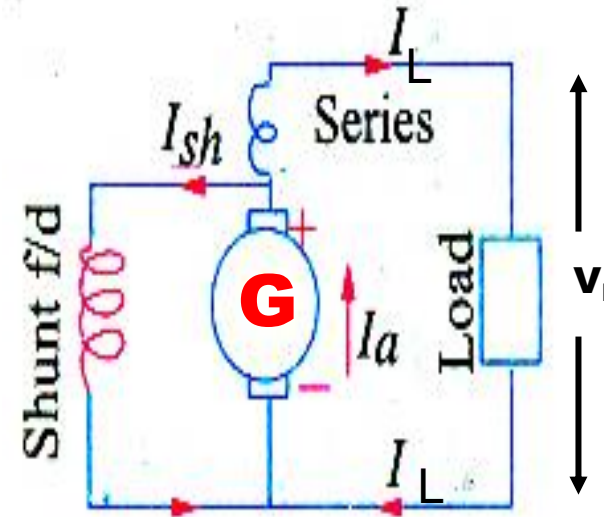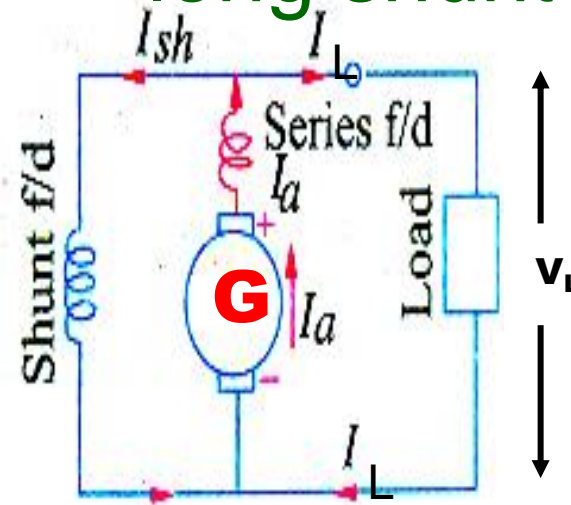

© Long shunt

$$I_a = I_{se} = I_L + I_{sh}$$

$$I_{sh} = \frac{V_L}{R_{sh}}$$

$$E_g = V_L + I_a R_a + I_{se} R_{se}$$

$$= V_L + I_a (R_a + R_{se})$$

$$I_{sh} = \frac{E_g - I_a (R_a + R_{se})}{R_{sh}}$$


© Short shunt

$$I_L = \frac{P_L \text{ (load in watts)}}{V_L}, \quad I_L = I_{se}$$

$$I_{sh} = \frac{V_L + I_{se} R_{se}}{R_{sh}}, \quad I_a = I_L + I_{sh}$$

$$E_g = V_L + I_a R_a + I_{se} R_{se}$$

# Power Stages in a DC Machine

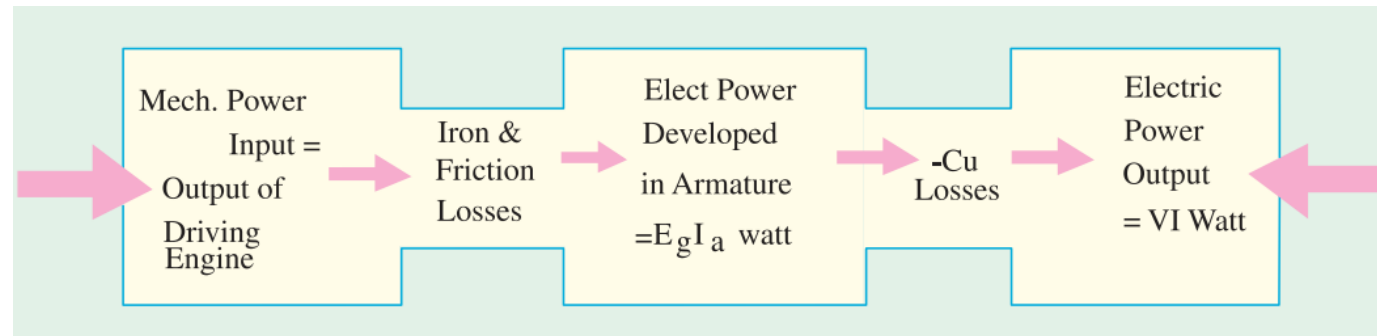

# Applications of D.C Generators

## Separately excited generators

- i) These are used for speed control of D.C motors over a large range.
- ii) These are used in areas where a wide range of terminal voltage is required

## Self excited generators

### i) shunt generators :-

- i) These are used as exciters for exciting the field of synchronous machines and separately excited D.C generators
- ii) These are used for battery charging because its terminal voltage are almost constant or can be kept constant.
- iii) Commonly used in ordinary lighting purposes and power supply purposes.


ii) series generators:-

- i) These are used for series arc lighting
- ii) Series incandescent lighting
- iii) As a series booster for increasing the voltage across the feeder to compensate the resistance drop of the line. because of their rising characteristic.
- iv) Special purposes such as supplying the field current for regenerative breaking of D.C locomotives (railway service).
- v) Constant current for welding.

iii) compound generators:-

- i) Compound generators are used where constant terminal voltages have to be maintained for different loading conditions.
- ii) Cumulatively compound generators:-These are for domestic lighting purposes and to transmit energy over long distance and for heavy power service such as electric railways.
- iii) Differential compound generator:- The use of this type of generators is very rare and it is used for special application like arc welding.

# Motors

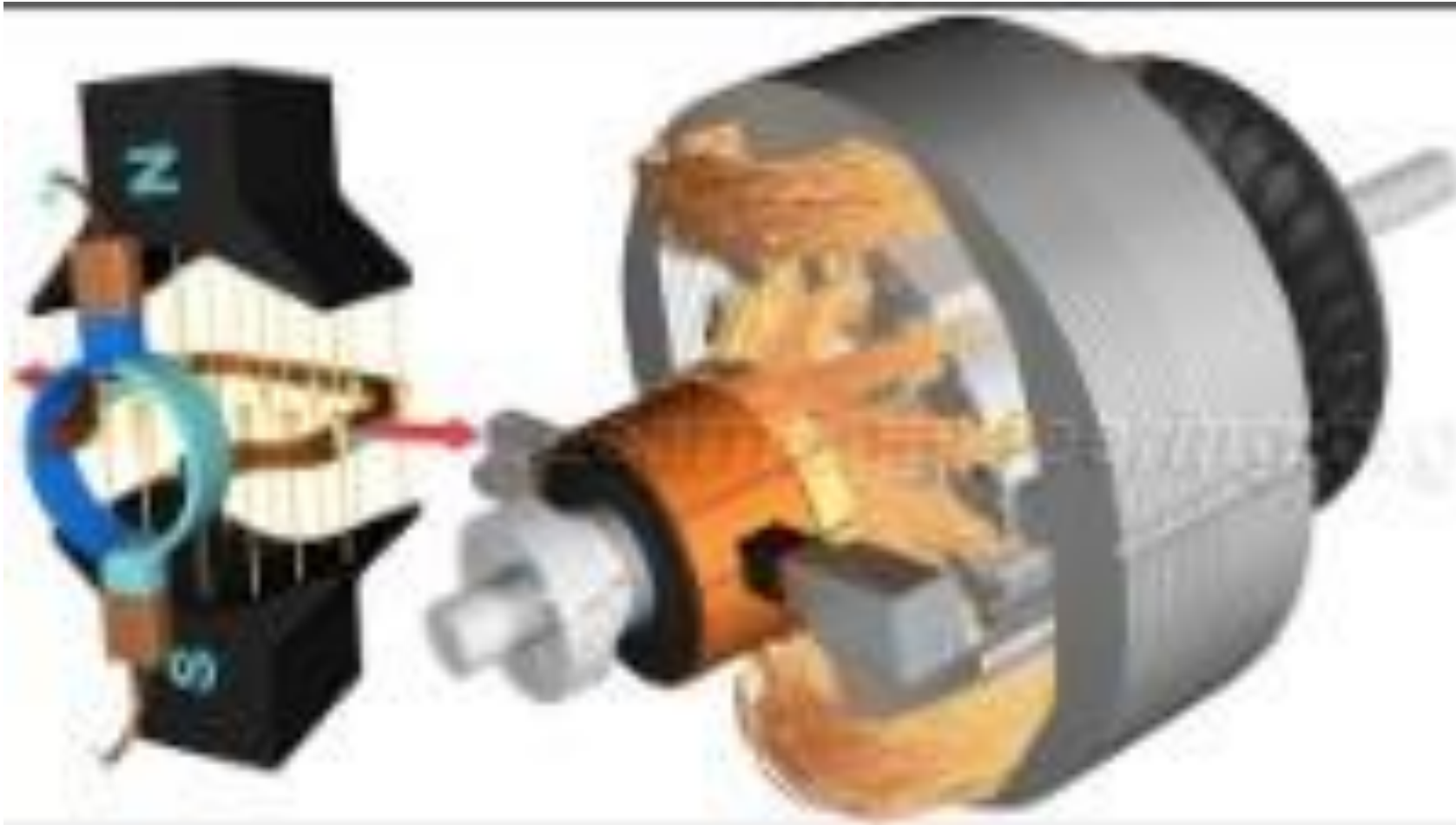


[Video](#)


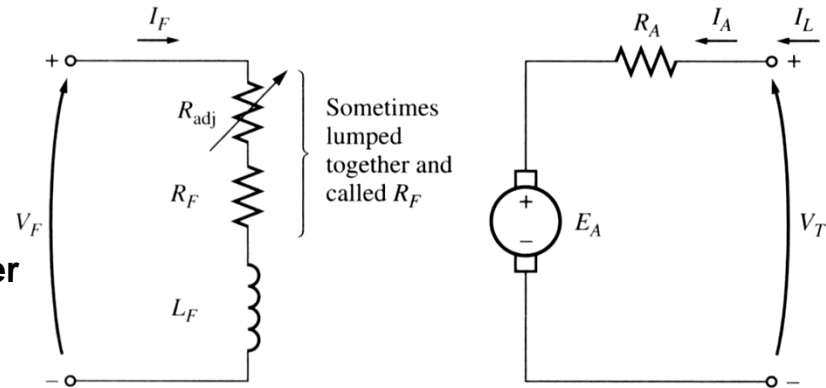
## Motor types: Separately Excited DC motors.

**Separately excited DC motor:**  
a field circuit is supplied from a  
separate constant voltage power  
source.



The Equivalent Circuit of Separately Excited dc Motor.

From the above figure,


$$I_F = \frac{V_F}{R_F}$$

$$V_T = E_A + I_A R_A$$

$$I_L = I_A$$
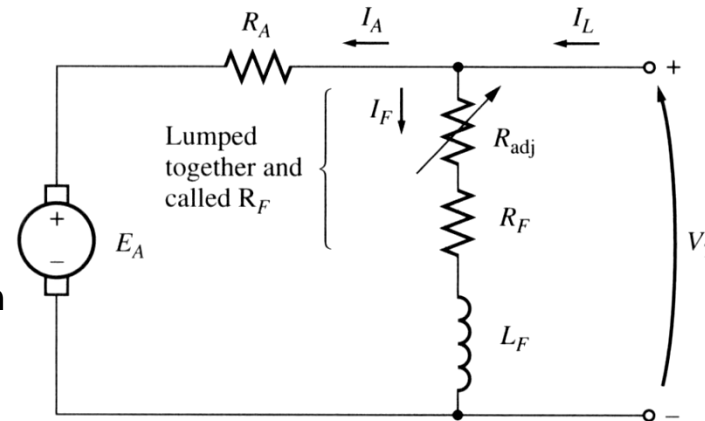
## Motor types: Shunt DC motors.

**Shunt DC motor:**  
a field circuit gets its power from  
the armature terminals of the  
motor.



The Equivalent Circuit of a Shunt dc

Motor.

✘ From the above figure,

$$I_F = \frac{V_F}{R_F}$$

$$V_T = E_A + I_A R_A$$

$$I_L = I_A + I_F$$

# Summary

Elementary generators

Construction of a DC  
machine

Types