

Unit - I

1.8 Capacitors

Dr.Santhosh.T.K.

CSP - Concentrating Solar-Thermal Power

Batteries

2017 → Zunum Aero

Eviation

↳ Alice

68

6

100 Vs 1100

↓
 Velis
Electro

Solar PV

↓
 ? → Storage

Solar Thermal

S

UNIT – I

10 Periods


Introduction and Basic Concepts: Concept of Potential difference, voltage, current - Fundamental linear passive and active elements to their functional current-voltage relation - Terminology and symbols in order to describe electric networks - Concept of work, power, energy and conversion of energy- Principle of batteries and application.

Principles of Electrostatics: Electrostatic field - electric field intensity - electric field strength - absolute permittivity - relative permittivity - capacitor composite – dielectric capacitors - capacitors in series & parallel - energy stored in capacitors - charging and discharging of capacitors.

Capacitors: the basics

What is a capacitor? $\rightarrow \Phi_{ans}$
 $\rightarrow \underline{TV}$

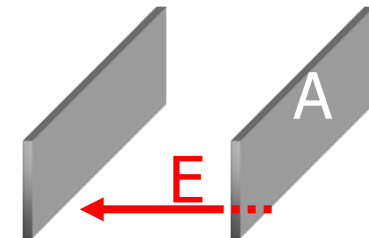- device for **storing charge**
- simplest example: two parallel conducting plates separated by air



V_0 \xleftarrow{d} V_1



assortment of
capacitors

How much charge can a capacitor store?

/ Supercapacitors

Better question: How much charge can a capacitor store per voltage?

Capacitance: $C = \frac{Q}{V}$

V is really $|\Delta V|$, the potential difference across the capacitor

capacitance C is a **device property**, it is always positive

unit of C: farad (F) *↙*

1 F is a large unit, most capacitors have values of C ranging from picofarads to microfarads (pF to μF).


micro $\Rightarrow 10^{-6}$, nano $\Rightarrow 10^{-9}$, pico $\Rightarrow 10^{-12}$ (Know for exam!)

Capacitance of parallel plate capacitor

electric field between two parallel charged plates:

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

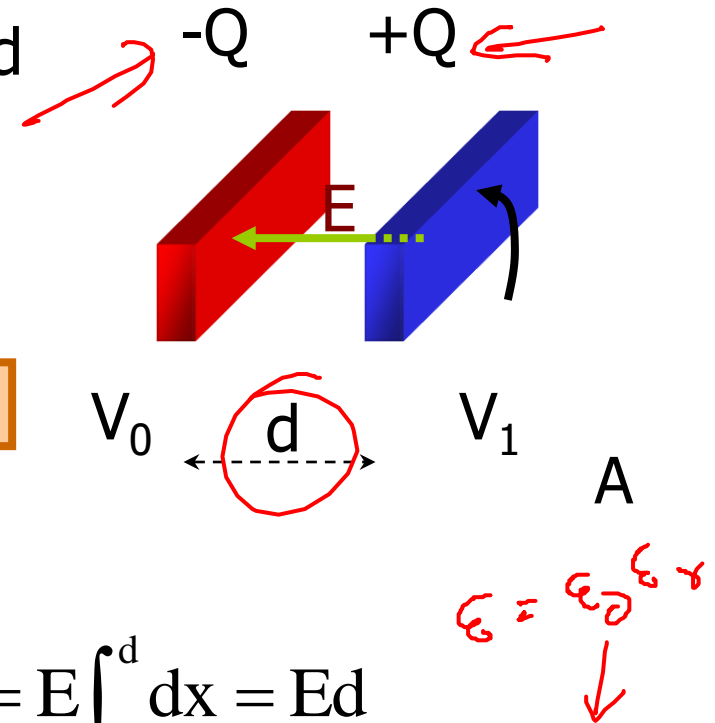Q is magnitude of charge on either plate.



potential difference:

$$\Delta V = V_1 - V_0 = -\int_0^d \vec{E} \cdot d\vec{\ell} = E \int_0^d dx = Ed$$

capacitance:

$$C = \frac{Q}{\Delta V} = \frac{Q}{Ed} = \frac{Q}{\left(\frac{Q}{\epsilon_0 A} \right) d} = \frac{\epsilon_0 A}{d}$$


Example: calculate the capacitance of a capacitor whose plates are 20 cm x 3 cm and are separated by a 1.0 mm air gap.

$$C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{(8.85 \times 10^{-12})(0.2 \times 0.03)}{0.001} \text{ F}$$

$$C = 53 \times 10^{-12} \text{ F}$$

$$C = 53 \text{ pF}$$

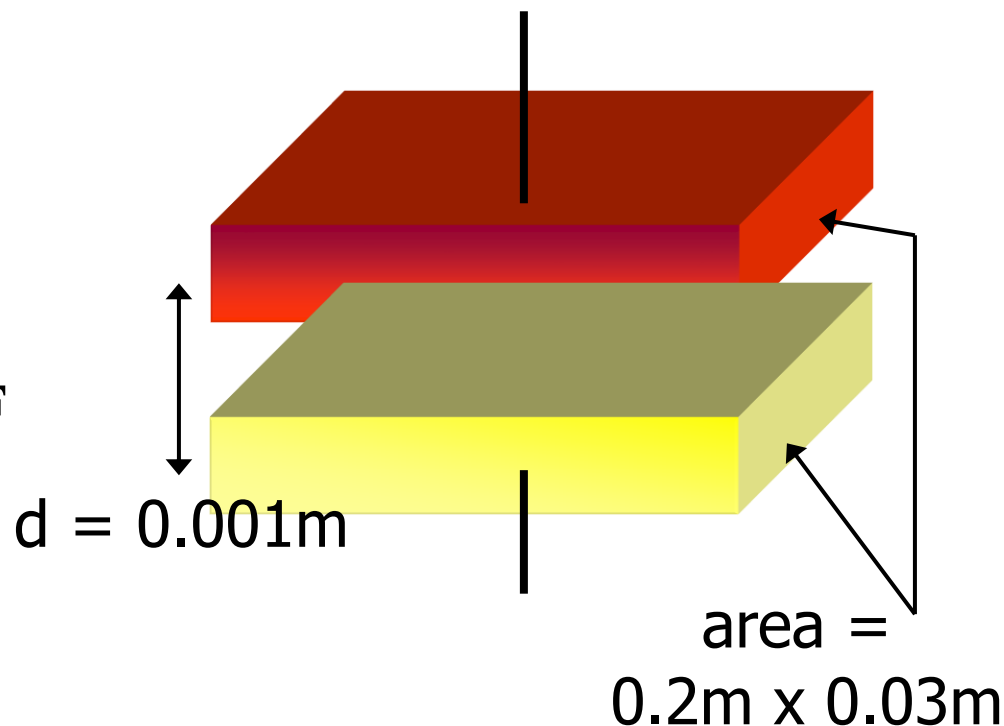


Example: what is the charge on each plate if the capacitor is connected to a 12 volt* battery?

↓

$$Q = CV$$

$$Q = (53 \times 10^{-12})(12) \text{ C}$$

$$Q = 6.4 \times 10^{-10} \text{ C}$$

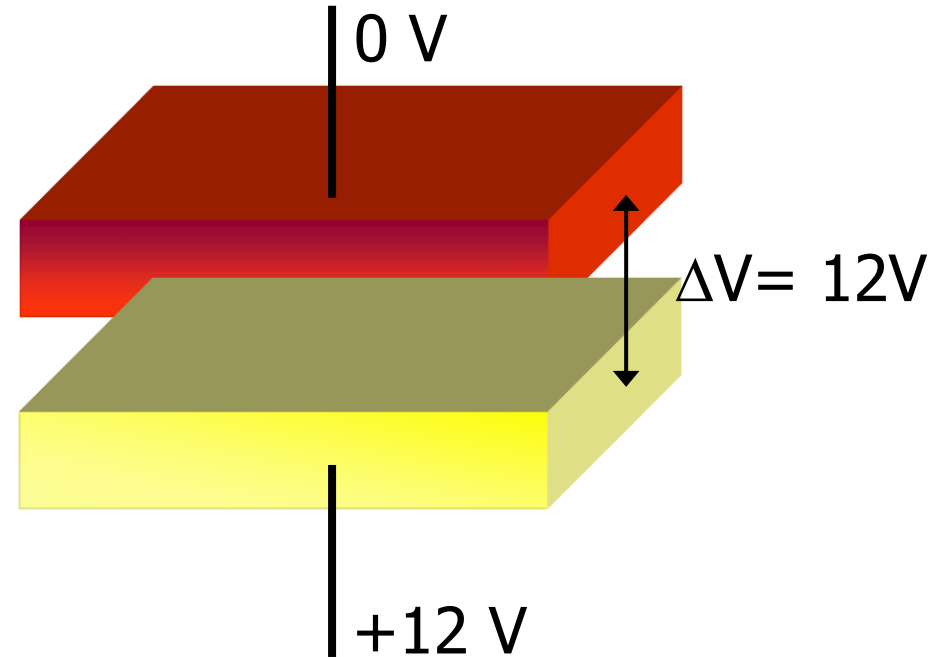


*Remember, it's the potential difference that matters.

Example: what is the electric field between the plates?



$$E = \frac{\Delta V}{d}$$

$$E = \frac{12\text{V}}{0.001\text{ m}}$$

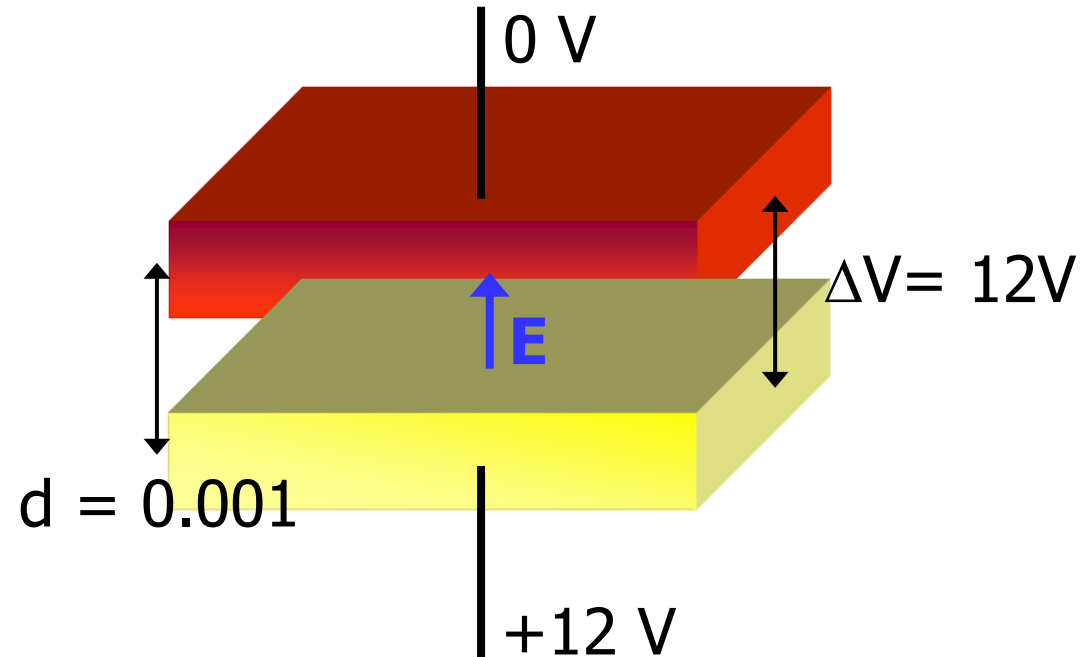
$$\vec{E} = 12000 \frac{\text{V}}{\text{m}}, \text{ "up."}$$




Capacitors in Series and Parallel

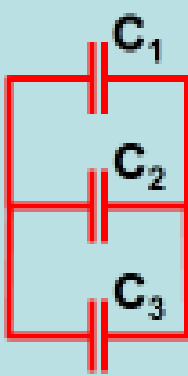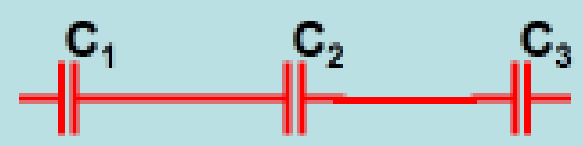	Parallel	Series
		
equivalent capacitance	$C_{eq} = \sum_i C_i$	$\frac{1}{C_{eq}} = \sum_i \frac{1}{C_i}$
charge	Q's add	V's add
voltage	same V	same Q

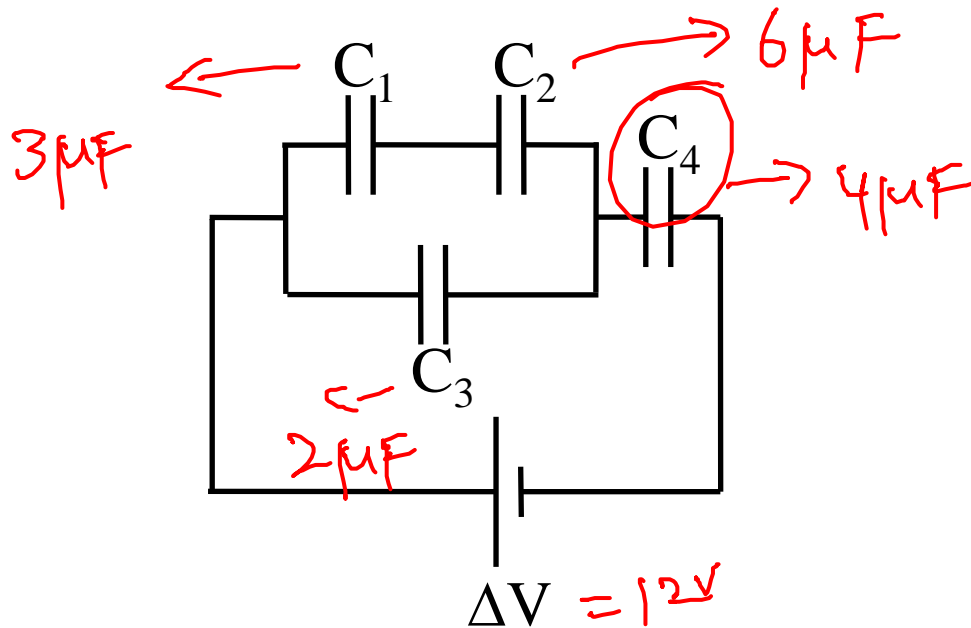Example: for the capacitor circuit shown, $C_1 = 3\mu\text{F}$, $C_2 = 6\mu\text{F}$, $C_3 = 2\mu\text{F}$, and $C_4 = 4\mu\text{F}$. (a) Find the equivalent capacitance. (b) if $\Delta V = 12\text{ V}$, find the potential difference across C_4 .



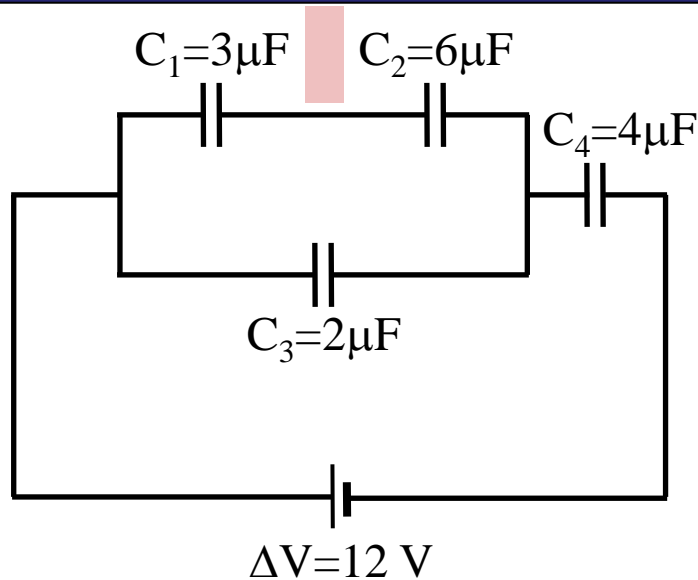(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



C_1 and C_3 are not in parallel. Make sure you understand why!


C_2 and C_4 are not in series. Make sure you understand why!

C_1 and C_2 are in series. Make sure you use the correct equation!

$$\frac{1}{C_{12}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{3} + \frac{1}{6} = \frac{2}{6} + \frac{1}{6} = \frac{3}{6} = \frac{1}{2}$$

Don't forget to invert: $C_{12} = 2 \mu\text{F}$.

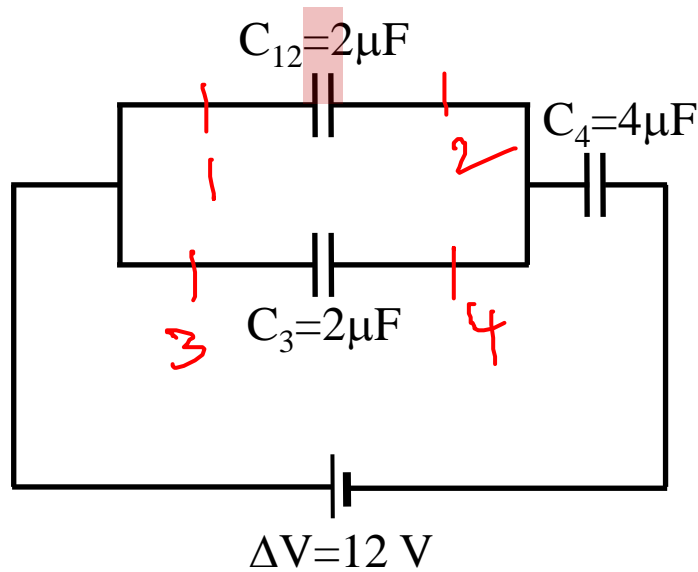(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .




C_{12} and C_4 are not in series. Make sure you understand why!

C_{12} and C_3 are in parallel. Make sure you use the correct equation!

$$C_{123} = C_{12} + C_3 = 2 + 2 = 4\mu\text{F}$$

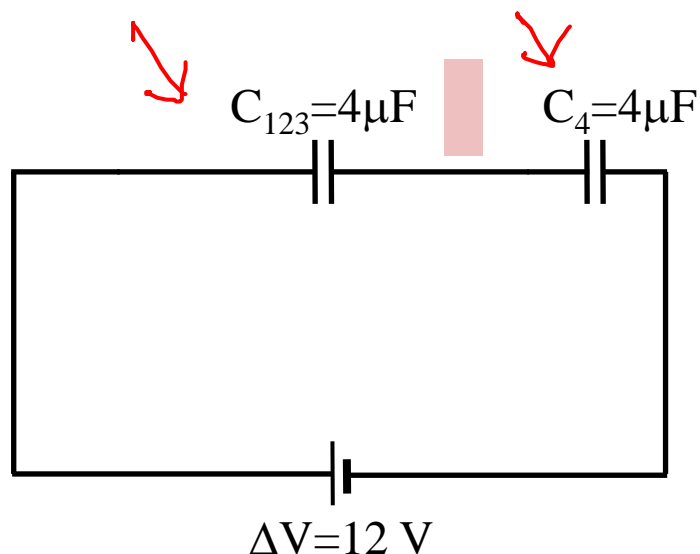(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



C_{123} and C_4 are in series. Make sure you understand why! Combined, they make give C_{eq} .


Make sure you use the correct equation!

$$\frac{1}{C_{eq}} = \frac{1}{C_{123}} + \frac{1}{C_4} = \frac{1}{4} + \frac{1}{4} = \frac{2}{4} = \frac{1}{2}$$

Don't forget to invert: $C_{eq} = 2 \mu\text{F}$.




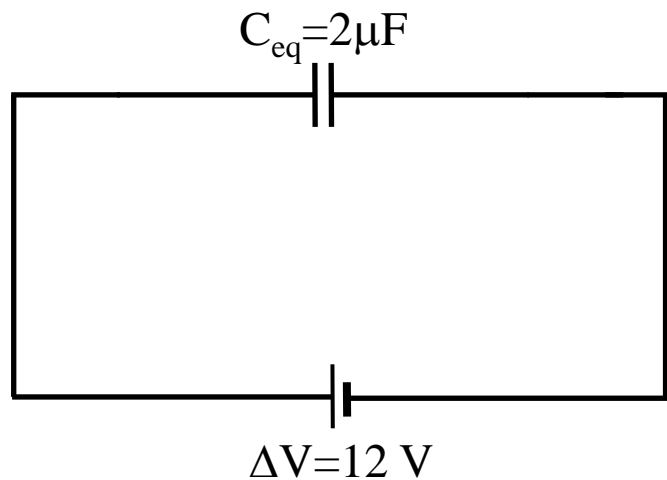(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



$$C_{eq} = 2 \mu\text{F}.$$


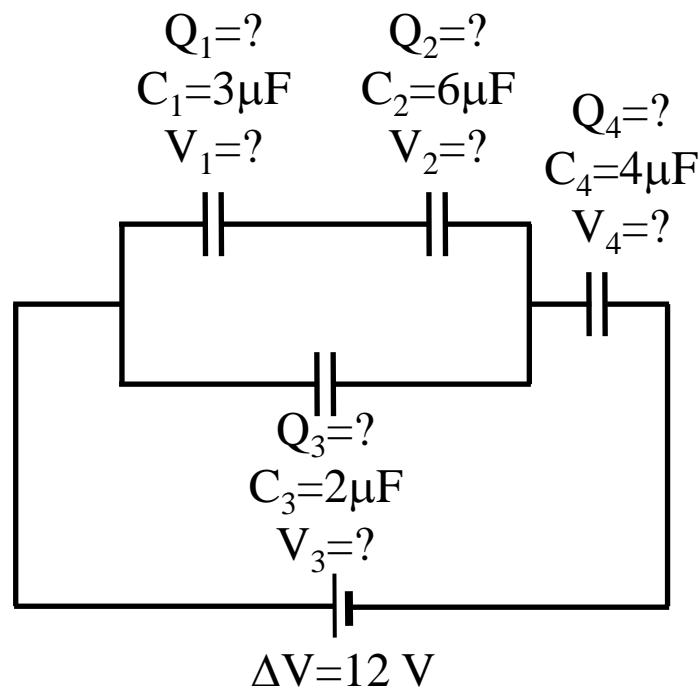
(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



Hint: each capacitor has associated with it a Q , C , and V . If you don't know what to do next, near each capacitor, write down $Q=$, $C=$, and $V=$. Next to the $=$ sign record the known value or a "?" if you don't know the value. As soon as you know any two of Q , C , and V , you can determine the third. This technique often provides visual clues about what to do next.

We know C_4 and want to find V_4 . If we know Q_4 we can calculate V_4 . Maybe that is a good way to proceed.

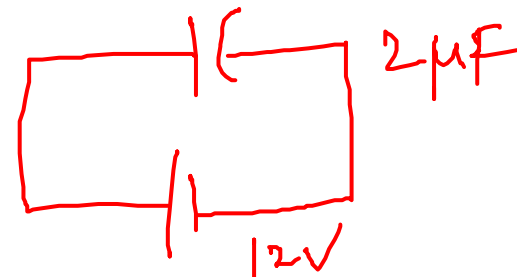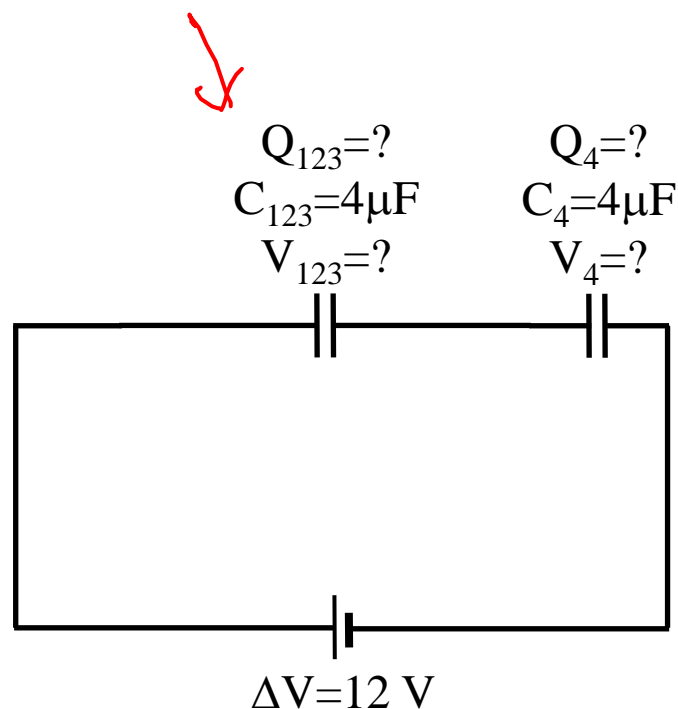(a) Find C_{eq} . (b) if $\Delta V = 12 \text{ V}$, find V_4 .



C_4 is in series with C_{123} and together they form C_{eq} .

Therefore $Q_4 = Q_{123} = Q_{eq}$.

$$Q_{eq} = C_{eq} \Delta V = (2)(12) = \underline{24\mu\text{C}} = \underline{Q_4}$$

$$C = \frac{Q}{V} \Rightarrow \underline{V} = \frac{Q}{C} \Rightarrow V_4 = \frac{Q_4}{C_4} = \frac{24}{4} = \underline{6\text{V}}$$


If you have to calculate the capacitance of a concentric spherical capacitor of charge Q ...

In between the spheres (Gauss' Law)

$$E = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$|\Delta V| = \frac{Q}{4\pi\epsilon_0} \int_a^b \frac{dr}{r^2} = \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{a} - \frac{1}{b} \right]$$

$$C = \frac{Q}{|\Delta V|} = \frac{4\pi\epsilon_0}{\left[\frac{1}{a} - \frac{1}{b} \right]}$$

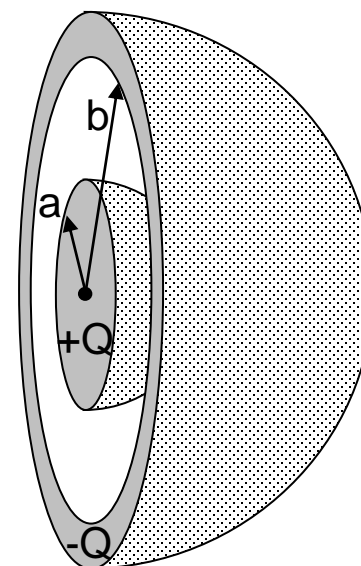

You need to do this derivation **if** you have a problem on spherical capacitors!

Energy Stored in Electrostatic Field of Capacitance

- The electrostatic field of the charge stored in the dielectric has electric energy supplied by the voltage source that charges C.
- Energy = $\epsilon = \frac{1}{2} CV^2$ (joules)
 - ✓ C = capacitance (farads)
 - ✓ V = voltage across the capacitor
 - ✓ ϵ = electric energy (joules)
- Stored energy is the reason why a charged capacitor can produce electric shock even when it is not connected into a circuit.

Problem

- A parallel plate capacitor with a plate of 0.25 m^2 and a plate separation of 6.00 mm is connected with 12 V source. Find:
 - (a) Charge on the capacitor
 - (b) Energy stored in the capacitor
 - (c) Potential difference across the capacitor is reduce to half, explain what will happen to charge on the capacitor and its stored energy

$$C = \frac{\epsilon_0 A}{d}$$

$$U_C = \frac{1}{2} CV^2$$

$$\begin{aligned} \text{(a)} \quad C &= \frac{\epsilon_0 A}{d} \\ &= \frac{(8.854 \times 10^{-12})(0.25 \text{ m}^2)}{0.006 \text{ m}} \\ &= 36.9 \times 10^{-9} \text{ F} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad U_c &= \frac{1}{2} CV^2 \\ &= \frac{1}{2} (36.9 \times 10^{-9} \text{ F})(12 \text{ V})^2 \\ &= 2.66 \times 10^{-6} \text{ J} \end{aligned}$$

(c) Since $Q = CV$, it halves.
Since $UC = \frac{1}{2} CV^2$, it doubles.

Problem

- *Given some capacitors of $0.1 \mu\text{F}$ capable of withstanding 15V . Calculate the number of capacitors needed if it is desired to obtain a capacitance of $0.1 \mu\text{F}$ for use in a circuit involving 60 V .*

Problem

- *Given some capacitors of $0.1 \mu\text{F}$ capable of withstanding 15V . Calculate the number of capacitors needed if it is desired to obtain a capacitance of $0.1 \mu\text{F}$ for use in a circuit involving 60 V .*

Summary

Capacitors → Electrostatics

→ Definition

→ Equations

→ Series / parallel

→ Energy

/ synthesis ?
↑